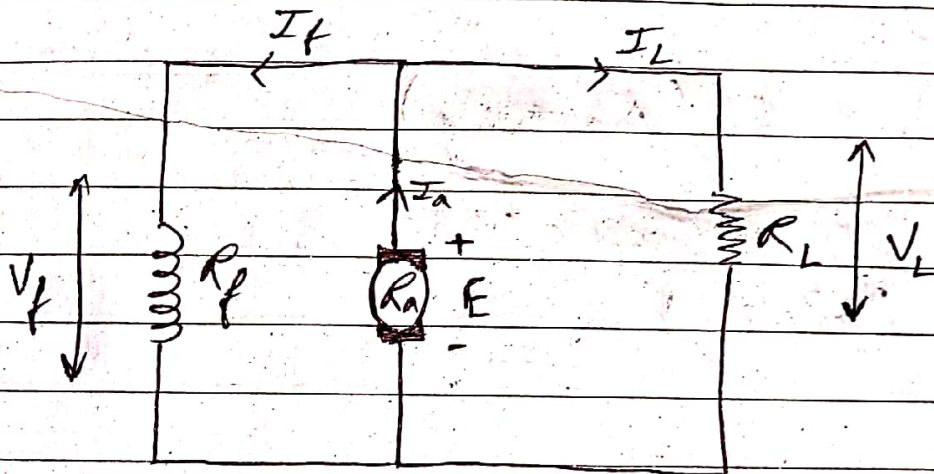


Assignment: 03 (DC Generator)

Bilwash Khanal
BCT A
Roll No: 34

- 1.) Shunt Generator gives full load output of 30 kW at a terminal voltage of 200 V. The armature and field resistance are 0.05Ω and 50Ω respectively. The iron & Friction Loss are 1000 W. Calculate Generated voltage ~~if~~, current and copper loss. Also calculate the efficiency here,

We know that for a shunt generator;



given;

$$V_L = 200 \text{ V}$$

$$R_a = 0.05 \Omega$$

$$R_f = 50 \Omega$$

$$(W_i + W_f) = 1000 \text{ W}$$

$$\text{Power o/p} = 30 \text{ kW}$$

So,

$$30 \text{ kW} = I_L \times V_L$$

$$\therefore I_L = \frac{30,000}{200} = 150 \text{ A}$$

$$\therefore R_L = \frac{200}{150} = 1.33 \Omega$$

then, we have

$$I_L \times R_L = I_f \times R_f \quad [\text{parallel branches}]$$

So,

$$V_L = I_f \times R_f$$

$$\text{or, } I_f = \frac{200}{50} = 4 \text{ A}$$

then, we have

$$\begin{aligned} I_a &= I_L + I_f \\ &= 150 + 4 = 154 \text{ A} \quad \underline{\text{Ans}} \end{aligned}$$

Now, using emf equation for shunt generator,

$$E = V_L + I_a (R_a)$$

$$= 200 + 154 \times 0.05$$

$$= 207.7 \text{ V} \quad \underline{\text{Ans}}$$

then,

$$\text{Copper loss} = I_a^2 R_a + I_f^2 R_f$$

$$= 1185.8 + 80$$

$$= 1985.8 \text{ W} \quad \underline{\text{Ans}}$$

$$\eta = \frac{P_{out}}{P_{out} + W_c + W_i + W_f} \times 100 \%$$


$$= \frac{30000}{30000 + 1000 + 1985.8}$$

$$= 90.948 \%$$

$$\underline{\text{Ans}}$$

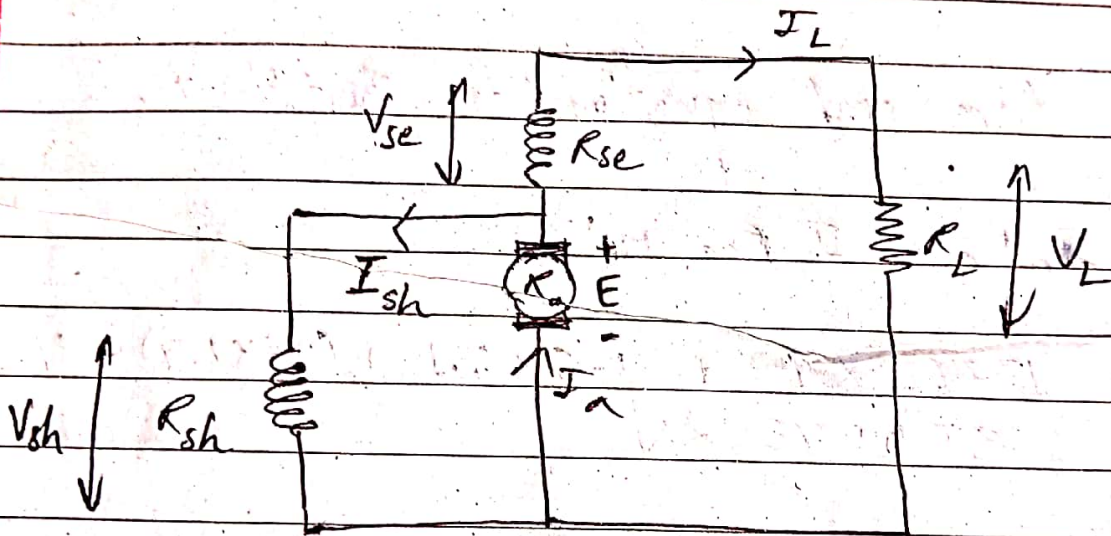- 2.) A short shunt compound dc generator supplies a load current of 175 A to a series of parallel heater load whose effective resistance is $1.4\ \Omega$. The generator has armature, series and shunt field resistance are $15\ \Omega$, $0.1\ \Omega$ and $100\ \Omega$ respectively. Calculate emf generated if carbon brush drop per brush is 2 V .

We know that, for a compound short shunt generator,



given,

$$\begin{aligned} I_L &= 175\text{ A}, \\ R_L &= 1.4\ \Omega \\ R_a &= 15\ \Omega \\ R_{se} &= 0.1\ \Omega \\ R_{sh} &= 100\ \Omega \\ V_{\text{brush}} &= 2 \times 2 = 4\text{ V} \end{aligned}$$

here,

$$I_L \times R_L + I_L \times R_{se} = I_{sh} \times R_{sh} \quad (\text{Parallel branches})$$
$$\text{or, } 175(1.4 + 0.1 \Omega) = I_{sh} \times 100$$

$$\text{or, } I_{sh} = 2.625 \text{ A}$$

So, using KCL,

$$\begin{aligned} I_a &= I_{sh} + I_L \\ &= 2.625 + 175 \\ &= 177.625 \text{ A} \end{aligned}$$

then,

we have, from emf equation for short shunt - -

$$-V_{\text{brush}} + E = I_a R_a + I_L R_{se} + V_L$$

$$\begin{aligned} \text{or, } E &= 177.625 \times 15 + 175 \times 0.1 + (175 \times 1.4) + 4 \\ &= 2936.875 \text{ KV} \end{aligned}$$

Ans

then,

$$\begin{aligned} \text{Copper loss} &= I_a^2 R_a + I_{sh}^2 R_{sh} + I_L^2 R_{se} \\ &= 177.625^2 \times 15 + 2.625^2 \times 100 + 175^2 \times 0.1 \\ &= 477011 \end{aligned}$$

then,


$$\text{efficiency} = \frac{I_L \times V_L}{E \times I_a} \times 100 \%$$

$$\begin{aligned} &= \frac{175 \times 1.4}{2936.875 \times 177.625} \times 100 \\ &= 8.235\% \end{aligned}$$

Ans

Ans.

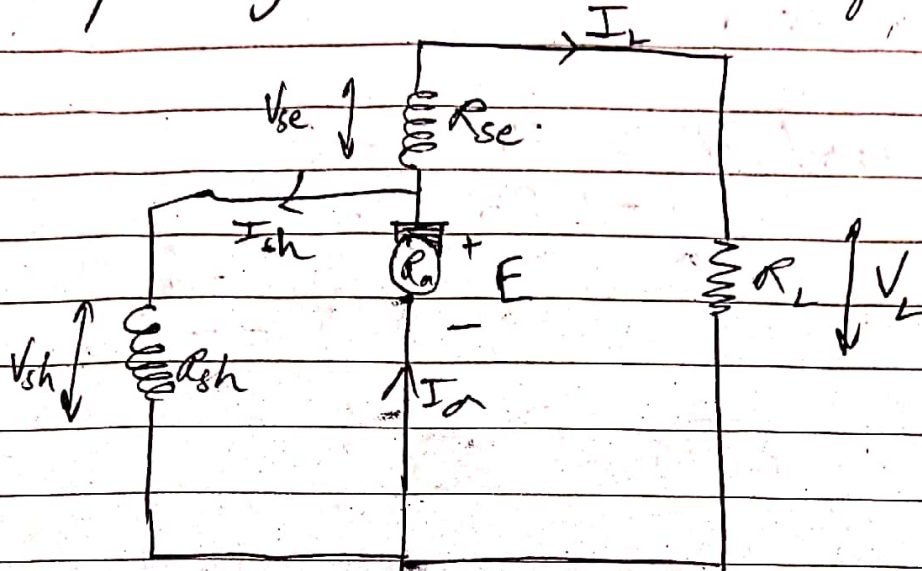- 3.) A short shunt Cumulative Compound generator supplies 7.5 kW at 230 V. The shunt, field, series field and armature resistance are 100, 0.3 & 0.4 Ω respectively. Calculate induced emf & load resistance.



Here, given,

$$V_L = 230 \text{ V}$$

$$P_{out} = 7.5 \text{ kW}$$

$$\therefore I_L = \frac{7.5 \text{ kW}}{230 \text{ V}} = 32.608 \text{ A}$$

also,

$$R_{sh} = 100 \Omega$$

$$R_{se} = 0.3 \Omega$$

$$R_a = 0.4 \Omega$$

$$\therefore R_L = \frac{V_L}{I_L} = \frac{230}{32.608} = 7.053 \Omega$$

So,

$$V_{sh} = V_{se} + V_L$$

$$I_{sh} \times R_{sh} = I_L (0.3 + R_L)$$

$$\therefore I_{sh} = \frac{32.608 (0.3 + 7.053)}{100} = 2.397 \text{ A}$$

$$\therefore I_a = 32.608 + 2.397 = 35 \text{ A}$$


Then, we have the emf equation,

$$\begin{aligned} E &= I_a R_a + I_f R_{se} + I_L R_L \\ &= 35 \times 0.4 + 32.608 \times 0.3 + 230 \\ &= 253.78 \text{ V} \end{aligned}$$

$$\begin{aligned} \therefore \text{Load Resistance} &= 7.053 \Omega \\ \therefore \text{Emf}_{\text{gen}} &= 253.78 \text{ V} \end{aligned}$$

Ans

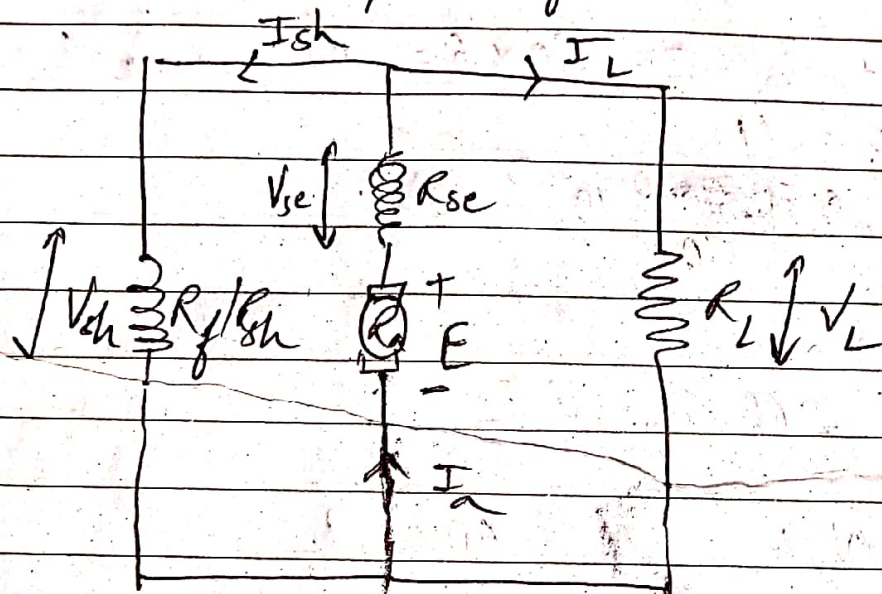- 4.) 4 pole 250 V dc long shunt C. generator supplies a load of 10 kW at rated voltage. The armature series and shunt field resistance are 0.1Ω , 0.15Ω and 250Ω respectively. Armature is lap wound with 50 slots, each slot containing 6 conductors. If the flux per pole is 50 mwb, calculate the speed of generator. What would be the speed if armature is wave wound?



Here,

$$V_L = 250 \text{ V}, \quad P_{\text{out}} = 10 \text{ kW}$$

$$\therefore I_L = \frac{10 \text{ kW}}{250 \text{ V}} = \underline{\underline{40 \text{ A}}}$$

also,

$$R_a = 0.1 \Omega$$

$$R_{se} = 0.15 \Omega$$

$$R_{sh} = 250 \Omega$$

then,

$$V_{sh} = V_L$$

$$\therefore I_{sh} = \frac{250}{R_{sh}} = 1 \text{ A}$$

$$\therefore I_a = I_{sh} + I_L$$

$$= \underline{\underline{41 \text{ A}}}$$

Then, we have, the eqn equation,

$$\begin{aligned} E &= V_L + I_a(R_a + R_{se}) \\ &= 250 + 41(0.1 + 0.15) \\ &= 260.25 \text{ V} \end{aligned}$$

then, for lap wound,

$$P = 4, \quad Z = 50 \times 6 = 300 \text{ conductors}$$

$$A = P = 4$$

$$\Phi = \frac{0.005}{50} \times 10^{-3} \text{ wb}$$

$$N = ?$$

$$E = 260.25 \text{ V}$$

So,

$$N = \frac{E \times 60 \times A}{\Phi \times Z \times P}$$

$$= \frac{260.25 \times 60 \times 4}{50 \times 10^{-3} \times 300 \times 4}$$

$$= 1041 \text{ rpm}$$

$$= 1041 \text{ rpm} \underline{\underline{\text{Ans}}}$$

for wave wound, $A = 2$, so,

$$N = \frac{260.25 \times 60 \times 2}{50 \times 10^{-3} \times 300 \times 4} = 520.5 \text{ rpm}$$

Ans


- 5.) In a 220 V compound generator, the armature series and shunt windings have resistances of 0.3Ω , 0.2Ω & 60Ω respectively. The load consists of 80 lamps each rated at 60 W and 220 V. Find the total emf and armature current when the machine is connected for
- long shunt
 - short shunt.

here,

$$V_L = 220 \text{ V}$$

$$P_{out} = 60 \times 80 = 4800 \text{ W}$$
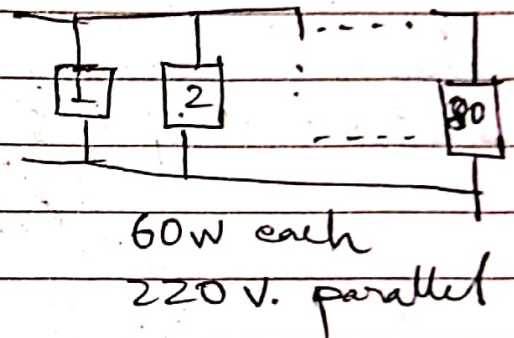
$$\therefore I_L = \frac{4800}{220} = 21.81$$




then,

$$R_a = 0.3$$

$$R_{se} = 0.2 \Omega$$

$$R_{sh} = 60 \Omega$$

(i) long shunt

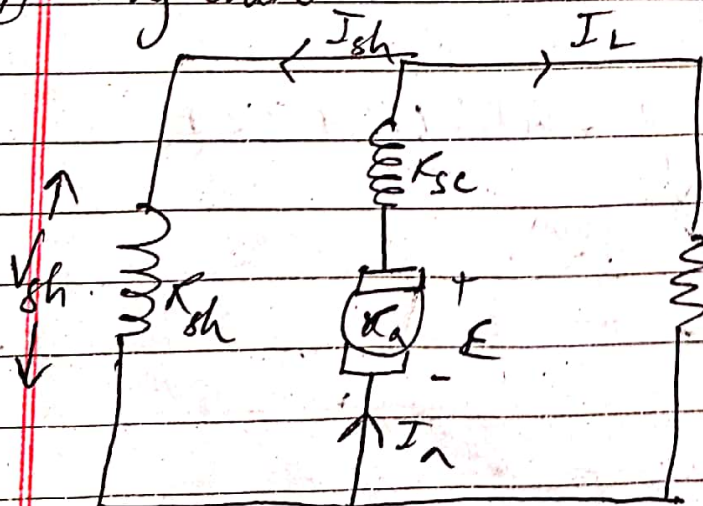

here, $I_{sh} = \frac{V_L}{R_{sh}} = 3.67 \text{ A}$

$$I_a = I_L + I_{sh} = 21.81 + 3.67 = 25.476 \text{ A}$$


$$E = V_L + I_a (R_a + R_{se})$$

$$= 220 + 25.476(0.3 + 0.2)$$

$$= 232.738 \text{ V}$$

Ans

Short Shunt

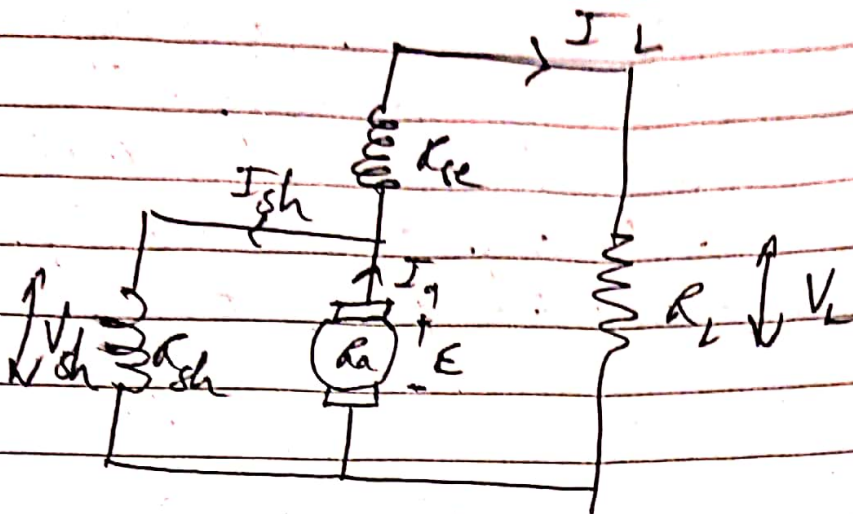

here,

$$I_{sh} = \frac{V_L + I_L R_{se}}{R_{sh}} = \frac{220 + 4.362}{60} = 3.739 \text{ A}$$

then

$$I_a = 21.81 + 3.739 = 25.5493 \text{ A}$$

then,

$$E = I_a R_a + I_L R_{se} + V_L$$


$$= 25.5493 \times 0.3 + 21.81 \times 0.2 + 220 = 232.026 \text{ V}$$

Ans

Q. A 4 pole dc shunt generator has wave wound armature. The armature and field winding resistance are 0.25Ω and 60Ω respectively. The brush contact drop is $1V$ per brush. The generator is delivering a power of $3 kW$ at $120 V$. Calculate

- (i) Total armature current coming out from the brush
- (ii) Current in each armature conductor
- (iii) Generated emf.

Here,

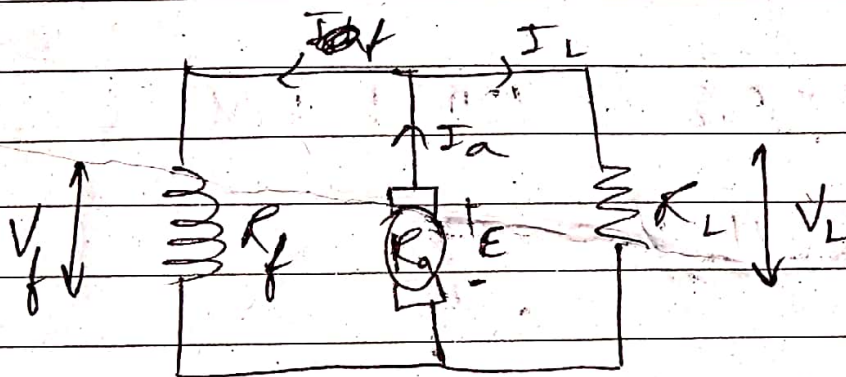

Here,

$$P_{out} = 3 kW,$$

$$V_L = 120 V$$

$$\therefore I_L = 25 A$$

then,

$$R_a = 0.25 \Omega \quad \rightarrow \quad V_{brush} = 1 \times 2 = 2 V$$

$$R_f = 60 \Omega$$

so,

$$I_f = \frac{V_L}{R_f} = \frac{120}{60} = 2 A$$

$$\therefore I_a = I_f + I_L = 2 + 25 = 27 A$$

(i) \therefore Total armature current 27 A

Let, the number of conductors be x
then,

(ii) \therefore Current per conductor = $\frac{27}{x}$ A

(iii) We have, the emf formula,

$$E = I_a R_a + V_L + V_{\text{brush}}$$

$$= 27 \times 0.2 + 120 + 2 \text{ V}$$

$$= 127.4 \text{ V}$$