


# Star-delta Tutorial - 5'

classmate

Date \_\_\_\_\_

Page \_\_\_\_\_

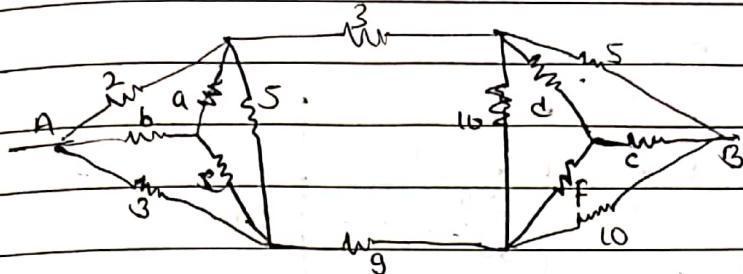- Q.1. Find the voltage to be applied across AB in order to drive a current of 5A into the circuit of figure 1 by using star delta transformation.



Let a, b, c, d, e, f, be equivalent star connection of the two delta circuit now.

$$a = \frac{2 \times 5}{2+3+5} = \frac{10}{10} \Omega$$

$$d) = \frac{10 \times 5}{10+5+10} = 2 \Omega$$


$$b = \frac{2 \times 3}{2+3+5} = \frac{6}{10} \Omega$$

$$e) = \frac{10 \times 5}{10+5+10} = 2 \Omega$$

$$c) = \frac{3 \times 3}{2+3+5} = \frac{9}{10} \Omega$$

$$f) = \frac{10 \times 10}{10+5+10} = 4 \Omega$$

Redrawing (kt)

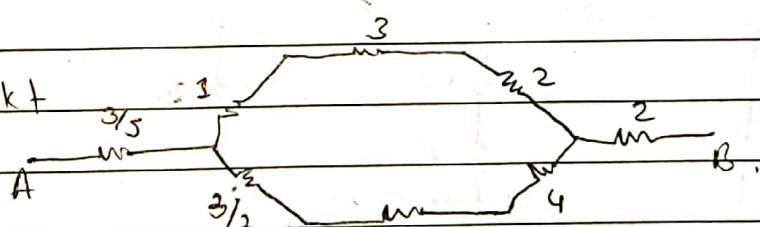

$$R_{eq} = \frac{3}{5} + \left[ \left( 1 + \frac{3}{5} + \frac{3}{2} \right) / \left( \frac{3}{5} + \frac{3}{2} + 4 \right) \right] + 2$$


$$= \frac{3}{5} + \left[ \left( 1 + \frac{3}{5} + \frac{3}{2} \right) / \left( \frac{3}{5} + \frac{3}{2} + 4 \right) \right] + 2$$

$$= \frac{3}{5} + \frac{174}{111} + 2$$

$$= 6.843 \Omega$$

$$\text{For } 5 \text{ A current } V_{AB} = IR = 5 \times 6.843 \\ = 34.2 \text{ V.}$$

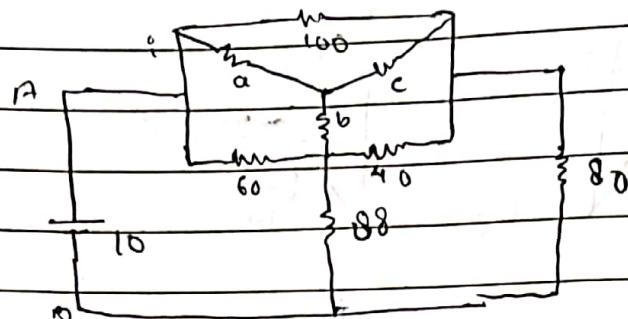2. Calculate the current I in the circuit if the resistance b/w the terminals A & B as shown in fig. 2. by using star-delta transformation.




Let a, b, c be equivalent star connection - Now,

$$a = \frac{100 \times 60}{100 + 60 + 40} = 30 \Omega, \quad b = \frac{60 \times 40}{60 + 40 + 100} = 12 \Omega$$

$$c = \frac{100 \times 40}{100 + 60 + 40} = 20 \Omega$$


The Ckt can be redrawn as

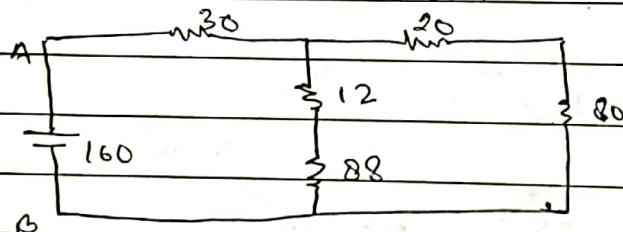

$$\begin{aligned} R_{eq} &= [(80 + 20) / (12 + 8)] + 30 \\ &= [100 / 100] + 30 \\ &= \frac{100 \times 100}{100 + 100} + 30 \\ &= 80 \Omega \end{aligned}$$


$$\begin{aligned} \text{Current } (I) &= \frac{160}{R_{eq}} = \frac{160}{80} \\ &= 2 \text{ A} \end{aligned}$$

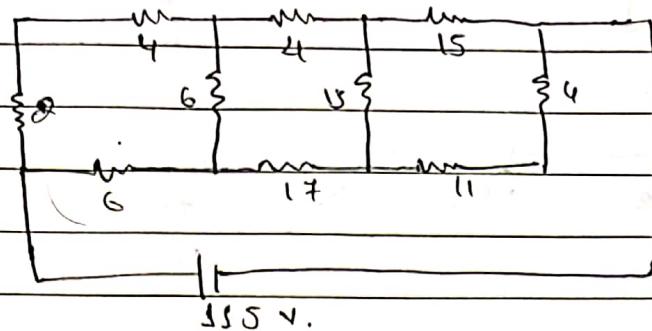3. Find the current in  $11\Omega$  resistor using star delta conversion.



$\Rightarrow$  Soln,


The Ckt can be redrawn as:

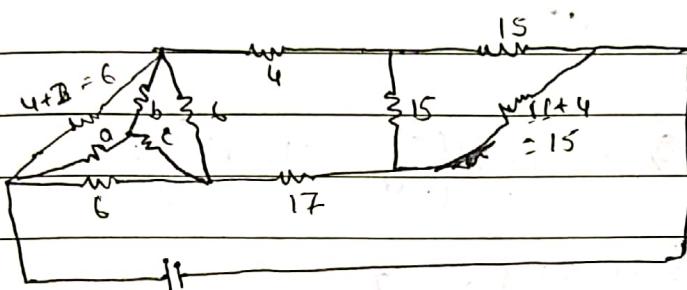

using star delta  $115V$

$$a = b = c = \frac{6 \times 6}{6+6+6} = 2\Omega$$

now, Redrawing Ckt

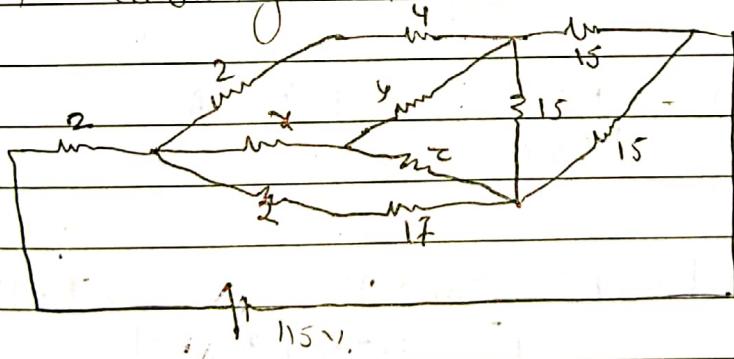

Using star delta conversion

$$x = \frac{(4+2)(2+17)}{(4+2)(2+17)+15} = \frac{57}{20}\Omega$$


$$z = \frac{15 \times (12+17)}{15+(2+17)(4+2)} = \frac{51}{8}\Omega$$

$$y = \frac{(4+2) \times 15}{(4+2)(2+17)+15} = \frac{9}{4}\Omega$$

$$= \frac{51}{8}\Omega$$

(2)

Redrawing the circuit.

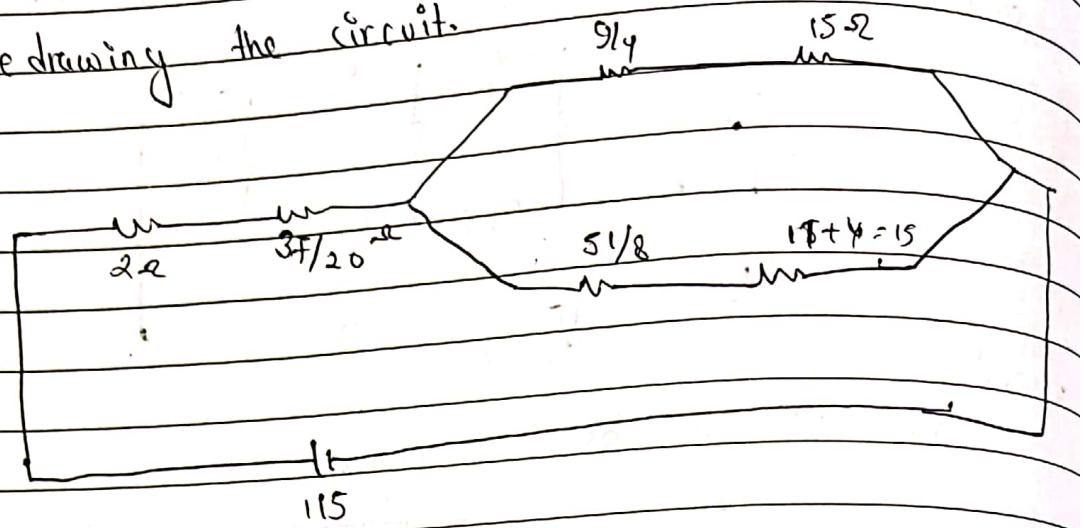


$$\begin{aligned}
 \text{Req.} &= \left[ \left( \frac{9}{4} + 15 \right) \parallel \left( \frac{51}{8} + 11 + 4 \right) \right] + \frac{57}{20} + 2 \\
 &= \left[ \frac{69}{4} \parallel \frac{171}{8} \right] + \frac{57}{20} + 2 \\
 &= \frac{39.88}{11.2} + \frac{57}{20} + 2 \\
 &= 14.39 \Omega
 \end{aligned}$$

$$\text{Total current } (I) = \frac{115}{14.39} = 7.988 \text{ A}$$

$$\begin{aligned}
 \text{Current through } (I_1) &= \frac{9V + 15}{\left( \frac{51}{8} + 11 + 4 \right) + \left( \frac{9}{4} + 15 \right)} \times 7.988 \\
 &= 3.56 \text{ A}
 \end{aligned}$$

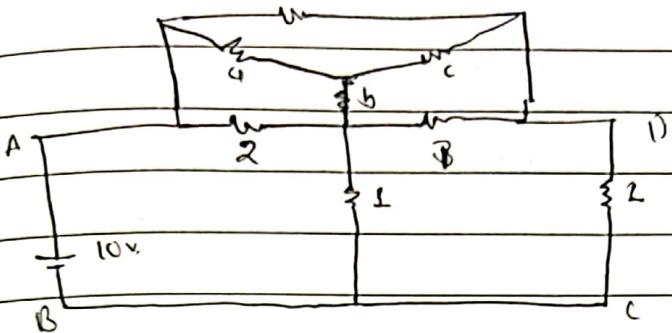Q. In the circuit given in fig. (1) calculate the amount through branch CD using star delta conversion.




Let a, b, c be equivalent star connection of delta connection  $2\Omega, 2\Omega, 4\Omega$  so

$$a = \frac{2 \times 2}{2+2+1} = \frac{4}{5} \Omega$$

$$b = \frac{2 \times 1}{2+2+1} = \frac{2}{5} \Omega$$

$$c = \frac{2 \times 1}{2+2+1} = \frac{2}{5} \Omega$$

The ckt can be redrawn as,

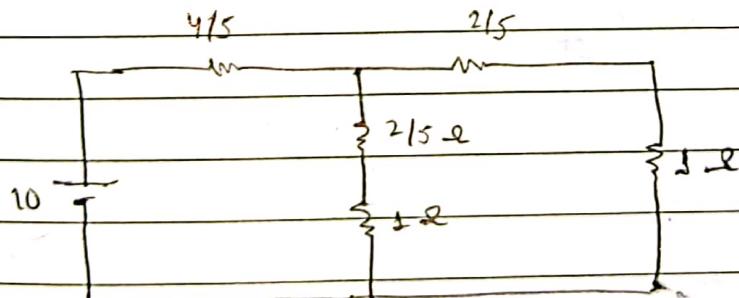

$$R_{eq} = \left[ \left( \frac{2}{5} + 1 \right) || \left( \frac{2}{5} + 1 \right) \right] + \frac{4}{5}$$

$$= \left[ \frac{7}{5} || \frac{7}{5} \right] + \frac{4}{5}$$

$$= \frac{\frac{7}{5} \times \frac{7}{5}}{\frac{7}{5} + \frac{7}{5}} + \frac{4}{5}$$

$$= \frac{\frac{49}{25}}{\frac{14}{5}} + \frac{4}{5} = 1.5 \Omega$$

total current ( $I$ ) =  $\frac{V}{R_{eq.}}$

$$= \frac{10}{1.5}$$

$$= 6.67 \text{ A}$$

Using CDP,

$$I_{eq} = \frac{\frac{2}{5} + 1}{(\frac{2}{5} + 1)(\frac{2}{5} + 1)} \times 6.67$$


$$= \frac{\frac{7}{2}}{\frac{7}{2} + \frac{7}{2}} \times 6.67$$

$$= \frac{\frac{7}{2}}{\frac{14}{2}} \times 6.67$$


$$= \frac{1}{2} \times 6.67$$

$$= 3.33 \text{ A}$$

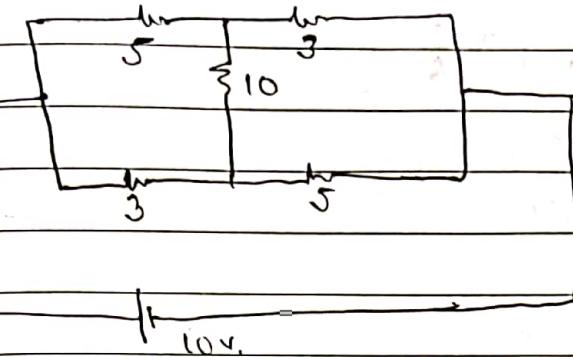5. Find the current in  $10\ \Omega$  resistor in fig. 5, using star delta transformation.



The ckt can be redrawn as:

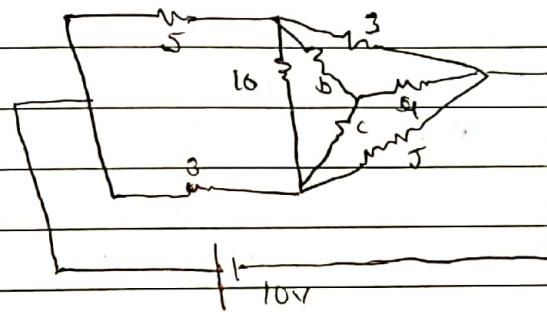


Changing the delta connection of  $10\ \Omega$ ,  $3\ \Omega$  &  $5\ \Omega$  into star connection.

$$a = \frac{3 \times 5}{3 + 5 + 10} = \frac{5}{6} \ \Omega$$

$$b = \frac{5}{3} \ \Omega$$

$$c = \frac{10 \times 5}{3 + 5 + 10} = \frac{25}{9} \ \Omega$$

The ckt can be redrawn as

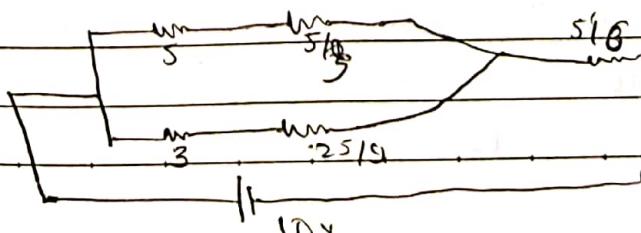

$$\begin{aligned}
 R_{eq} &= \left[ \left( 5 + \frac{5}{3} \right) || \left( 3 + \frac{25}{9} \right) \right] + \frac{5}{6} \\
 &= \left[ \frac{20}{3} || \frac{52}{9} \right] + \frac{5}{6} \\
 &= \frac{\frac{20}{3} \times \frac{52}{9}}{\frac{20}{3} + \frac{52}{9}} + \frac{5}{6} \\
 &= \frac{65}{21} + \frac{5}{6} \\
 &= 3.928 \text{ ohms}
 \end{aligned}$$

$$\begin{aligned}
 \text{Total current } (I) &= \frac{V}{R_{eq}} = \frac{10}{3.928} \\
 &= 2.54 \text{ A.}
 \end{aligned}$$

Using CDR

$$I_1 = \frac{3 + \frac{25}{9}}{(3 + \frac{25}{9}) + (5 + \frac{5}{3})} \times 2.54$$

$$I_1 = 1.179 \text{ A}$$

$$\begin{aligned}
 I_2 &= 2.54 - 1.179 \\
 &= 1.361 \text{ A}
 \end{aligned}$$


Applying KVL.

$$\begin{aligned}
 -5I_1 - 10I_{10} + 3I_2 &= 0 \\
 -5(1.179) - 10I_{10} + 3(1.361) &= 0 \\
 -10I_{10} &= 1.812
 \end{aligned}$$

$$I_{10} = -0.1812 \text{ A}$$


$$I_{10} = 0.1812 \text{ A} (-i_1)$$

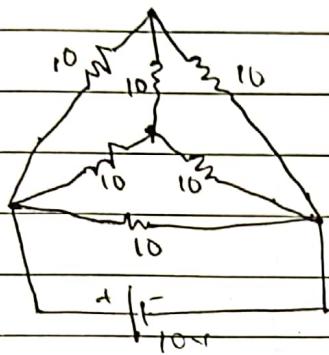6) Find the current supplied by the 10V battery using star delta transformation.



$\Rightarrow$  Sol.

The circuit can be redrawn as:

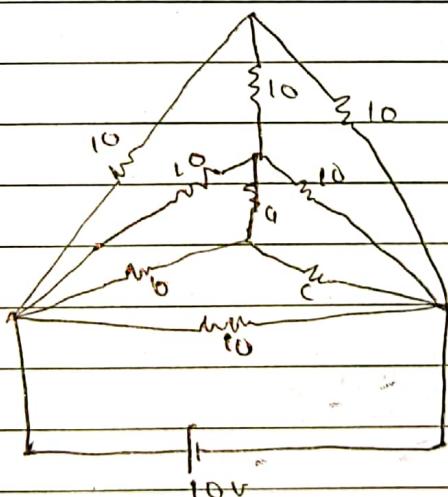

Using star delta transformation.

$$a = \frac{10 \times 10}{10 + 10 + 10}$$


$$= \frac{10}{3}$$

My,

$$b = \frac{10}{3}$$

$$c = \frac{10}{3}$$

Redrawing the Ckt

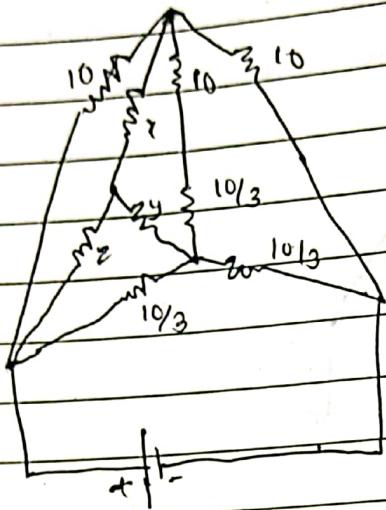

Again, using star-delta transformation.

$$y = \frac{(10+10)}{3} \times \frac{10}{3}$$

$$(10+10) + 10 + 10$$

$$= \frac{5}{3} \Omega$$


$$x = 10 \times \frac{(10+\frac{10}{3})}{\frac{10}{3} + (\frac{10}{3}) + 10} = 5 \Omega$$

$$z = \frac{10}{3} \times 10$$

$$\approx \frac{10 + 10}{3} + \frac{10}{2} + 10$$

$$= 5\frac{1}{4} \Omega$$

Redrawing okt.

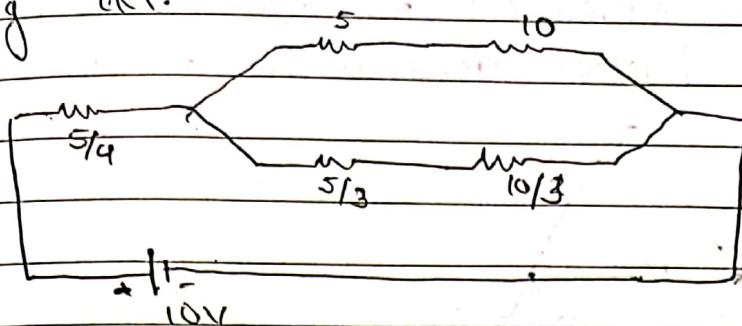

$$R_{eq} = \frac{5}{4} + \left[ (5+10) // \left( \frac{5}{3} + \frac{10}{3} \right) \right]$$


$$= \frac{5}{4} + [15 // 5]$$

$$= \frac{5}{4} + \frac{15}{4}$$

$$= 5$$


$$\text{Current } (I) = \frac{10}{5} = 2 \text{ A.}$$

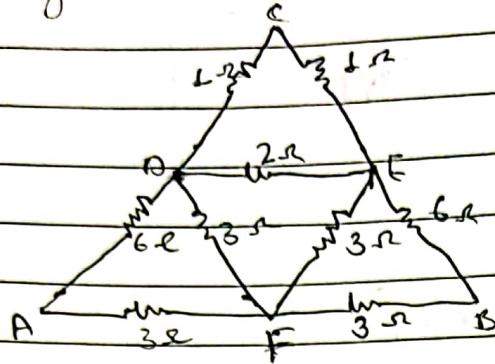7) Calculate the equivalent resistance b/w points A & B by star / delta transformation in the circuit below.



$\Rightarrow$  Sol.

Redrawing Ckt

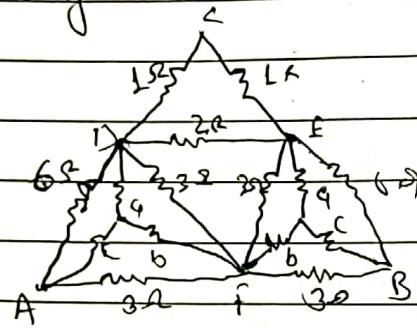


using star - delta transformation.

$$a = \frac{6 \times 3}{6+3+3} = \frac{3}{2} \text{ ohm}$$

$$c = \frac{6 \times 3}{6+3+3} = \frac{3}{2} \text{ ohm}$$


$$b = \frac{3 \times 3}{6+3+3} = \frac{3}{4} \text{ ohm}$$

Redrawing Ckt

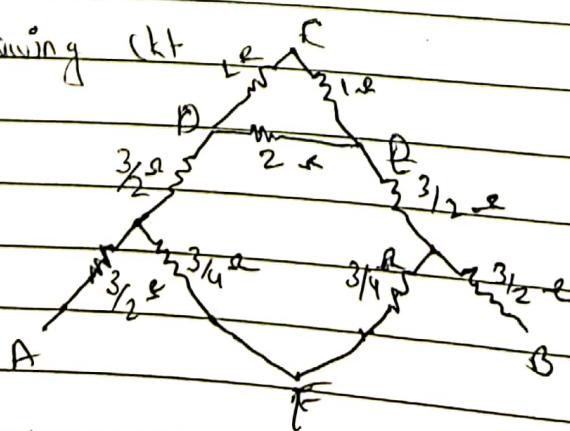


$$\begin{aligned}
 R_{eq} &= \left\{ \left[ \left( 1+1 \right) \parallel 2 \right] + \frac{3}{2} + \frac{3}{2} \right\} \parallel \left\{ \left( \frac{3}{2} + \frac{3}{2} \right) \parallel \frac{3}{2} \right\} + \frac{3}{2} + \frac{3}{2} \\
 &= \left\{ [2 \parallel 2] + 3 \parallel \frac{3}{2} \right\} + 3 \\
 &= \left\{ \frac{2 \times 2}{2+2} + 3 \parallel \frac{3}{2} \right\} + 3 \\
 &= \left\{ 4 \parallel \frac{3}{2} \right\} + 3 \\
 &= \frac{4 \times \frac{3}{2}}{4 + \frac{3}{2}} + 3 \\
 &= 4.09 \Omega
 \end{aligned}$$

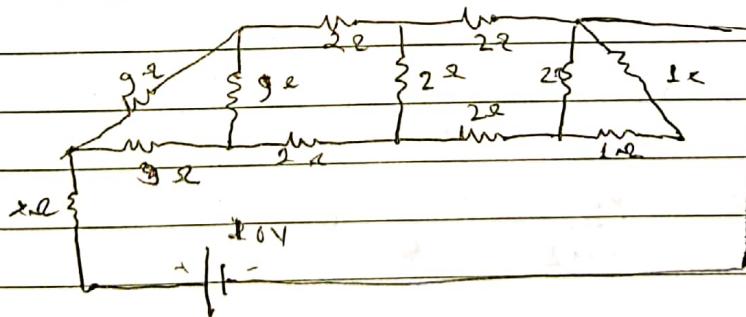8) Determine the equivalent resistance betn the terminal af b & the current supplied by the battery for the network shown in fig. 8.



$\Rightarrow$  Soln.


Redrawing the AB portion.

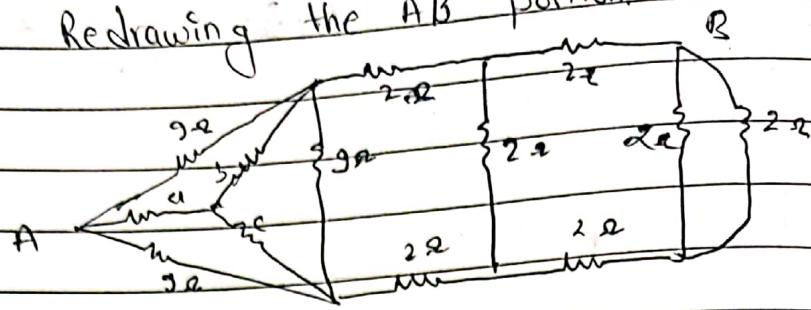

Using star - delta.

$$a = b = c = \frac{9 \times 9}{9+9+9} = 3\Omega$$

Redrawing ckt of AB

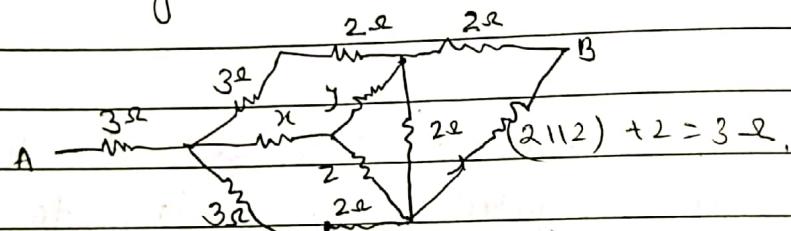


Using star - delta.

$$x = \frac{5 \times 5}{5+5+2} = \frac{25}{12} \Omega$$

$$y = 2 = \frac{2 \times 5}{5+5+2} = \frac{5}{6} \Omega$$

Redrawing ckt of AB.

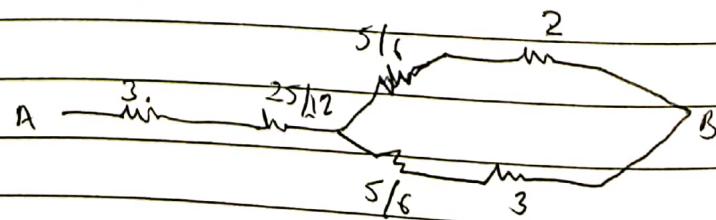

$$R_{eq} = 3 + \frac{25}{12} + \left[ \left( \frac{5}{6} + 2 \right) \parallel \left( \frac{5}{6} - 3 \right) \right]$$

$$= 3 + \frac{25}{12} + \left[ \frac{17}{6} \parallel \frac{23}{6} \right]$$

$$= 3 + \frac{25}{12} + \frac{391}{240}$$

$$= \frac{537}{80}$$

$$= 6.7125 \Omega$$

$$\text{For open (1) } (k) = 2\Omega + 6.7125 \Omega \\ = 8.7125 \Omega$$

$$\text{current } (I) = \frac{V}{R_T} = \frac{10}{8.7125} \\ = 1.1477 A$$