
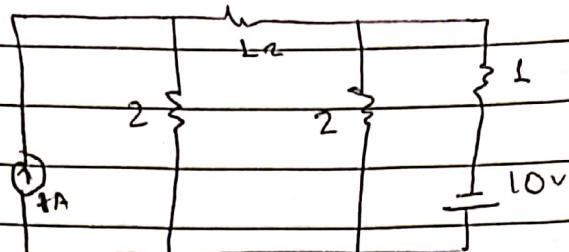


Tutorial - 2.

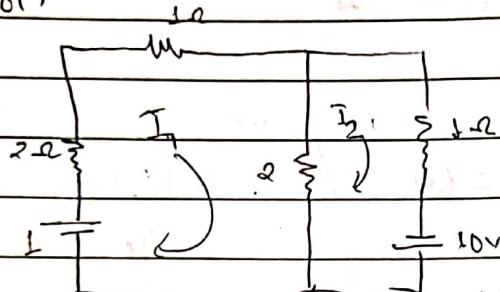- ii) Using mesh analysis, obtain the current through the 10V battery for the circuit shown in fig.



\Rightarrow Sol^r.



In mesh I

$$2I_1 + 5 + 2(I_1 - I_2) = 2$$

$$3I_1 + 2I_2 - 2I_2 = 2$$

$$5I_1 - 2I_2 = 2 \quad (i)$$

In mesh II

$$I_2 + 2(I_2 - I_1) = 10$$

$$3I_2 - 2I_1 = 10 \quad (ii)$$


Solving (i) & (ii)

$$I_1 = 2.36A$$

$$I_2 = 4.9A$$

current through 10V battery is 4.9A

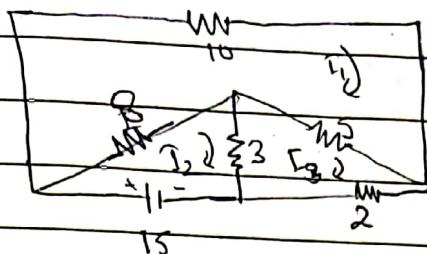2) What is the power loss in the 10Ω resistor in the network shown. Use mesh method.



In mesh I

$$10I_1 + 5(I_2 - I_3) + 8(I_1 - I_2) = 0$$

$$10I_1 + 5I_1 - 5I_3 + 8I_1 - 8I_2 = 0$$

$$23I_1 - 5I_3 - 8I_2 = 0 \quad (i)$$

In mesh II

$$8(I_2 - I_1) + 3(I_2 - I_3) = 15$$

$$8I_2 - 8I_1 + 3I_2 - 3I_3 = 15$$

$$-8I_1 + 11I_2 - 3I_3 = 15 \quad (ii)$$

In mesh III

$$5(I_3 - I_1) + 2I_3 + 3(I_3 - I_2) = 0$$

$$5I_3 - 5I_1 + 2I_3 + 3(I_3 - 3I_2) = 0$$

$$-5I_1 - 3I_2 + 10I_3 = 0 \quad (iii)$$

Solving eqn (i), (ii) & (iii) we get

$$I_1 = 1.23 \text{ A}$$

$$I_2 = 2.63 \text{ A}$$


$$I_3 = 1.89 \text{ A}$$

Power loss in 10Ω is $I_1^2 \times R$

$$= 1.23^2 \times 10$$

$$= 15.129 \text{ W}$$

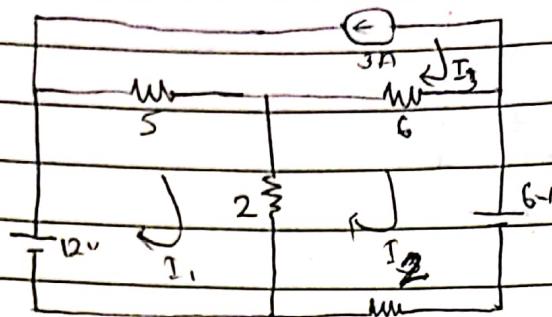3) Determine the current through resistor using mesh method.



$\Rightarrow \text{so}$

$$I_3 = -3A$$

In mesh I

$$5(I_1 - I_3) + 2(I_1 - I_2) = 12$$

$$5I_1 + 15A + 2I_1 - 2I_2 = 12$$

$$7I_1 - 2I_2 = -3 \quad (\text{eqn } i)$$

In mesh II

$$2(I_2 - I_1) + I_2 + 6(I_2 - I_3) = -6$$

$$2I_2 - 2I_1 + I_2 + 6I_2 + 18 = -6$$

$$-2I_1 + 9I_2 = -2A \quad (\text{eqn } ii)$$

Now eqn (i) & (ii) we get.

$$I_1 = -5.27A$$

$$I_2 = -2.91A$$

$$I_3 = -3A$$


$$\text{current through } 5\Omega = I_1 - I_3 = -1.27 + 3 \\ = 1.73A$$

$$\text{current through } 2\Omega = I_1 - I_2 = -1.27 + 2.915 \\ = 1.68A$$

$$\text{current through } 6\Omega = I_2 - I_3 = -2.95 + 3 \\ = 0.05A$$

$$\text{current through } 3\Omega = I_2 = -2.95A \\ = 2.95A (B \rightarrow A)$$

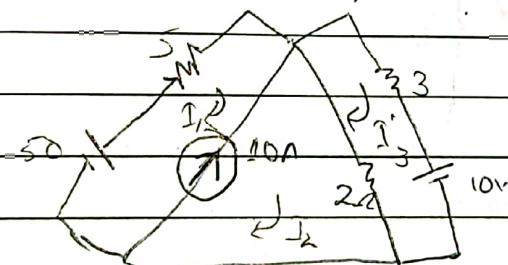4) Using mesh analysis find current flowing through 5Ω source



$$I_2 - I_1 = 10 \\ -I_1 + I_2 = 10 - i$$

Applying KVL in super mesh

$$5I_1 + 2(I_2 - I_3) = 50$$

$$5I_1 + 2I_2 - 2I_3 = 50 \quad \text{(i)}$$

In mesh III

$$3I_3 + 2(I_3 - I_2) = -10$$

$$3I_3 + 2I_3 - 2I_2 = -10$$

$$-2I_2 + 5I_3 = -10 \quad \text{(iii)}$$

Solving


$$I_1 = 5.48$$

$$I_2 = 15.48$$

$$I_3 = 4.19$$

current through 5Ω is 5.48 A .

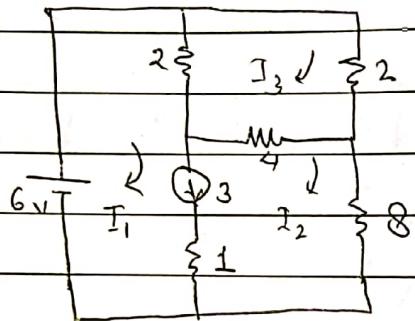(8) Use mesh analysis to determine i_1, i_2, i_3 in fig



\Rightarrow soln,

$$I_1 - I_2 = 3 \quad (i)$$

Applying KVL on super mesh

$$2(I_1 - I_3) + 4(I_2 - I_3) + 8I_2 = 6$$

$$2I_1 - 2I_3 + 4I_2 - 4I_3 + 8I_2 = 6$$

$$2I_1 + 12I_2 - 6I_3 = 6 \quad (ii)$$

In mesh III

$$2I_3 + 4(I_3 - I_2) + 2(I_3 - I_1) = 6$$

$$2I_3 + 4I_3 - 4I_2 + 2I_3 - 2I_1 = 6$$

$$-2I_1 - 4I_2 + 9I_3 = 0 \quad (iii)$$


Solving the eqn. we get

$$I_1 = 3.4 A$$

$$I_2 = 0.4 A$$

$$I_3 = 0.93 A$$

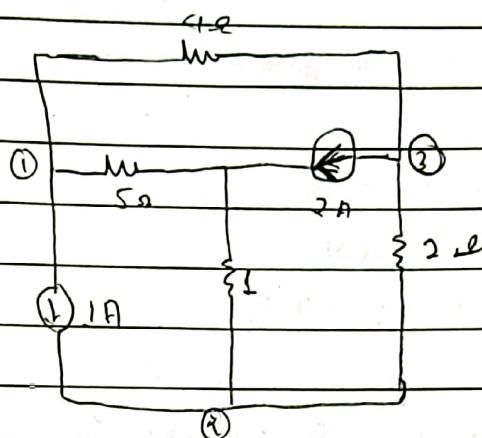Q) Find the current & voltage drops through 5Ω resistor



\Rightarrow Sol.

Applying KVL on note (i)

$$-1 = \frac{V_1 - V_2}{6} + \frac{V_1 - V_3}{4}$$

$$\text{or } -1 = \left(\frac{1}{3} + \frac{1}{4} \right) V_1 - \frac{1}{5} V_2 - \frac{1}{4} V_3$$

$$-1 = 0.45 V_1 - \frac{1}{5} V_2 - \frac{1}{4} V_3$$

$$-1 = 0.45 V_1 - 0.2 V_2 - 0.25 V_3 \quad \text{--- (i)}$$

Applying KVL on note (ii)

$$2 = \frac{V_2 - V_1}{5} + \frac{V_2 - V_3}{1}$$

$$2 = \left(-\frac{1}{3} \right) V_1 + \left(\frac{1}{6} + 1 \right) V_2$$

$$2 = -0.2 V_1 + 1.2 V_2 \quad \text{--- (ii)}$$

Applying KVL on node 1 (iii)

$$\frac{V_4 - V_3}{2} = 2 + \frac{V_3 - V_1}{4}$$

$$\frac{0 - V_3}{2} = 2 + \frac{-V_2}{4} - \frac{V_1}{4}$$

$$-2 = -\frac{V_1}{4} + \left(\frac{1}{2} + \frac{1}{4}\right)V_3$$

$$-2 = -0.25V_1 + 0.75V_3 \quad (\text{iii})$$

Solving ii, iii & iv


$$V_1 = -4V$$

$$V_2 = 3V$$

$$V_3 = -4V$$

$$\text{Current through } 5\Omega \text{ resistor} = \frac{V_2 - V_1}{5} = \frac{1 - (-4)}{5} = 1A$$

$$\begin{aligned} \text{Voltage drop through } 5 \text{ resistor} &= V_2 - V_1 \\ &= 1 - (-4) \\ &= 5V. \end{aligned}$$

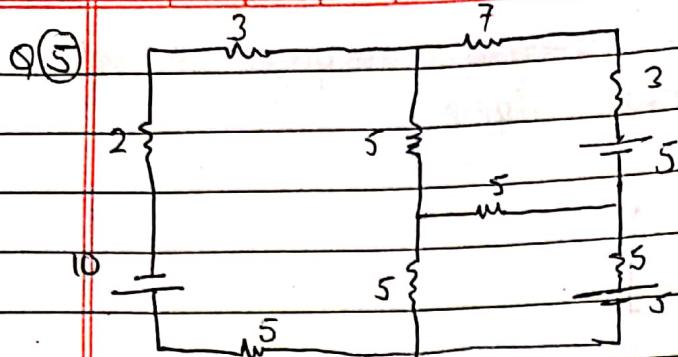 $\Rightarrow \text{JOL}$,

Mesh I

$$-10 + 2I_1 + 3I_2 + 5(I_1 - I_2) + 5(I_1 - I_3) + 5I_1 = 0$$

$$\therefore 2I_1 + 3I_2 + 5I_1 - 5I_2 + 5I_1 - 5I_3 + 5I_1 = 10$$

$$\therefore 20I_1 - 5I_2 - 5I_3 = 10 \quad \text{--- (1)}$$

Mesh II

$$-5 + 5I_2 - 5I_3 + 5I_2 - 5I_1 + 7I_2 + 3I_2 - 5I_3 - 5I_1 = 0$$

$$\therefore 5I_2 + 5I_2 + 7I_2 + 3I_2 - 5I_3 - 5I_1 = 5$$

$$\therefore -5I_1 + 20I_2 - 5I_3 = 5 \quad \text{--- (2)}$$

Mesh III

$$-5 + 5I_3 - 5I_1 + 5I_3 - 5I_2 + 5I_1 = 0$$

$$5I_3 + 5I_3 + 5I_3 - 5I_1 - 5I_2 = 0$$

$$-5I_1 - 5I_2 + 15I_3 = 0 \quad \text{--- (3)}$$

Solving (1), (2) & (3)

$$I_1 = 0.88 \text{ A}$$

$$I_2 = 0.68 \text{ A}$$

$$I_3 = 0.85 \text{ A}$$


$$P_{10} = I_1 V = 8.8 \text{ W}$$

$$P_5 = I_2 V = 3.4 \text{ W}$$

$$P_3 = I_3 V = 4.15 \text{ W}$$

Q. Determine the current in 10Ω by applying Maxwell's loop-current method in given figure.

\Rightarrow Sol:

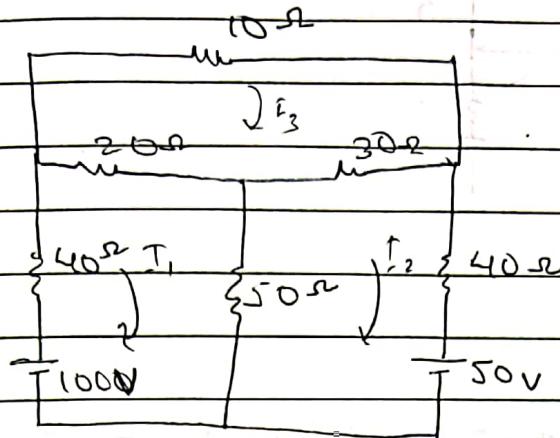

In mesh (I)

$$100 - 40I_1 - 20[I_1 - I_3] - 50(I_1 - I_2) = 0$$

$$100 - 40I_1 - 20I_1 + 20I_3 - 50I_1 + 50I_2 = 0$$

$$100 - 110I_1 + 20I_3 + 50I_2 = 0 \quad (i)$$

In mesh (II)

$$-I_2 - (I_2 - I_3) 30 - 20(I_2 - I_1) = 0$$

$$-10I_2 - 30I_2 + 30I_3 - 20I_2 + 20I_1 = 0$$

$$20I_1 - 80I_2 + 30I_3 = 0 \quad (ii)$$

In mesh (III)

$$-50 - 50(I_2 - I_1) - 30(I_3 - I_1) - 40I_2 = 0$$

$$-50 - 50I_2 + 50I_1 - 30I_2 + 30I_1 - 40I_2 = 0 \quad (iii)$$

$$80I_1 - 120I_2$$



Solving (i), (ii) & (iii) we get

$$I_1 = 1.034 \text{ A}$$

$$I_2 = 0.1150 \text{ A}$$

$$I_3 = 0.4023 \text{ A}$$

Current through 10Ω = $I_3 = 0.4025 \text{ Amp}$

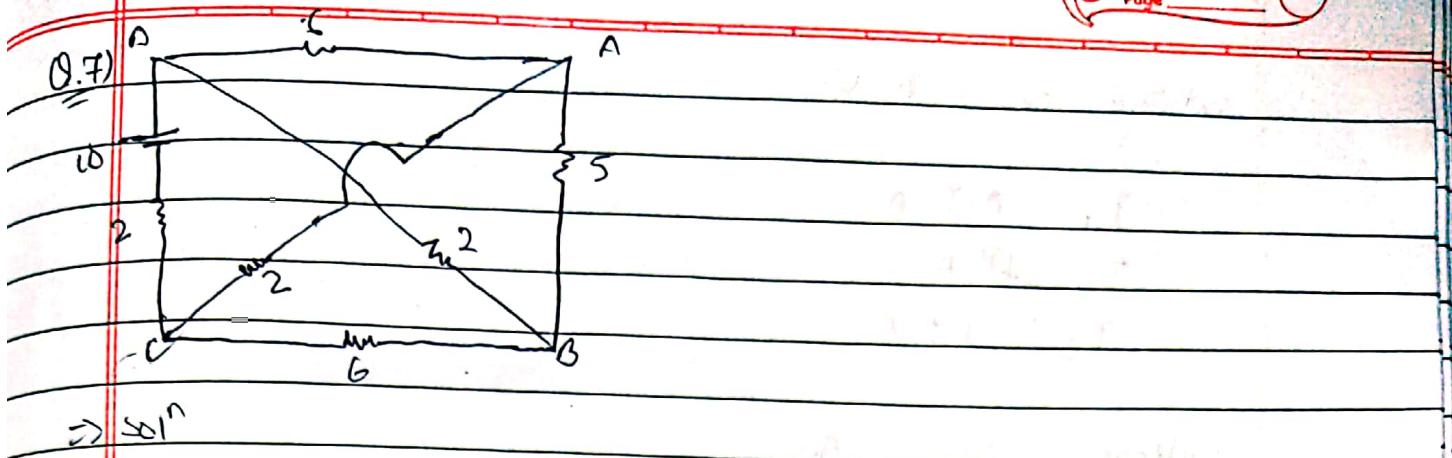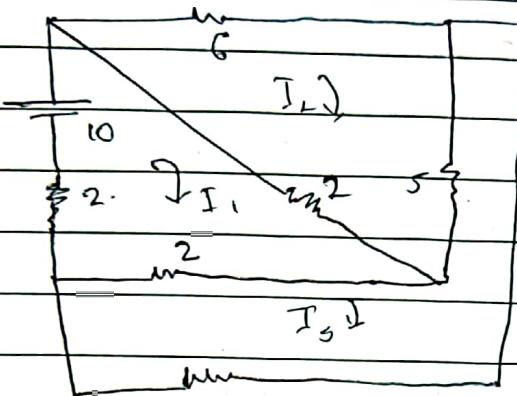 $\Rightarrow \text{Soln}$ 

Mesh I

$$-6I_1 - 5(I_1 - I_2) - 2(I_1 - I_2) = 0$$

$$-6I_1 - 5I_1 + 5I_3 - 2I_1 + 2I_2 = 0$$

$$-13I_1 + 2I_2 + 5I_3 = 0 \quad \rightarrow \text{i})$$

Mesh II

$$10 - 2(I_2 - I_1) - 6(I_2 - I_3) - 2I_2 = 0$$

$$10 - 2I_2 + 2I_1 - 6I_2 + 6I_3 - 2I_2 = 0$$

$$10 - 10I_2 + 2I_1 + 6I_3 = 0$$

$$2I_1 - 10I_2 + 6I_3 = -10 \quad \rightarrow \text{ii})$$

Mesh III

$$-2I_3 - 6(I_3 - I_2) - 5(I_3 - I_1) = 0$$

$$-2I_3 - 6I_3 + 6I_2 - 5I_3 + 5I_1 = 0$$

$$-13I_3 + 6I_2 + 5I_1 = 0$$

$$5I_1 + 6I_2 - 13I_3 = 0 \quad \rightarrow \text{iii})$$

Solving eqn (i) & (ii)

$$I_1 = 0.7 \text{ A}$$

$$I_2 = 1.8 \text{ A}$$

$$I_3 = 1.1 \text{ A}$$

Voltage across AB

$$\text{current} = I_2 - I_3 \\ = 0.4 \text{ Amp}$$


$$V = IR$$


$$= 0.4 \times 2 = 0.8.$$

$$= 2V$$

Since the direction of current is clockwise

polarity

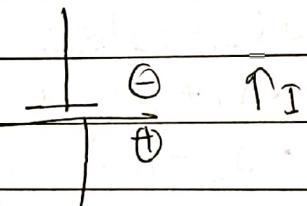

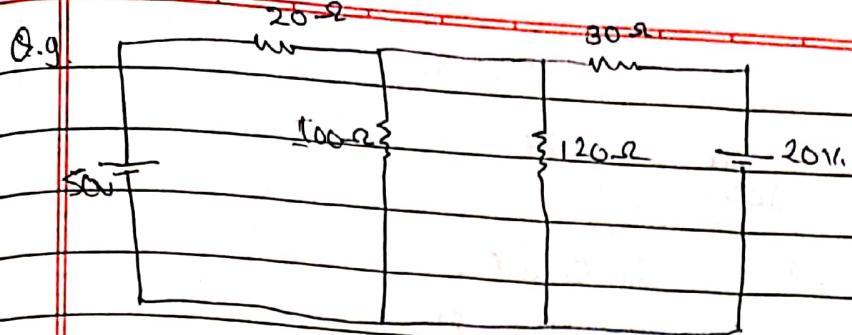



The voltage source is transformable to current source

$$V = IR$$

$$I = \frac{V}{R}$$

$$5\text{V} \text{ vs} \rightarrow 2.5 \text{ Amp (S.)}$$
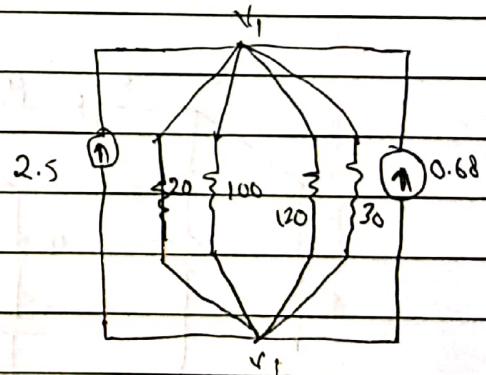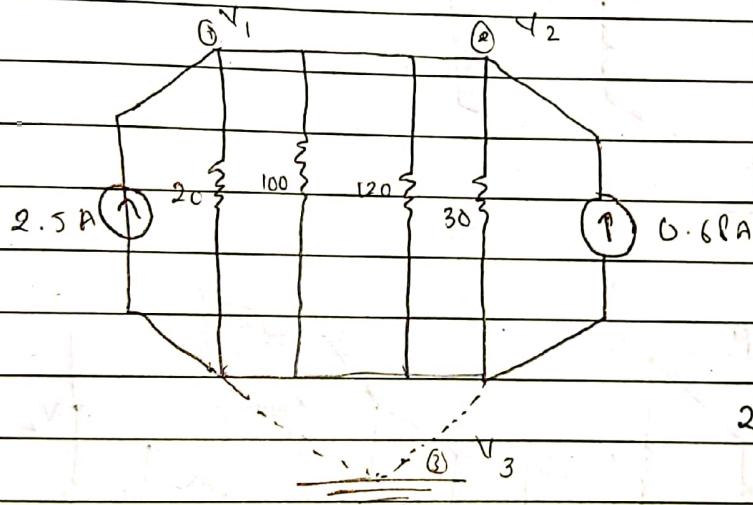
$$20\text{V} \text{ vs} \rightarrow 0.68 \text{ Amp (S.)}$$



At node (3)

$$\sum I_{(\text{entering})} = \sum I_{(\text{outgoing})}$$

$$2.5 + 0.68 = \left(\frac{V_1 - V_2}{20} \right) + \left(\frac{V_1 - V_2}{100} \right) + \left(\frac{V_1 - V_2}{120} \right) + \left(\frac{V_1 - V_2}{30} \right)$$

$$V_2 = 0$$

$$\therefore 3.18 = \left(\frac{1}{20} + \frac{1}{100} + \frac{1}{120} + \frac{1}{30} \right) V_1$$

$$V_1 = 3.18 \times \frac{600}{61}$$

$$V_1 = 31.27 \text{ V}$$



Current through 100Ω resistor


$$I = \frac{V_1 - V_2}{100} = \frac{3.37}{100}$$

$$= 0.31 \text{ Amp}$$

i.e. 3.11 m Ω mp

Q(1)

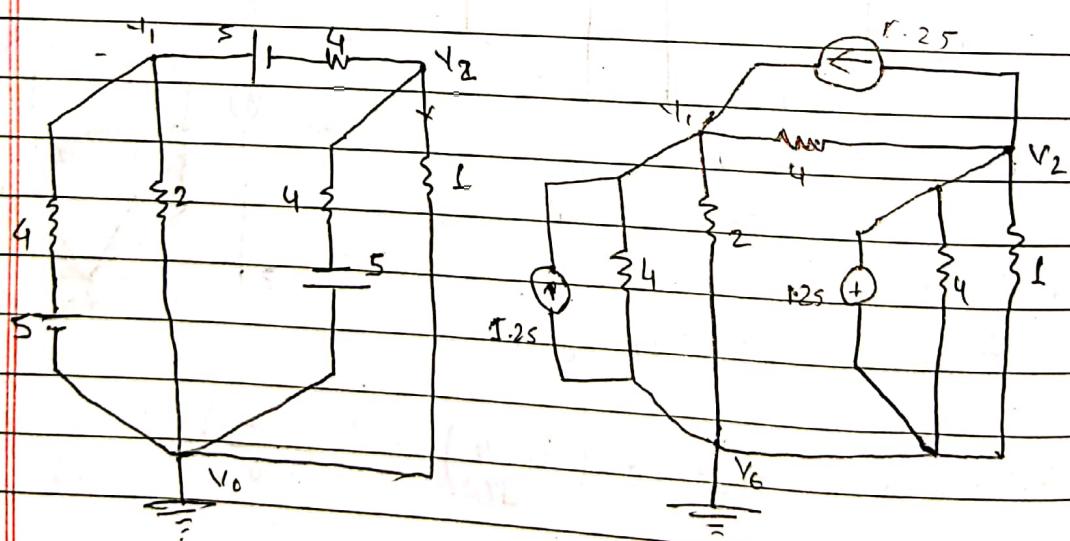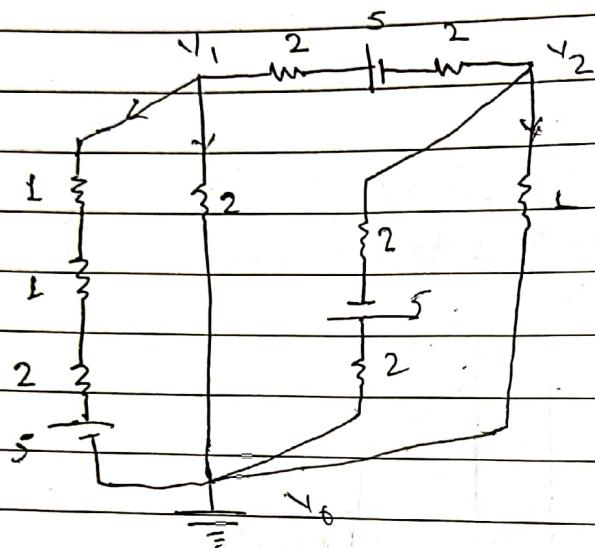

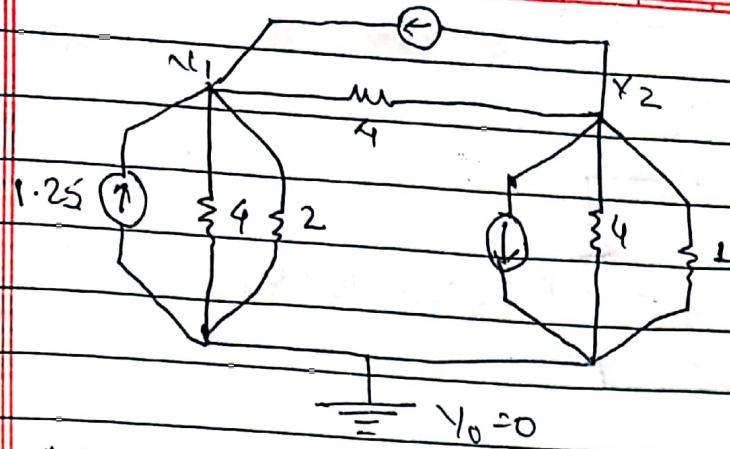At V_1 ,

$$\sum I_{\text{(incoming)}} = \sum I_{\text{(outgoing)}}$$

$$1.25 + 1.25 = \left(\frac{V_1 - V_2}{1}\right) + \left(\frac{V_1 - V_0}{1/4}\right) + \left(\frac{V_1 - V_0}{1/2}\right)$$

$$2.5 = \frac{1}{4}V_1 - \frac{1}{4}V_2 + \frac{1}{4}V_1 + \frac{1}{2}V_1$$

$$2.5 = V_1 - \frac{1}{4}V_2$$

$$\text{i.e. } V_1 - 0.25V_2 = 2.5 \rightarrow$$

At V_2 ,

$$\sum I_{\text{(incoming)}} = \sum I_{\text{(outgoing)}}$$

$$0 = 1.25 + 1.25 + \frac{V_2 - V_1}{1} + \frac{V_2 - V_0}{1/4} + \frac{V_2 - V_0}{1/2}$$

$$-2.5 = \frac{1}{4}V_2 - \frac{1}{2}V_1 + V_2 + \frac{1}{4}V_2$$

$$-2.5 = -0.25V_1 + 1.5V_2 \quad \text{From } 5V$$

$$V_1 = 2.12$$

$$V_2 = -1.30$$

$$\uparrow = \frac{V_2}{4} + 1.25 = 0.925 A$$

From another 5V

$$I = \frac{V_1 - V_2 - 1.25}{1} = 0.8675 - 1.25$$

$$= 0.3825 \text{ Amp.}$$

Current flowing

$$\text{From } 5V. \quad I = \frac{V_1}{A} = 1.25$$

$$= 0.7075 \text{ Amp.}$$