

Q.1) A 10kVA, 200/400V, 50Hz, 1-phase, transformer gave the following results:

OC tests (H.V open): 200V 1.3A 120W

SC test (L.V short): 22V 30A 200W

Determine Shunt and series branch parameters referred to Low voltage side and hence draw equivalent circuit diagram also

⇒ Soln -

we have given,

$$S = 10 \text{ kVA}$$

$$V_1 = 200 \text{ V} \quad V_2 = 400 \text{ V} \quad K = \frac{V_2}{V_1} = \frac{400}{200} = 2$$

From OC test, we have (referred to L.V side)

$$V_1 = 200 \text{ V} \quad I_0 = 1.3 \text{ A} \quad W_0 = 120 \text{ W}$$

$$W_0 = V_1 I_0 \cos \phi_0$$

$$\cos \phi_0 = \frac{W_0}{V_1 I_0} = \frac{120}{200 \times 1.3} = 0.461$$

$$R_0 = \frac{V_1}{I_0 \cos \phi_0} = \frac{200}{1.3 \times 0.461} = 333.72 \Omega$$

$$X_0 = \frac{V_1}{I_0 \sin \phi_0} = \frac{200}{1.3 \times \sqrt{1 - (0.461)^2}} = 173.36 \Omega$$

From short test, we have (referred to H.V side)

$$V_{SC} = 22 \text{ V} \quad I_{SC} = 30 \text{ A} \quad W_{SC} = 200 \text{ W}$$

$$Z_{02} = \frac{V_{SC}}{I_{SC}} = \frac{22}{30} = 0.733 \Omega$$

$$R_{02} = \frac{W_{SC}}{I_{SC}^2} = \frac{200}{30^2} = 0.22 \Omega$$

$$X_{02} = \sqrt{Z_{02}^2 - R_{02}^2} = \sqrt{0.733^2 - 0.22^2} = 0.699 \Omega$$

Equivalent resistance and reactance (R_{02} and X_{02}) referred to L.V side,

$$R_{01} = \frac{R_{02}}{K^2} = \frac{0.22}{2^2} = 0.055 \Omega$$

$$X_{01} = \frac{X_{02}}{K^2} = \frac{0.699}{2^2} = 0.174 \Omega$$

The equivalent circuit diagram referred to LV side is,

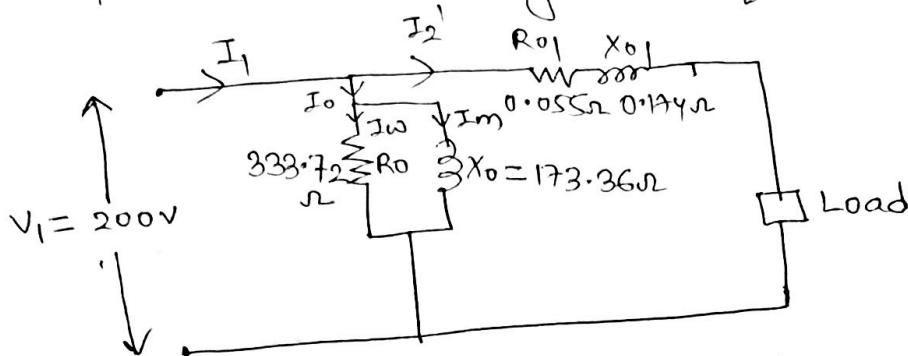


Fig. eq. ckt diagram referred to LV side

Q.2) The following test results were obtained on a 20kVA, 2200/220V, 50Hz single phase transformer:

Open ckt test (LV side): 220V 1.1A 125W

Short ckt test (HV side): 52.7V 8.4A 287W

Calculate the equivalent ckt referred to LV side and draw the equivalent ckt.

⇒ Soln -

we have given,

$$S = 20 \text{ kVA}$$

$$V_1 = 2200 \text{ V}$$

$$V_2 = 220 \text{ V}$$

From open ckt test, (referred to LV side)

$$V_2 = 220 \text{ V} \quad I_0 = 1.1 \text{ A} \quad W_0 = 125 \text{ W}$$

$$W_0 = V_2 I_0 \cos \phi_0$$

$$\cos \phi_0 = \frac{125}{220 \times 1.1} = 0.516$$

$$R_0' = \frac{V_2}{I_0 \cos \phi_0} = \frac{220}{1.1 \times 0.516} = 387.59 \Omega$$

$$X_0' = \frac{V_2}{I_0 \sin \phi_0} = \frac{220}{1.1 \times \sqrt{1 - 0.516^2}} = 233.48 \Omega$$

From short ckt test, (referred to H.V side)

$$V_{SC} = 52.7V \quad I_{SC} = 8.4A \quad W_{SC} = 287W$$

$$R_{01} = \frac{W_{SC}}{I_{SC}^2} = \frac{287}{8.4^2} = 4.067$$

$$Z_{01} = \frac{V_{SC}}{I_{SC}} = \frac{52.7}{8.4} = 6.27 \Omega$$

$$X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = \sqrt{6.27^2 - 4.067^2} = 4.77 \Omega$$

Equivalent series resistance and reactance (R_{01} and X_{01}) referred to L.V side. (Secondary side)

$$R_{02} = K^2 R_{01} = \left(\frac{220}{2200}\right)^2 \times 4.067 = 0.04067 \Omega$$

$$X_{02} = K^2 X_{01} = (0.1)^2 \times 4.77 = 0.0477 \Omega$$

The equivalent ckt diagram referred to L.V side,


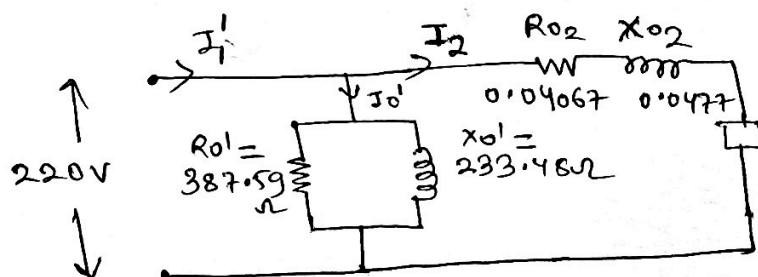


Fig Equivalent ckt diagram referred to L.V side

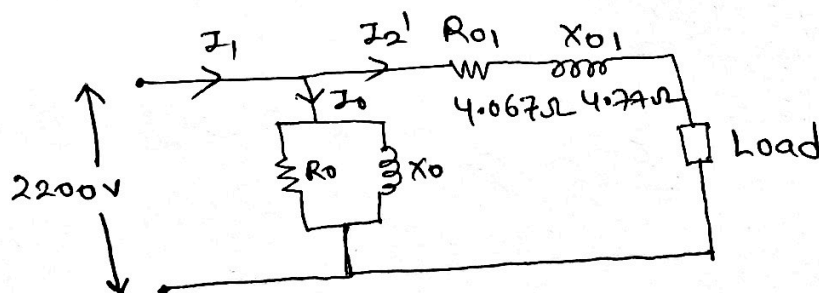

Equivalent ckt diagram referred to H.V side

$$R_0 = \frac{R_{01}}{K^2} = \frac{387.59}{(0.1)^2}$$

$$X_0 = \frac{X_{01}}{K^2} = \frac{233.48}{(0.1)^2}$$