

## Assignment-01

Q1 Assume that your group has decided to make microprocessor based instrumentation system for Ice cream factory using an 8255 PPI card at base address 5000H in memory mapped I/O mode for controlling purpose. You need to measure pressure and temperature of a manufacturing plant.

- i) List out the collected documents and components.
- ii) List out different signals you need to derive and how can be directly connected to your interfacing circuit.
- iii) Draw minimum mapping circuit for above system.
- iv) What are the addresses captured by your card? Generate the control word for the system.
- v) WAP module for measuring temperature and control if the temperature is not in the range. Assume suitable data if necessary.

### SOLN


- i) Components:
  - a) 8255 card.
  - b) ADC
  - c) MUX
  - d) Memory
  - e) Processor
- f) connecting wires.
- g) power supplies
- h) gates
- etc.

Documents: Datasheet, technical and specification documents of above mentioned components.

ii. Signals needed to be derived are:

- A<sub>0</sub>, A<sub>1</sub>
- Chip select ( $\overline{CS}$ )
- Read ( $\overline{RD}$ )
- Write ( $\overline{WR}$ )
- Reset (reset out)
- Start of conversion (SOC)
- End of conversion (EOC)
- Data lines (D<sub>0</sub>-D<sub>7</sub>)
- Address lines (A<sub>2</sub>-A<sub>15</sub>)

iii. Minimum mapping circuits:

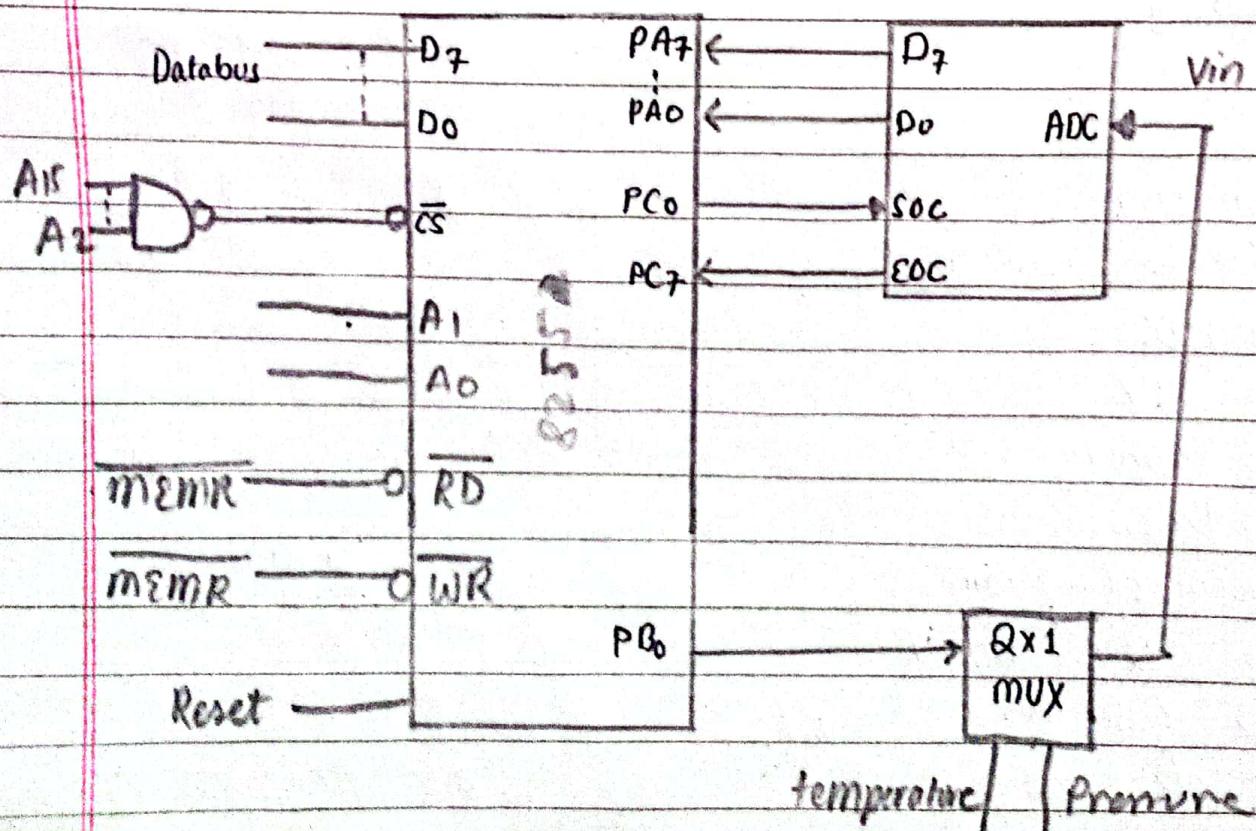

iv) Address captured by the card:

Port A = 5000H ( $A_1 = 0, A_0 = 0$ )

Port B = 5001H ( $A_1 = 0, A_0 = 1$ )

Port C = 5002H ( $A_1 = 1, A_0 = 0$ )

Control Register = 5003H ( $A_1 = 1, A_0 = 1$ )

Control Word

1	0	01	L	0	00	= 98H
PC7				PC0		

v. Program module:

LXI H, Memory

MVI A, 98H ; control word on

STA 5003H ; control register

MVI B, 00H ; selection pin for MUX

MOV A, B

STA 5001H ; select temp. from MUX

MVI A, 01H ; BSR word to set PC0

STA 5003H ; readable for C

Read : LDA 5002H ; read port C for EOC

RLC

JNC READ

LDA 5000H ; read temp. at port A

MOV M, A

CPI MAX-VAL

JNC CONTROL

CPI MIN-VAL

## JG CONTROL


INX H  
RET

Q.2. A/D converter requires signal to start the conversion and indicates the completion of operation with the end of conversion signal. 8255 PPI is interfaced with 8085 microprocessor at 80H. Microprocessor reads 8 bit output data of the ADC at port A and displays the same data to eight LED's connected to port B of 8255A. State any assumptions made.

- a. Identify the address captured by the card.
- b. Determine the necessary control word.
- c. Draw the schematic interfacing circuit.
- d. WAP to perform the operation.

P.T.O

Ans:

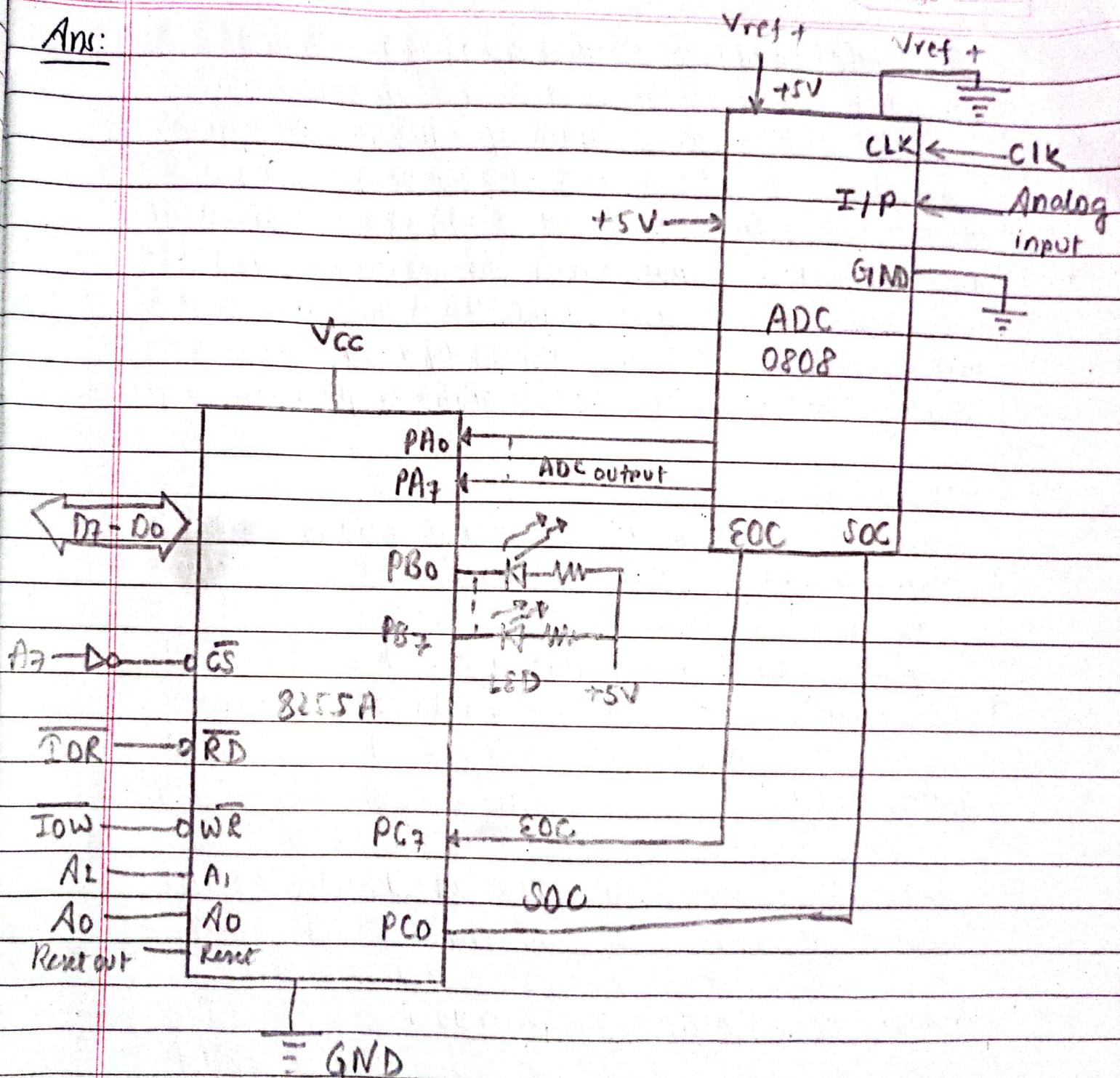

Above figure shows that the interfacing connections of ADC 0808 with 8085 using 8255. The analog input is used and a clock input of suitable frequency is available for ADC. Port C lower acts as the output port to send SOC (start of the conversion) to ADC and port C upper acts as the input port to receive the digital data output from the ADC while port TS acts as an 8 bit output data port to display the received data using eight LEDs.

Port addresses:

Circuit is I/O mapped I/O using A<sub>7</sub> high

Port A = 80H (A<sub>1</sub>=0, A<sub>0</sub>=0)

Port B = 81H (A<sub>1</sub>=0, A<sub>0</sub>=1)

Port C = 82H (A<sub>1</sub>=1, A<sub>0</sub>=0)

Control register = 83H (A<sub>1</sub>=1, A<sub>0</sub>=1)

Control word:

D <sub>7</sub>	D <sub>6</sub>	D <sub>5</sub>	D <sub>4</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
1	0	0	1	1	0	0	0

 $= 98H$ 

Program to perform the operation

```
MVI A, 98H ; control word
OUT 83H ; control register
MVI A, 01H ; BSR word to set PC0 (SOC)
OUT 83H ; starts conversion
NEXT: IN 82H ; read port C to check EOC
```

RLC  
JZ NEXT

; check PC7

IN 80H ; read ADC data in port A  
OUT 81H ; display data in port B  
RET

Q.3. A microprocessor kit has an onboard 8255. Interface to the 8255 eight single-pole-double-throw (SPDT) switches numbered S0 to S7 and a seven segment common anode LED display. Draw the complete circuit setup. Define clearly the function of all ports. Write a program to initialize 8255, detect a switch closure, and display the value of the switch number on the LED display.

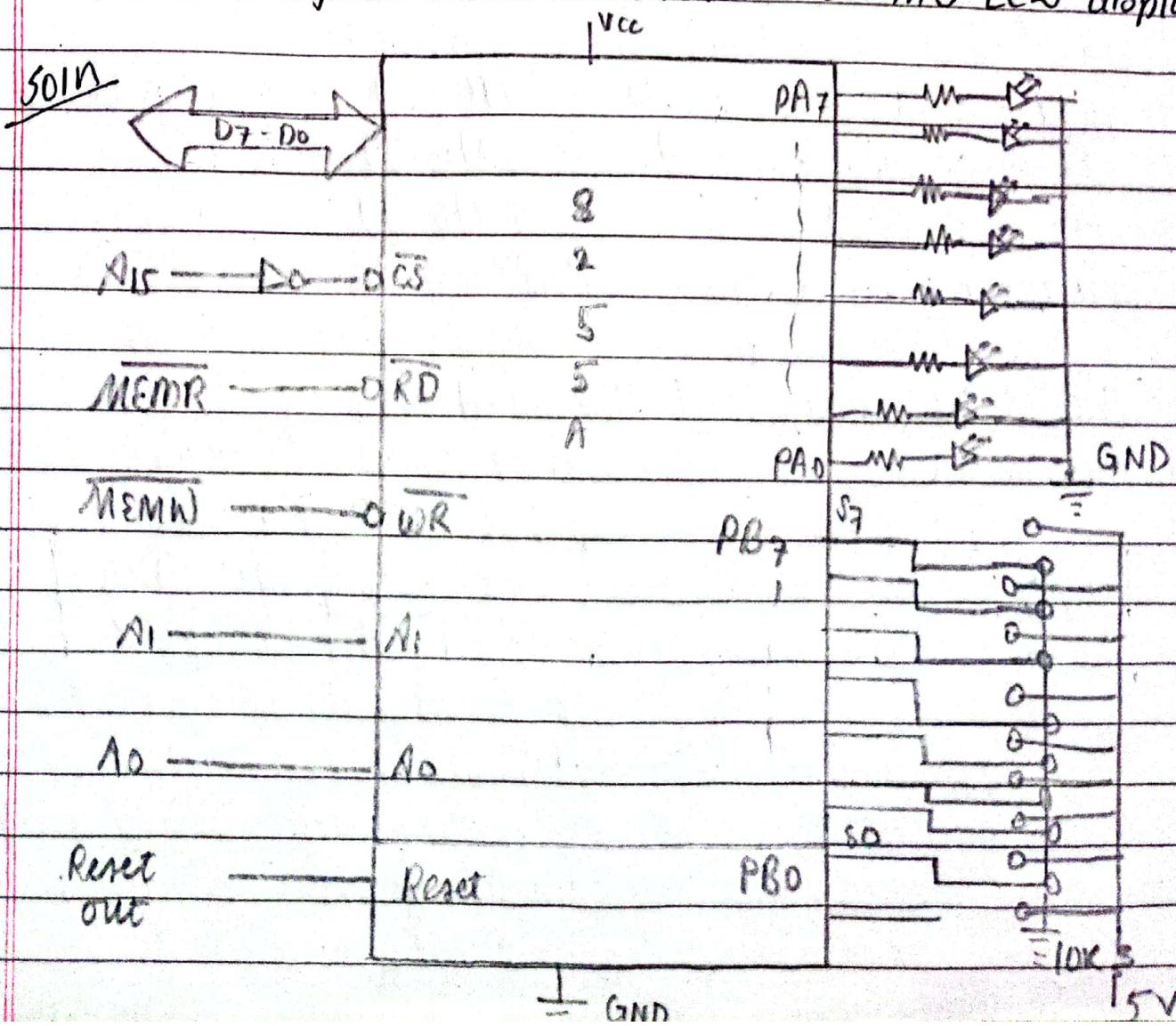


Fig: 8255 interfacing circuit with SPDT switch and seven segment common LED display

The interfacing circuit is drawn to interface an 8255A with single pole double throw (SPDT) switch and seven segment common LED display. Here port B is connected in mode 0 with SPDT switches numbered S<sub>6</sub> to S<sub>7</sub>, which are tied high through 10k resistor. Port A is connected in mode 0 with seven segment common LED display.

The 8255A connected as memory mapped I/O using A<sub>15</sub> high. The addresses of individual ports are selected as:

$$\text{port A} = 8000\text{H} \quad (A_1 = 0, A_0 = 0)$$

$$\text{port B} = 8001\text{H} \quad (A_1 = 0, A_0 = 1)$$

$$\text{port C} = 8002\text{H} \quad (A_1 = 1, A_0 = 0)$$

$$\text{Control register} = 8003\text{H} \quad (A_1 = 1, A_0 = 1)$$

The control word of the interfacing circuit will be:

D <sub>7</sub>	D <sub>6</sub>	D <sub>5</sub>	D <sub>4</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
1	0	0	0	X	0	1	X

$$= 82\text{H}$$

Below is the program subroutine to initialize 8255A to detect switch closure and display the switch number on LED display;

```
MVI A, 82H ; control word  
STA 8003H ; control register address  
CALL KCHECK ; check if a switch is pressed  
CALL KPUSH ; check the pushed switches  
CALL KNUM ; check the pressed switch number  
CALL DISP ; display switch number in 7-segment  
; LED display.  
RET
```

```
KCHECK: LDA 8001H ; read port B for SPDT switch  
CPI FFH ; check key is pressed or not  
JNZ KCHECK ; if not, wait in loop  
RET
```

```
KPUSH ; LDA 8001H ; read port B for SPDT switch  
CPI FFH ; check key is pressed or not  
JZ KPUSH ; if not, wait in loop  
CMA ; set 1 for key number  
; set 0 for other.  
RET
```

```
KNUM: MVI C, 0FH ; set code counter  
NEXT : DCR C ; adjust the code  
RAL ; place MSB in CY  
JNC NEXT ; if bit=0 go back to check next bit  
MOV A,C ; place key number in accumulator.  
RET
```

DISP: LX1H, HCODE ; define hexcode of number;  
; which are stored in  
; lookup table

ADD L

MOV L,A

MOV A,M

; read LED code to display  
; key number

STA 8000H

; display key number in 7  
; segment LED

RET

HCODE: DB40H, 79H, 24H, 30H, 19H, 12H, 02H, 78H  
; common anode seven segment codes for digits  
; from 0 to 7 are stored sequentially in  
; memory as table lookup

Q.4

~~Assume that~~

You have to interface ADC with 8085 using 8255A ports. Interface a fan and a heater using opto-couplers to drive the I/O devices. If the temperature is less than  $10^{\circ}\text{C}$ , turn on the heater and if the temperature is higher than  $35^{\circ}\text{C}$ , turn on the fan. Use port A of 8255 for transferring digital data output of ADC to the CPU and port C for control signals.

Assume that an analog input is present at second input of the multiplexer and a clock input of suitable frequency is available for ADC. Draw the circuit diagram of your design and write the subroutine.

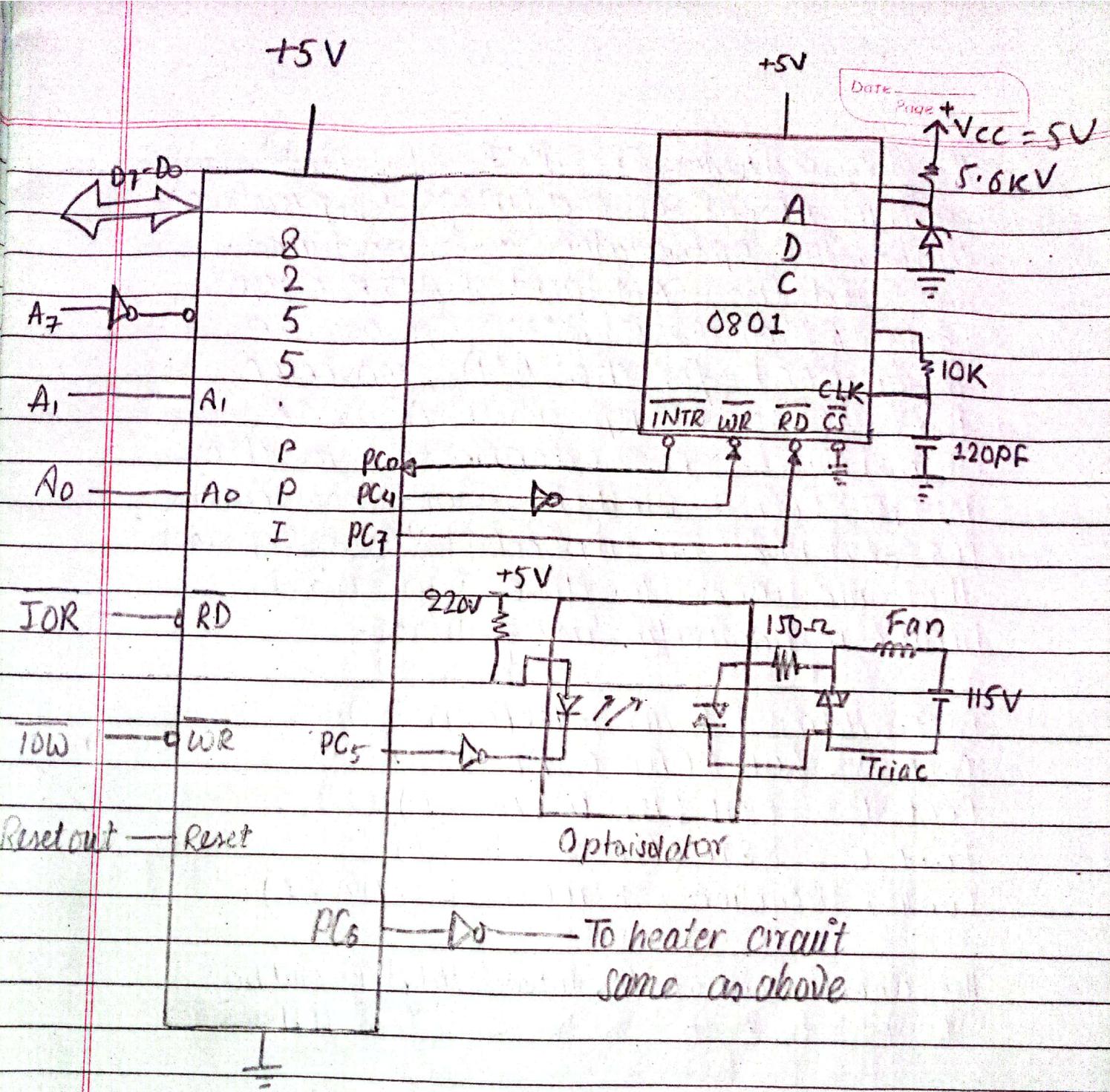


fig : circuit Diagram

This design includes 8255 PPI, 8 bit A/D converter ADC 0801 and LM135 temperature sensor. Two optoisolators and two triacs are used for FAN and HEATER circuits.

Port A of 8255 is set up as an input port for the A/D converter.

Port C is set up in BSR mode.

Signal lines PC0 is connected to the INTR, PC4 is used to start conversion, PC5 and PC6 are connected to optoisolators that are used to drive fan and heater respectively using triacs.

Port address of an interfacing circuits are

Port A = 80H ( $A_1=0, A_0=0$ )

Port B = 81H ( $A_1=0, A_0=1$ )

Port C = 82H ( $A_1=1, A_0=0$ )

Control Register = 83H ( $A_1=1, A_0=1$ )

The control word of the interfacing ckt will be:

1 0 0 1 0 X X 1 = 91H


Here, Port A = mode 0 input

Port B = not used

Port C = Input (PC0)

Port CU = Output (PC4 - PC7)

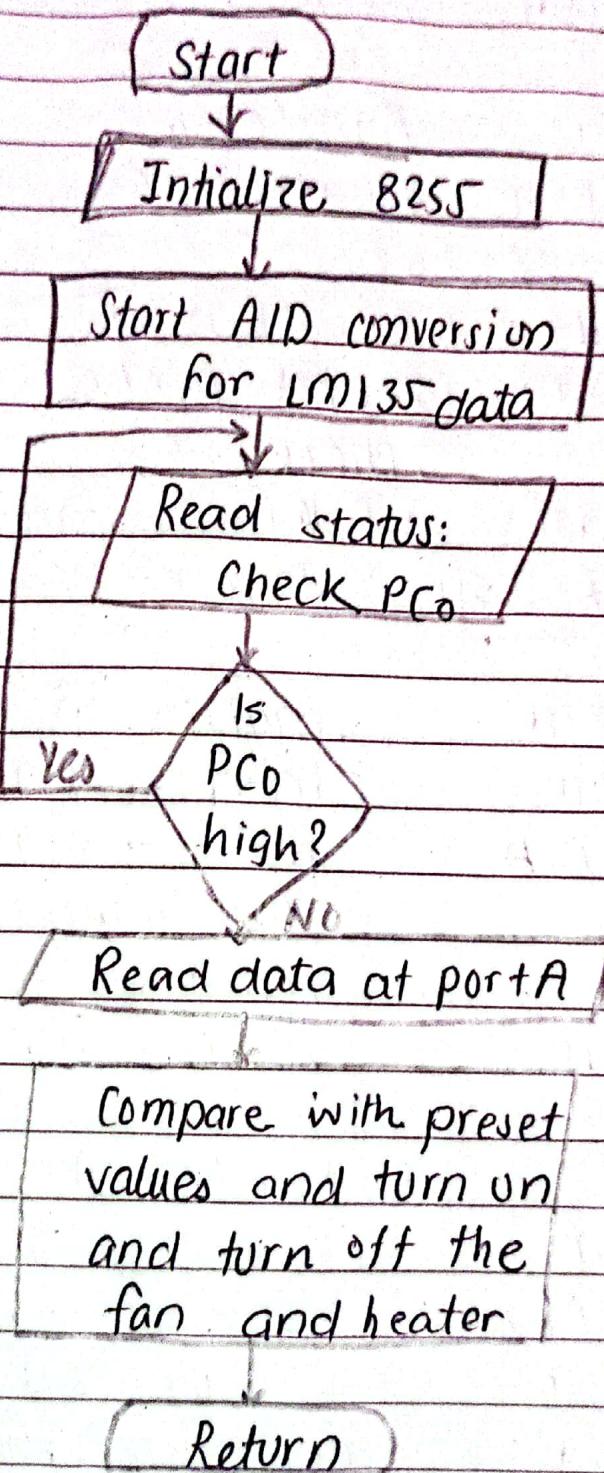The following flowchart facilitates the operation of the design:



Following sub-routine facilitates the software operation

TEMP : MVI A, 91H ; control word  
OUT 83H ; control register  
MVI A, 0FH ; to set PC7

OUT 83H ; disable RD  
MVI A,09H ; to set PC4

OUT 83H ; enable WR  
MVI A,08H ; to reset PC4

OUT 83H ; SOC when WR goes to 1  
STATW: IN 82H ; read port G  
RAR ; check PC0  
JC STATUS ; if # high stay in loop  
MVI A,0EH ; to reset PC7

OUT 83H ; enable RD  
IN 80H ; read port A  
MOV B,A ; read port P  
; save temperature  
; reading  
OUT 83H ; disable RD

IN 80H ; read port A  
MOV B,A ; save temperature reading  
MVI A,0FH ; to set PC7  
OUT 83H ; disable RD  
MOV A,B ; get temperature reading  
CPI 23H ; check 35°C  
CNC FAN ON ;  
CC FAN OFF ;  
CPI 0AH ; check 10°C


DATE

Page

CNC Heater ON  
CNC HEATER OFF  
RET

Q.5 Interface a keyboard and a printer in mode 1. Port A is designed as input for keyboard with interrupt I/O port B is designed as output for printer with status check I/O. Draw the mapping circuit and write the control word and address map.

Soin

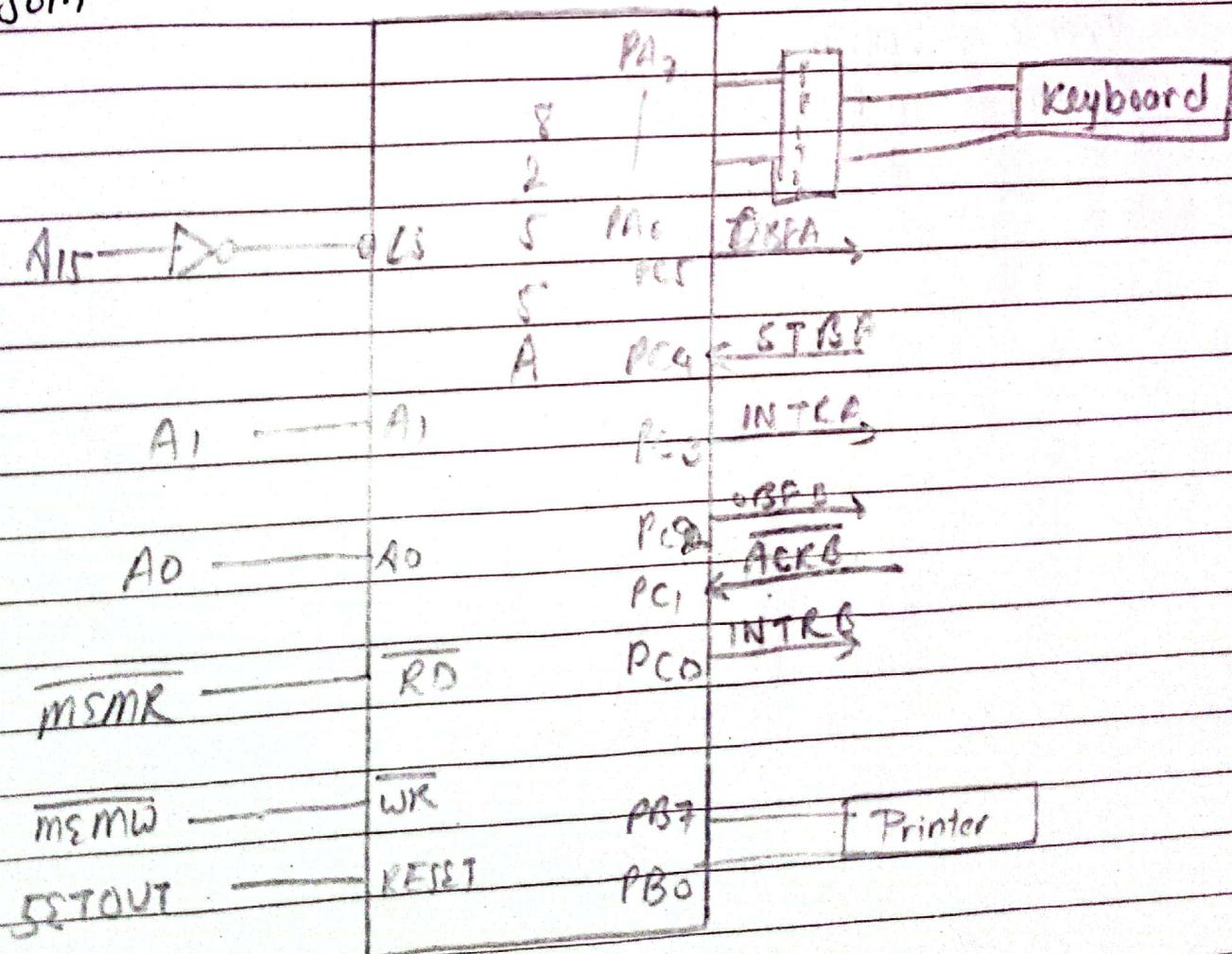

Control word:

D<sub>7</sub> D<sub>6</sub> D<sub>5</sub> D<sub>4</sub> D<sub>3</sub> D<sub>2</sub> D<sub>1</sub> D<sub>0</sub>  

1	0	1	1	X	1	1	X
---	---	---	---	---	---	---	---

 = C6H

Address A<sub>15</sub> A<sub>14</sub> A<sub>13</sub> A<sub>12</sub> A<sub>11</sub> A<sub>10</sub> A<sub>9</sub> A<sub>8</sub> A<sub>7</sub> A<sub>6</sub> A<sub>5</sub> A<sub>4</sub> A<sub>3</sub> A<sub>2</sub> A<sub>1</sub> A<sub>0</sub>  
2000H 0 0 1 X X X X X X X X XX XX X X

Hence Port address are

Port A : 2000H

Port B : 2001H

Port C : 2002H

Control Register : 2003H