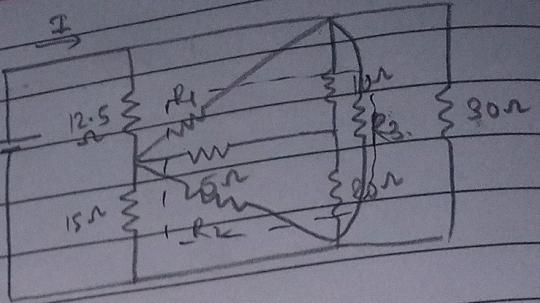


2018  
fall

[Q.No. 1b]

Soln.

Converting  $(5\Omega - 10\Omega - 20\Omega)$  into delta form.




$$R_1 = \frac{5 \times 10 + 5 \times 20 + 10 \times 20}{20} = 20\Omega$$

$$R_2 = \frac{5 \times 10 + 5 \times 20 + 10 \times 20}{10} = 40\Omega$$

$$R_3 = \frac{5 \times 10 + 5 \times 20 + 10 \times 20}{5} = 80\Omega$$

Convert

80Ω and 80Ω are in parallel so,

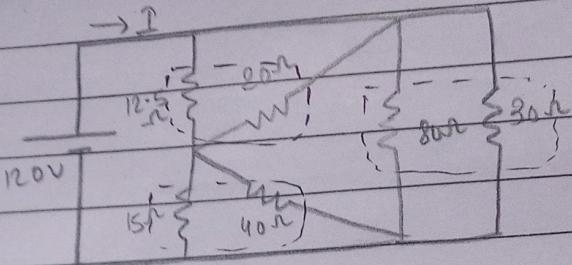


$$\text{Reqv}_1 = \frac{80 \times 80}{80 + 80} = 21.81\Omega$$

12.5Ω and 20Ω in parallel,

$$\text{Reqv}_2 = 12.5 // 20 = 7.69\Omega$$

15Ω and 40Ω are in parallel,
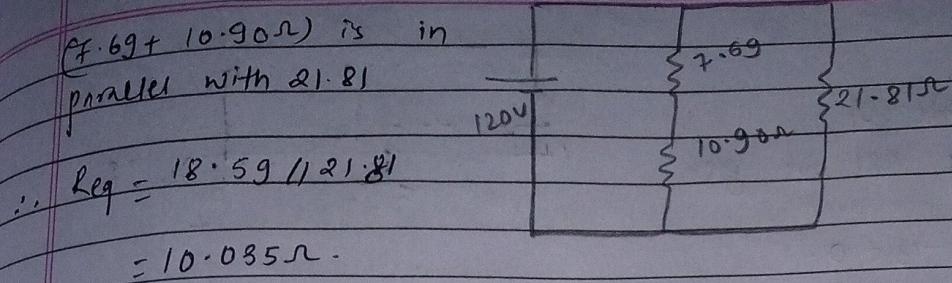
$$\text{Reqv}_3 = 15 // 40 = 10.90\Omega$$



Finally,

$$\text{current } (I) = \frac{V}{R} = \frac{120}{10.035} = 11.958 \text{ A Ans}$$

Q. No. 2a

QCL :-

It states that "The sum of electrical currents in any node of circuit is zero. It follows the law of conservation of energy. which met. Therefore, total incoming current is equal to total outgoing current.

KVL :-

It states that "The sum of total emf in any loop is equal to the sum of voltage drops in the same loop."


$\Rightarrow$

Soln:

Here,

At node  $V_1$ ,

Applying KCL we get,

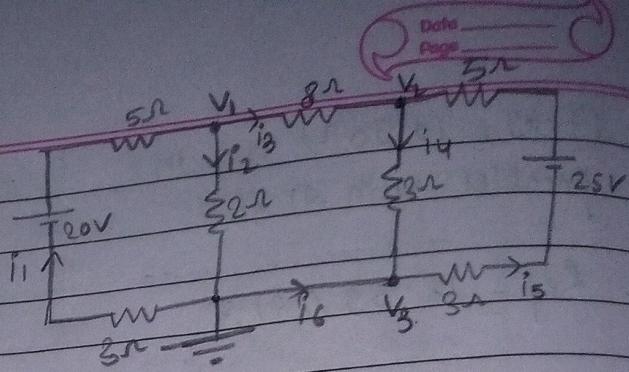

$$i_1 - i_2 - i_3 = 0.$$

$$\text{or, } \frac{0 - V_1 + 20}{8} - \frac{V_1 - 0}{2} - \frac{V_1 - V_2}{8} = 0.$$

$$\text{or, } -8V_1 + 160 - 20V_1 - 5V_1 + 5V_2 = 0$$

$$\text{or, } -28V_1 - 20V_1 - 5V_1 + 5V_2 = 0$$

$$\text{or, } -6V_1 + V_2 + 20 = 0 \quad \text{--- (1)}$$

At node  $V_2$ , applying KCL,

$$i_3 - i_4 + i_5 = 0$$

$$\text{or, } \frac{V_1 - V_2}{8} - \frac{V_2 - V_3}{3} + \frac{V_3 - V_2 + 25}{8} = 0$$

$$\text{or, } -3V_1 + 3V_2 - 8V_2 + 8V_3 + 8V_3 - 3V_2 + 25 = 0$$

$$\text{or, } 8V_1 - 14V_2 + 11V_3 + 25 = 0. \quad \text{--- (II)}$$

Applying KCL at node  $V_3$ ,

$$i_6 + i_4 - i_5 = 0$$

$$\text{or, } 0 - V_3 + \frac{V_2 - V_3}{3} - \frac{V_3 - V_2 + 25}{8} = 0.$$

$$1) -24V_1 + 8V_2 - 8V_3 - 3V_4 + 3V_5 - 75 = 0$$

$$2) -24V_1 + 11V_2 - 11V_3 - 75 = 0 \quad (ii)$$

Solving (i), (ii) and (iii) using calculator we get

$$V_1 = -1.53V$$

$$V_2 = 10.76V$$

$$V_3 = 20.944V$$


Ans

[A.N.2b]


Thevenin theorem.

Norton's theorem.

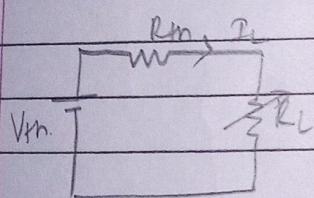- They are used in parallel circuit.
- They're also used in parallel circuit.
- They're used in solving electric circuit where circuit part is fixed & load is variable.
- They're also used in solving the electric circuit where circuit part is fixed & load is variable.
- It is similar to that of practical current source.
- It is similar to that of practical current source.





$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

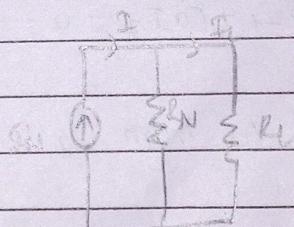

$$I_L = \frac{R_N}{R_N + R_L} \times I_N$$

Next part :-

Here,  
finding  $R_N$ ,

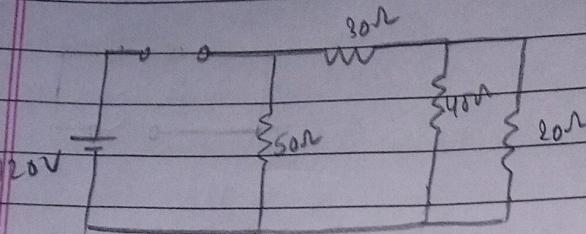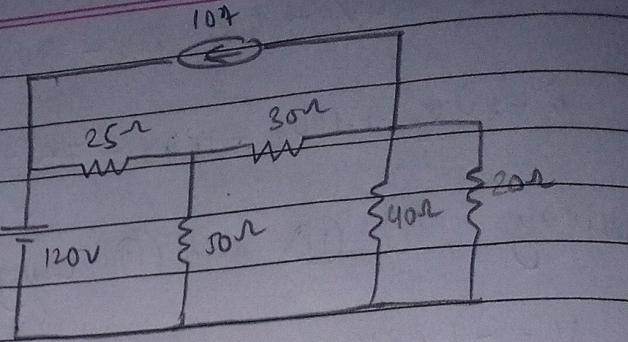

$$R_N = (50 + 30) // [40 // 20]$$

$$= 80 // 13.33$$


$$= 11.42\Omega$$

Now,

Finding  $I_N$  :-

Current in mesh  $I_4$  is,

$$I_4 = -10A$$

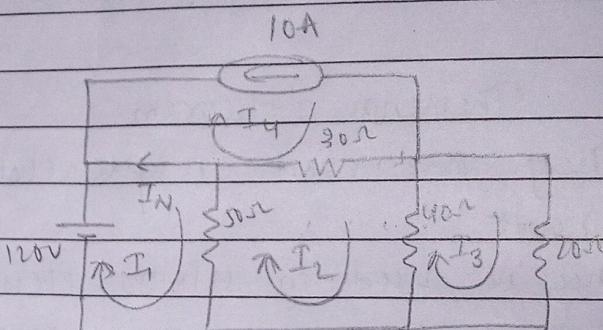

Applying KVL at mesh  $I_1$

$$120 - 50I_1 - I_2 = 0$$

$$\therefore 120 - 50I_1 + 50I_2 = 0 \quad \text{--- (1)}$$

Applying KVL at mesh  $I_2$ ,

$$-50(I_2 - I_1) - 30(I_2 - I_4) - 40(I_2 - I_3) = 0$$

$$\therefore -50I_2 + 50I_1 - 30I_2 + 30I_4 - 40I_2 + 40I_3 = 0$$

$$50I_1 - 120I_2 + 40I_3 - 300 = 0$$

Applying KVL at mesh I<sub>3</sub>,

$$-40(I_3 - I_2) - 20I_3 = 0 \quad (1)$$

$$40I_2 - 60I_3 = 0 \quad (2)$$

Solving (1), (2) and (3) using calculator we get,

$$I_1 = 1.75A$$

$$I_2 = 4.15A$$

$$I_3 = 2.46A$$

$$\therefore I_N = I_1 = -1.75A (\leftarrow) = 1.75A (\rightarrow)$$

finally,

$$I_{25} = \frac{R_N}{R_N + R} \times I_N$$
$$= \frac{11.42}{11.42 + 25} \times 1.75$$
$$= 0.54A \text{ Ans}$$

[Q.No. 39]


$\Rightarrow$

801n.

Here,

$$R_L = ?$$

Max power = ?

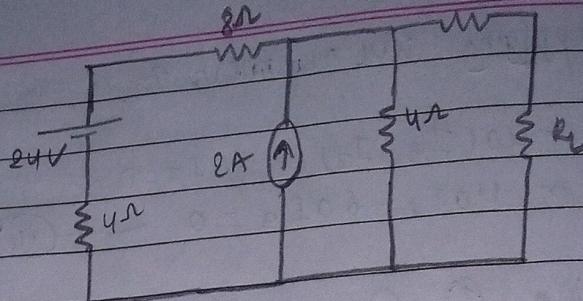


Now,

finding  $R_L$ ,

$$R_L = (4+8)/(4+6)$$

$$= 12/10$$

$$= 5.45\Omega$$

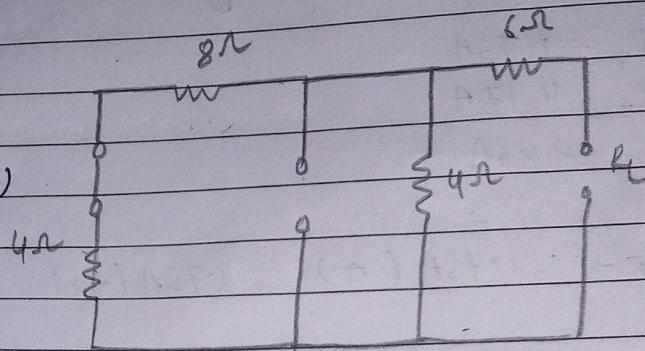


Now We know, for maximum power transferred to the load, load resistance must be equal to thevenin resistance.

$$\therefore R_{th} = R_L = 5.45\Omega$$

finding  $V_{th}$  :-

$$V_{th} = V_2 - 0.$$

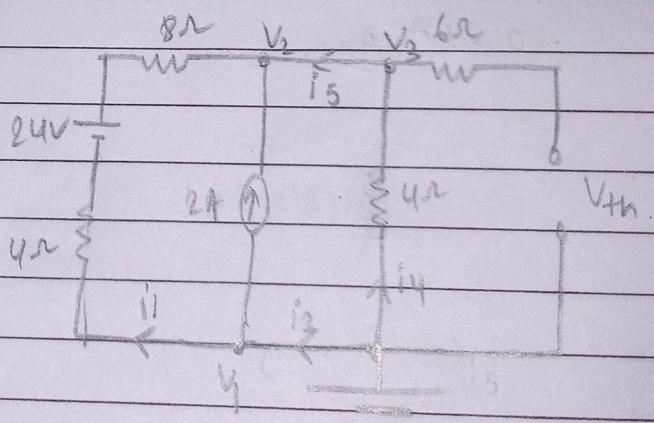

Applying KCL at node  $V_1$

$$i_2 - i_1 - 2 = 0$$

$$\text{or } 0 - V_1 - \frac{V_1 - V_2 + 24}{12} - 2 = 0$$

$$\text{or } -V_1 - \frac{V_1 - V_2 + 24}{12} - 2 = 0$$

$$\text{or } -13V_1 + V_2 = 0 \quad (1)$$

$$\therefore V_2 = 13V_1 \quad (1)$$

Applying KCL at node  $V_2$

$$i_5 + 2 + i_1 = 0$$

$$\text{or } V_3 - V_2 + 2 + \frac{V_1 - V_2 + 24}{12} = 0$$

$$\text{or } 12V_3 - 12V_2 + 24 + V_1 - V_2 + 24 = 0$$

$$\text{or } V_1 - 13V_2 + 12V_3 + 48 = 0 \quad (10)$$

Applying KCL at node  $V_3$

$$i_4 - i_5 = 0$$

$$\text{or } 0 - V_3 - \frac{V_3 - V_2}{4} = 0$$

$$\text{or } -V_3 - 4V_3 + 4V_2 = 0$$

$$\text{or } -5V_3 + 4V_2 = 0 \quad (11)$$

Solving (i), (ii) and (iii) using calculator.

$$\text{Q} V_1 = -1.11 \text{ V}$$

$$V_2 = -14.44 \text{ V}$$

$$V_3 = -11.56 \text{ V}$$

$$\therefore V_{ph} = V_3 - 0 = -11.56 \text{ V}$$

Now,

The maximum power dissipated is:

$$P_{max} = \frac{(V_{ph})^2}{4R_{th}} = \frac{(-11.56)^2}{4 \times 5.45} = 6.129 \text{ watt Ans}$$

[A.No. 4(a)]

Phase - 80°

Given,

$$Z_1 = (80 + j5) \Omega$$

$$Z_2 = (80 + j8) \Omega$$

$$\therefore Z = (80 + j5) + (80 + j8)$$

$$= 81.66 \angle 14.57^\circ \Omega$$

Active power (P) =  $VITC$

$$\text{Current (I)} = \frac{V_{ph}}{Z_{ph}} = \frac{400}{81.66 \angle 14.57^\circ} = 7.74 \angle -14.57^\circ \text{ A. (lag).}$$

$$(ii) \text{ power factor} = \cos \phi \\ = \cos 14.57 \\ = 0.96.$$


$$(iii) \text{ Active power } (P) = VI \cos \phi \\ = 200 \times 7.74 \times 0.96 \\ = 1486.08 \text{ WATT}$$

$$(iv) \text{ Reactive power } (Q) = VI \sin \phi \\ = 200 \times 7.74 \times \sin(14.57) \\ = 887 \text{ VAR}$$

$$(v) \text{ Apparent power } (S) = \sqrt{P^2 + Q^2} \\ = \sqrt{1486.08^2 + 387^2} \\ = 1535.644 \text{ VA. Am}$$

[Q.No. 4b]

Resonance in parallel RLC circuit:-

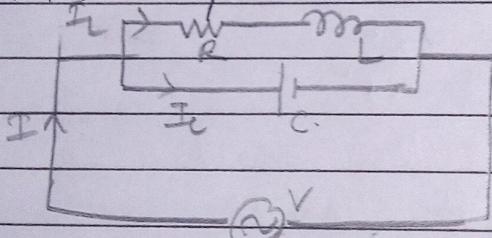

Let a circuit where capacitance  $C$  is connected in parallel with an inductive coil of resistance  $R$  & Inductive inductance  $X_L$  as shown in figure.

where  
 $I_R$  = current through resistor  
 $I_C$  = current through capacitor.  
 $I$  = total current.

Under resonance,  $P_f$  is unity, reactive component of total current is zero. The reactive component of the ~~total~~ current is  $\cancel{I_C} (I_C - I_L \sin \phi) = 0$ .  
 where,  $\phi$  is the power factor angle of coil.

Hence,

$$I_C = I_L \sin \phi$$

$$\frac{V_L}{X_C} = \frac{V}{Z_L} \times \frac{X_L}{Z_L}$$

$$\text{or, } X_L X_C = Z_L^2$$

$$\text{or, } \frac{w_L}{w_C} = Z_L^2 = R^2 + (w_L)^2$$

$$\text{or, } (w_L)^2 = \frac{1}{C} - R^2$$

$$\text{At resonance, } w_r = \sqrt{\frac{1}{LC} - \frac{R^2}{C^2}}$$

At resonance frequency,

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

If resistance is neglected,

$$\omega_r = \frac{1}{\sqrt{LC}}$$

and,

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

If resistance is neglected, resonance frequency of parallel RLC circuit is equal to the series RLC circuit.


At resonance:-

- Resonance frequency,  $f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$

- Pf is unity.

- Net susceptance is zero i.e.  $\left( w_L - \frac{1}{w_C} \right) = 0$

[Q.No. 5a]

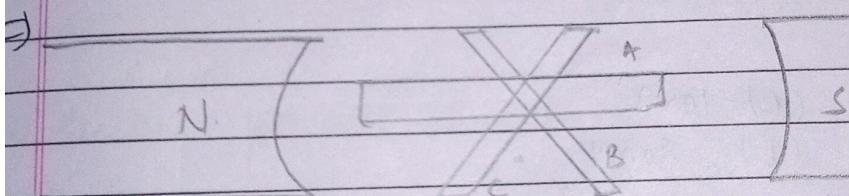

Three phase voltage can be generated by placing three rectangular coils displaced in space by  $120^\circ$  in a uniform magnetic field. When these coils rotate with uniform angular velocity of  $n$  rad/sec, a sinusoidal emf displaced by  $120^\circ$  is induced in these coils.

Next part:-

Advantages of 3  $\phi$  over 1  $\phi$ :

- Power in 3 phase is always almost constant i.e. power never falls to zero. But in single phase power may fall to zero.
- 3  $\phi$  requires less copper i.e. only  $3/4$ th the total copper than 1  $\phi$  system.
- Efficiency in polyphase generator is very high than single phase.
- 3  $\phi$  motors can be made self starting.

For the given size of frame, output in 3 phase machine is very high.

[Q No. 5b]

Sol/h:

Given,

$$\text{Resistance } (R) = 100 \Omega$$

$$\text{Inductance } (L) = 20 \text{ mH}$$

$$= 20 \times 10^{-3} \text{ H}$$

$$= 0.02 \text{ H}$$

$$\therefore X_L = \omega \pi f L = 6.28 \Omega$$

$\Rightarrow$

Case II:-

In delta connected load:-

We know,

$$V_L = V_{ph} = V = 2100 \text{ V.}$$

$$I_L = \sqrt{3} I_{ph}$$

Now,

$$Z_{ph} = R + jX_L = 100 + j6.28 \Omega = 100.196 \angle 3.59^\circ \Omega$$

$$(i) I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{400 \angle 0^\circ}{100.196 \angle 3.59^\circ} = 3.992 \angle -3.59^\circ \text{ A (lag)}$$

$$(ii) I_L = \sqrt{3} I_{ph} = \sqrt{3} (3.992 \angle -3.59^\circ) \\ = 6.914 \angle -3.59^\circ \text{ A (lag)}$$

$$(iii) \text{pf} = \cos \phi = \cos 3.59^\circ = 0.99$$

$$v) \text{Active power}(P) = VI \cos \phi = 400 \times 3.992 \times 0.99 \\ = 1580.832 \text{ Watt.}$$

$$i) \text{Reactive power}(Q) = VI \sin \phi = 400 \times 3.992 \times \sin(3.59^\circ) \\ = 99.6016 \text{ VAR}$$

$$iv) \text{Apparent power}(S) = \sqrt{P^2 + Q^2} \\ = \sqrt{1580.832^2 + 99.6016^2}$$

$$= 1583.929 \text{ VA Ans}$$

Case II:-  
By star connected load,

We know,

$$V_L = \sqrt{3} V_{ph} \quad \text{and} \quad I_L = I_{ph}$$
$$(ii) \quad P_L = I_{ph} = 9.992 \angle -3.59^\circ A$$

$$(iii) \text{ Active power} = VI$$

Now,

$$V_L = \sqrt{3} V_{ph}$$
$$V_{ph} = \frac{400}{\sqrt{3}} = 230.94 V$$

$$\therefore I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.94}{100.196 \angle 3.59^\circ} = 2.30 \angle -3.59$$

$$(i) \quad I_L = I_{ph} = 2.30 \angle -3.59^\circ A (1y)$$

$$(ii) \quad \text{Active power} = VI \cos \phi$$
$$= 230.94 \times 2.30 \times 0.99$$
$$= 525.85 \text{ Watt}$$

$$(iii) \quad \text{Reactive power} = VI \sin \phi$$
$$= 230.94 \times 2.30 \times \sin 3.59$$
$$= 32.932 \text{ VAR}$$

$$iv) \quad \text{Apparent power} = \sqrt{P^2 + Q^2}$$
$$= \sqrt{525.85^2 + 32.932^2}$$
$$= 526.8801 \text{ VA}$$

[Q.No. 6b]

Soln.

Given,

$$\text{primary leakage resistance } (x_1) = 0.7 \Omega$$

$$\text{secondary leakage resistance } (x_2) = 0.9 \Omega$$

$$\text{per primary resist resistance } = 0.5 \Omega$$

$$\text{secondary resistance } (R_2) = 0.8 \Omega$$

$$K = \frac{250}{500} = 0.5$$

Equivalent <sup>resistance</sup> referred to primary side :-

$$R_{01} = R_1 + \frac{R_2}{K^2} = 0.5 +$$

$$= 0.5 + \frac{0.8}{(0.5)^2} = 3.7 \Omega$$

Equivalent resistance referred to secondary side :-

$$X_{01} = \frac{x_1 + x_2}{K^2} = \frac{0.7 + 0.9}{(0.5)^2} = 4.3 \Omega$$

$$Z_{01} = \sqrt{R_{01}^2 + X_{01}^2} = \sqrt{3.7^2 + 4.3^2}$$

$$= 5.67 \Omega$$

(b) Equivalent parameter referred to secondary side:



$$\begin{aligned} R_{01} &= R_2 + k^2 R_1 \\ &= 0.8 + (0.5)^2 \times (0.5) \\ &= 0.925 \Omega \end{aligned}$$

$$X_{01} = X_2 + k^2 X_1 = 1.075 \Omega$$

$$Z_{01} = \sqrt{X_{01}^2 + R_{01}^2} = 1.041 \Omega \text{ Ans}$$

[Q.No. 7b]

⇒ Operation of transformer on load:-

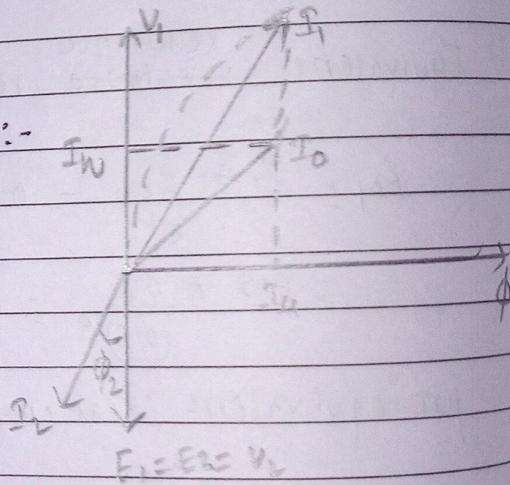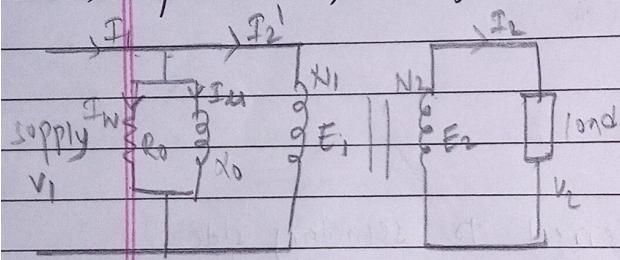

When the load is connected to the secondary, the load current flows through the load as well as secondary winding ( $I_2$ ). It includes the self mmf ( $N_2 I_2$ ) which produces the flux  $\phi_2$ , that opposes the main flux  $\phi_1$  and weakens it hence tries to reduce the  $E_1$ . If  $E_1$  falls below the initial level, the extra current flowing from source to primary winding ( $I_1'$ ) produces the flux ( $\phi_1'$ ) which

It includes the self mmf ( $N_2 I_2$ ) which produces the flux  $\phi_2$ , that opposes the main flux  $\phi_1$  and weakens it hence tries to reduce the  $E_1$ . If  $E_1$  falls below the initial level, the extra current flowing from source to primary winding ( $I_1'$ ) produces the flux ( $\phi_1'$ ) which

neutralize the main flux ( $\phi_2$ ). Hence the main flux  $\phi$ , remains unchanged irrespective of load.

[Q.No.7c]

Working principle of 3 phase induction motor:-

When a  $3\phi$  supply is given to the stator, a rotating magnetic field is produced in stator. The rotating magnetic field produced by stator cuts the rotor conductor and hence emf will be induced on the rotor conductor as per law of electromagnetic induction.

As the rotor conductor are short circuited, current will circulate within the rotor conductor. Since these current carrying rotor conductor are lying in the magnetic field produced by the stator, hence, force will develop on rotor conductor and the rotor starts rotating under the action of this force.