

**INSTITUTE OF ENGINEERING
ADVANCED COLLEGE OF ENGINEERING
& MANAGEMENT**

**KUPONDOLE , LALITPUR
(AFFILATED TO TRIBHUVAN UNIVERSITY)**



LAB REPORT

EXP. No - 03 .

SUBMITTED BY

NAME – ASHWANI KUMAR CHAUDHARY

ROLL NO. – 020

DATE - 2018/07/05

SUBMITTED TO

**DEPARTMENT OF
Electrical.**

TITLE : To Calculate & Verify AC Parameters.





OBJECTIVE:

To calculate & verify AC parameters.

THEORY:

An Alternating ^{quantity} (Current or Voltage) is one whose magnitude change continuously with time betⁿ zero & a maximum value & whose direction reverse periodically. Some graphical representation for alternating quantities.

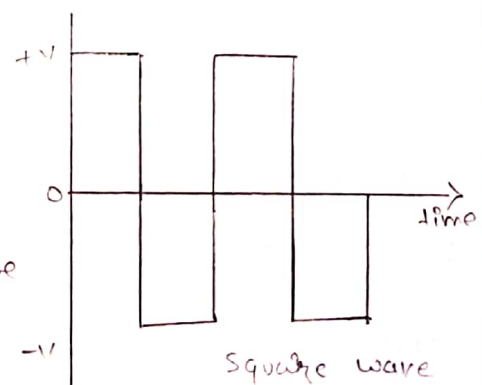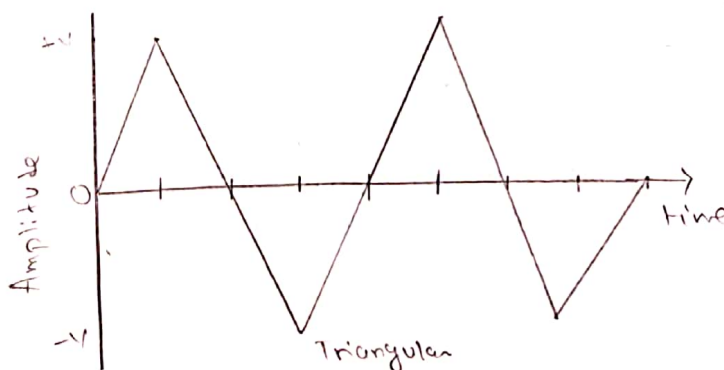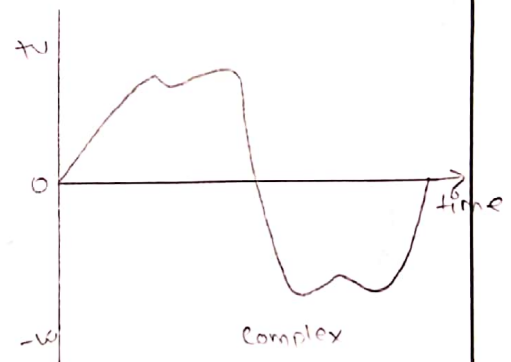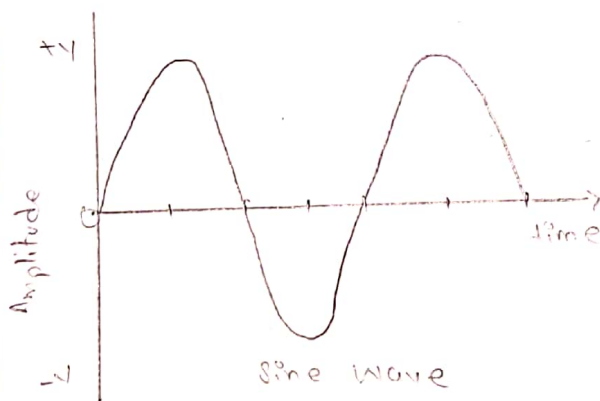As shown in the image below, AC wave form can be sinusoidal (sine wave), complex, square or triangle.



① Amplitude: The maximum value of attained by alternating quantity is called amplitude.

② frequency: Total no. of cycles per second.

③ Time period: Time (msec) required by an alternating quantity to complete its one cycle is known as time period.

④ Angular Velocity: The frequency of an alternating quantity expressed in electrical radians per second is known as Angular velocity.

⑤ Peak voltage (V_p): The maximum instantaneous value of function as measured from the zero voltage level.

⑥ Peak to peak voltage (V_{p-p}):
The full voltage between positive & negative peaks of waveform that is the sum of the magnitude of the positive & negative peaks.

⑦ RMS voltage (V_{rms}):
The root mean-square or effective value of a waveform.

⑧ Average Voltage (V_{avg}):
The level of waveform defined by the condition that the area enclosed by the curve above this level is exactly equal to the area enclosed by the curve below this level.

OBSERVATION 1 : AC Signal.

Vertical deflection (p-p) = 6.8 cm

$$\text{Volt/cm} = 2 \text{ V/cm}$$

$$V_{p-p} = 13.6 \text{ V}$$

$$V_{rms} = \frac{V_{p-p}}{2\sqrt{2}} = 4.8 \text{ V}$$

$$V_{avg} = \frac{2V_p}{\pi} \text{ or } \frac{V_{p-p}}{\pi} = 4.32 \text{ V}$$

for 50 Hz.

Horizontal deflection (p-p) = 4 cm

Time/cm = 5 ms

Total time period (T) = 20 ms

$$\begin{aligned} \text{frequency (f)} &= \frac{1}{T} \text{ Hz} \\ &= 50 \text{ Hz} \end{aligned}$$

for 100 Hz.

Horizontal deflection = 4 cm

Time/cm = 2.4 ms

Total time period (T) = 10 ms

$$\begin{aligned} \text{frequency (f)} &= \frac{1}{T} \text{ Hz} \\ &= \frac{1000}{10} = 100 \text{ Hz} \end{aligned}$$

OBSERVATION 2.

R-C series circuit

$$\text{frequency } (f) = 100 \text{ Hz}$$

$$\Delta t = \frac{2.5}{5} \times 2.5$$

$$= 1.25 \text{ ms}$$

$$= 1.25 \times 10^{-3}$$

$$\phi = 360 \times f \times \Delta t$$

$$= 360 \times 100 \times 1.25 \times 10^{-3}$$

$$= 45^\circ$$

$$C = 1 + 0.1$$

$$= 1.1 \mu\text{f}$$




$$= 1.1 \times 10^{-6} \text{ f}$$

$$X_C = \frac{1}{2\pi fC}$$

$$= 1446.28 \text{ } \Omega$$

$$\tan \theta = \frac{X_C}{R}$$

$$R = 1446.28$$

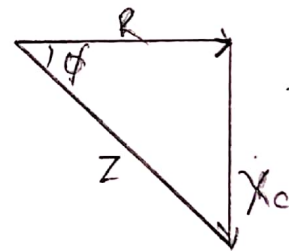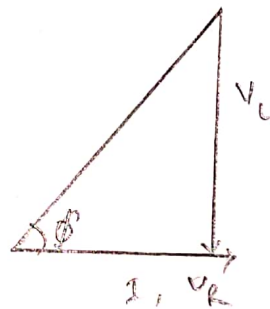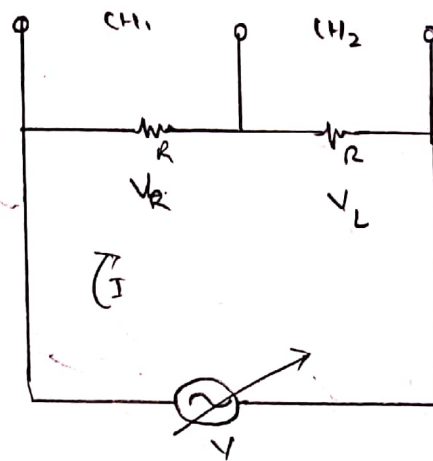

R-L Series

$$f = 100 \text{ Hz}$$

$$\Delta t = \frac{2.5}{5} \times 1$$

$$= 0.5$$

$$= 0.5 \times 10^{-3}$$

$$L = 602 \text{ mH}$$

$$= 602 \times 10^{-6} \text{ H}$$

$$\phi = 360 \times f \times \Delta t$$

$$= 360 \times 100 \times 0.5 \times 10^{-3}$$

$$= 18^\circ$$

$$X_L = 2\pi fL$$

$$= 2 \times \frac{22}{7} \times 100 \times 602 \times 10^{-6}$$

$$= 3.78 \times 10^{-3} \text{ H}$$

$$R = 0.0156 \Omega$$

Discussion & Conclusion

**INSTITUTE OF ENGINEERING
ADVANCED COLLEGE OF ENGINEERING
& MANAGEMENT**

**KUPONDOLE, LALITPUR
(AFFILATED TO TRIBHUVAN UNIVERSITY)**



LAB REPORT

EXP. No - 04.

SUBMITTED BY

NAME – ASHWANI KUMAR CHAUDHARY

ROLL NO. - 020

DATE - 2078/07/05

SUBMITTED TO

**DEPARTMENT OF
Electrical.**

TITLE: Three - phase AC circuit

OBJECTIVE:

1. To measure current & voltage in three phase AC circuit.
2. To prove star-delta transformation.

THEORY:

A balanced three phase network is one in which the impedance in the three phase are identical with such a balanced load, if a balanced three-phase supply is applied, the current will also be balanced.

A balanced three phase voltage or current is one in which the size of each phase is the same & the phase angle of the three phase differ from each other by 120° degrees.

In three phase circuit connections can be given in two types.

- (a) Star - connection
- (b) delta - connection

1. Star- Connection.

$$V_{pn} = \frac{V_L}{\sqrt{3}}$$

$$I_{PH} = I_L$$

Table 1.

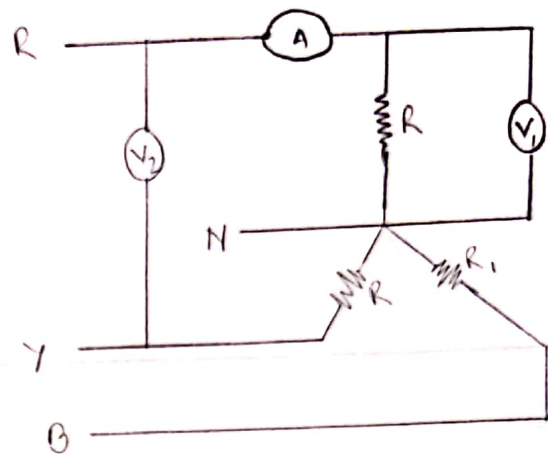


Table : 1.

| S.N | V_L | V_P | $I_L = I_P$ | $V' = \sqrt{3} V_P$ | $P = \sqrt{3} V_L I_L$ |
|-----|-------|-------|-------------|---------------------|------------------------|
| 1 | 50 | 29.5 | 0.09 | 51.095 | 7.794 |
| 2 | 75 | 42.8 | 0.13 | 74.181 | 16.887 |
| 3 | 100 | 57.8 | 0.18 | 99.246 | 31.176 |
| | | | | | |


→ In star-connection, the line voltage is $\sqrt{3}$ times of phase voltage.

$$I_{line} = \sqrt{3} I_{phase} \quad \& \quad I_{line} = I_{phase}$$

2. Delta-Connection.

$$I_{PH} = \frac{I_L}{\sqrt{3}}$$

$$V_{PH} = V_L$$

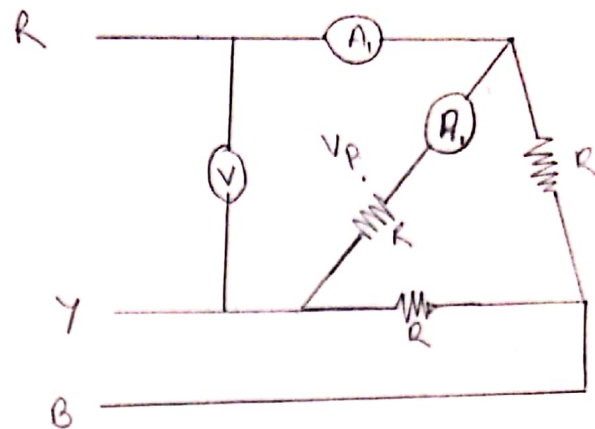

| S.N | $V_{PH} = V_L$ | I_P | I_L | $I_L' = \sqrt{3} I_P$ | $P = \sqrt{3} V_L I_L$ |
|-----|----------------|-------|-------|-----------------------|------------------------|
| 1 | 50 | 0.3 | 0.47 | 0.519 | 40.73 |
| 2 | 75 | 0.45 | 0.7 | 0.779 | 90.93 |
| 3 | 100 | 0.61 | 0.93 | 1.056 | 161.08 |
| | | | | | |

In delta connection, the line voltage is the same as that of phase voltage & the line current is $\sqrt{3}$ times of phase current. It is shown as below.

$$I_{line} = I_{phase} \text{ \& } I_{line} = \sqrt{3} I_{phase}.$$

Discussion & Conclusion.

Thus, we verified the current & voltage in three phase AC circuit & star-delta transformation of AC circuits.

Hence, current & voltage source were measured in three phase AC circuit & star-delta transformation was proved.

Precautions.

- 1) The instruments should be handled with care.
- 2) The connection should be tight.
- 3) Error should be minimized.