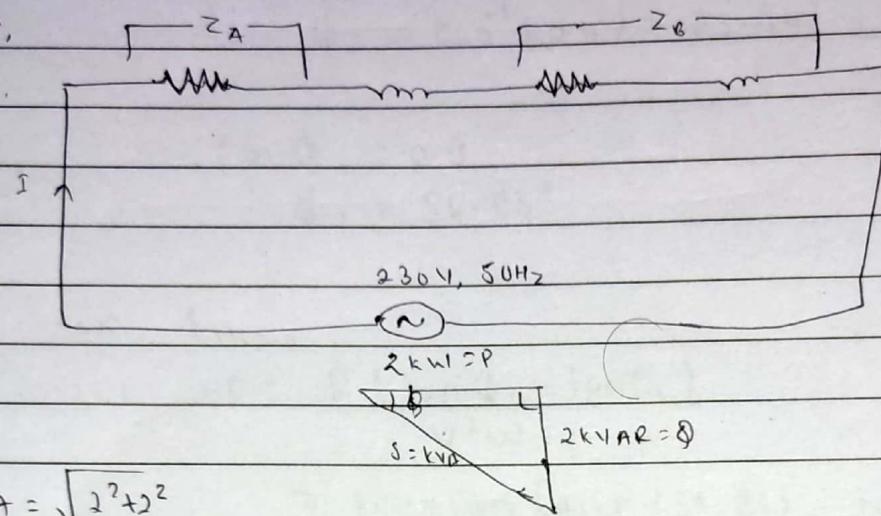


Assignment - 4

Q

$\Rightarrow 50\text{VA}$



$$\text{KVA} = \sqrt{Z^2 + 2^2}$$

$$= 2.82$$

$$= 2820 \text{ VA}$$

Th,

$$\text{Current through circuit (I)} = \frac{2820}{230} = 12.26 \text{ A}$$

Also,

$$P = I^2 R_{\text{eqv}}$$

$$2000 = (12.26)^2 (R_A + R_B)$$

$$\frac{2000}{(12.26)^2} = 5 + R_B$$

$$R_B = 8.30 \Omega$$

Then,

$$\text{Impedance of whole circuit } (Z_r) = \frac{230}{12.26}$$

$$= 18.76$$

$$\begin{aligned} X_A + X_B &= \sqrt{Z^2 - (R_A + R_B)^2} \\ &= \sqrt{(18.76)^2 - (5 + 8.30)^2} \\ &= \sqrt{(18.76)^2 - (13.3)^2} \\ &= 13.23 \Omega \end{aligned}$$

Now,

$$\begin{aligned} X_B &= 2\pi f L_B \\ &= 2\pi \times 50 \times 0.018 \\ &= 5.65 \Omega \end{aligned}$$

$$\begin{aligned} X_A &= 13.22 \Omega - 5.65 \Omega \\ &= 7.58 \Omega \end{aligned}$$

$$2\pi f L_A = 7.58$$

$$\begin{aligned} L_A &= \frac{7.58}{2\pi f} = \frac{7.58}{2\pi \times 50} \\ &= 0.024 \text{ H.} \end{aligned}$$

Then,

$$\begin{aligned} Z_A &= \sqrt{R_A^2 + X_A^2} \\ &= \sqrt{8^2 + 7.58^2} \\ &= 9.080 \Omega \end{aligned}$$

Then,

$$\begin{aligned} \text{Pd across coil A} &= I \cdot Z_A \\ &= 12.26 \times 9.08 \\ &= 120.148 \text{ V.} \end{aligned}$$


$$\begin{aligned} Z_B &= \sqrt{R_B^2 + X_B^2} = \sqrt{8.30^2 + 5.65^2} \\ &= 10.048 \Omega \end{aligned}$$

Then,

$$\begin{aligned} \text{Pd. across coil B} &= I \cdot Z_B \\ &= 12.26 \times 10.04 \\ &= 123.09 \text{ V} \end{aligned}$$

Inductance of coil A (L_A) = 0.024 HResistance of coil B (R_B) = 8.30 ΩVoltage across each coil. (V_A) = 120.148 V
(V_B) = 123.09 V

Q. 4b

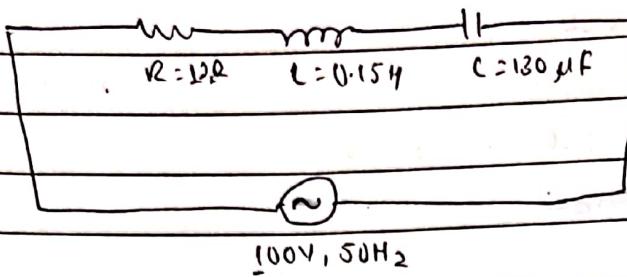 \Rightarrow Soln.

$$R = 12 \Omega$$

$$L = 0.15 \text{ H}$$

$$C = 130 \mu\text{F} = 130 \times 10^{-6} \text{ F}$$

$$f = 50 \text{ Hz}$$

Then,

$$X_L = 2\pi f L = 2\pi \times 50 \times 0.15 \\ = 47.12 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 130 \times 10^{-6}} \\ = 24.48 \Omega$$

Then,


$$\text{i) Impedance } (Z) = R + jX_L - jX_C \\ = 12 + j47.12 - j24.48 \\ = 25.62 \angle 62.07^\circ$$

$$\text{ii) Current through circuit } (I) = \frac{100 \angle 0^\circ}{25.62 \angle 62.07^\circ} \\ = 3.90 \angle -62.07^\circ$$

$$\text{iii) Phase angle } (\phi) = 62.07^\circ$$

$$\text{iv) Power factor} = \cos \phi \\ = \cos (62.07^\circ) \\ = 0.468 \text{ (lagg)}$$

Q40

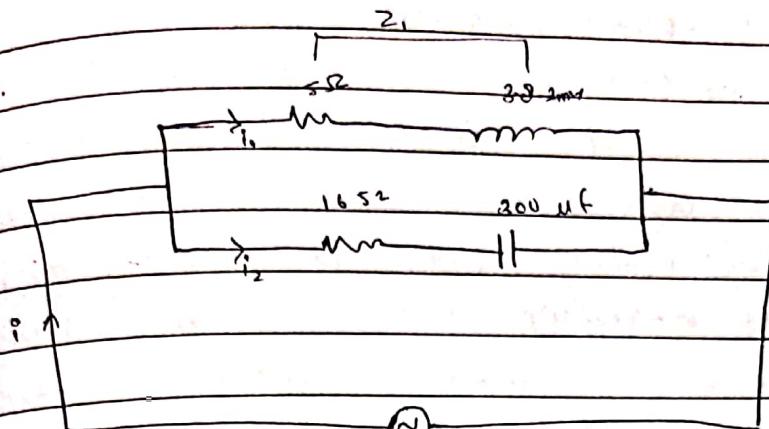 $\Rightarrow 50\text{ A}$ 

$$I = 20 \cdot 2 \text{ mH} = 0.382 \times 10^{-3} \text{ A}$$

$$e = 300 \mu\text{F} = 300 \times 10^{-6} \text{ F}$$

Then,

$$X_L = 2\pi f L = 2\pi \times 50 \times 38.2 \times 10^{-3}$$

$$\approx 12 \Omega$$

$$Y_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 300 \times 10^{-6}}$$

$$= 10.63 \Omega$$

Then

$$Z_1 = R_1 + jX_L = 5 + j12$$

$$= 13 \angle 67.38^\circ$$

$$Z_2 = R_2 - jX_C = 16 - j10.61$$

$$= 19.198 \angle -33.54^\circ$$

Now,

(ii) Current in each branch.

$$i_1 = \frac{V}{Z_1} = \frac{240 \angle 0^\circ}{13 \angle 67.38^\circ} = 18.46 \angle -67.38^\circ$$

$$i_2 = \frac{V}{Z_2} = \frac{240 \angle 0^\circ}{19.198 \angle -33.54^\circ} = 12.5 \angle 33.54^\circ$$

vii Total current

$$\begin{aligned} i &= i_1 + i_2 \\ &= 18.46 \angle -67.38^\circ + 12.5 \angle 33.54^\circ \\ &= 20.23 \angle -30.04^\circ \text{A} \end{aligned}$$

viii Circuit phase angle

$$\begin{aligned} V &= 240 \angle 0^\circ \text{V} \\ I &= 20.23 \angle -30.04^\circ \text{A} \end{aligned}$$

Hence

current is lagging voltage by 30.04°

$$\phi = 30.04^\circ$$

ix) circuit impedance

$$\begin{aligned} Z_T &= \frac{Z_1 \times Z_2}{Z_1 + Z_2} \\ &= \frac{(13 \angle 67.38^\circ)(13.198 \angle -33.54^\circ)}{(13 \angle 67.38^\circ) + (13.198 \angle -33.54^\circ)} \\ &= 11.85 \angle 0.045^\circ \Omega \end{aligned}$$

5a)

It is very important to understand that what fraction of total apparent power is actually the active power as active power is required to perform useful work. This factor is known as power factor i.e. the ratio of true or active power to total or apparent power.

i.e.

$$\text{Power factor} = \frac{\text{Active Power } (P)}{\text{Apparent power } (S)} = \frac{VI \cos \phi}{VI} = \cos \phi$$

Cause of low power factor:

i) Almost 90% of industrial loads consist of induction machine which draw reactive component of current to produce magnetic field hence cause low power factor.

ii) Due to improper wiring or electrical failure power imbalance occurs which is also a cause of low power factor.

Numerical Part.

Ques

$$V = 240V$$

$$f = 50Hz$$

$$I = 20A$$

$$P = VI \cos \phi = 240 \times 20 \times 0.75 \\ = 3600 \text{ watt}$$

$$\omega = 2\pi f = 2\pi \times 50$$

$$P_f_1 = 0.75 \text{ (lagging)}$$

$$\cos \phi = 0.75$$

$$\phi = \cos^{-1}(0.75)$$

$$= 41.40^\circ$$

Now,

$$P_f_2 = 0.95 \text{ (lagging)}$$

$$\cos \phi_2 = 0.95$$

$$\phi_2 = \cos^{-1}(0.95) = 18.19^\circ$$

Then,

if C be the capacitance of capacitor connected in series then,

$$C = P_i \left(\tan \phi - \tan \phi_2 \right)$$

$$\frac{V^2}{W}$$

$$= \frac{3600 \left(\tan 41.40 + \tan 18.19 \right)}{240^2 \times 2\pi \times 50}$$

$$= \frac{3600 \times 0.55}{240^2 \times 2\pi \times 50}$$

$$= 1.094 \times 10^{-4}$$

$$= 1.094 \times 100 \times 10^{-6}$$

$$= 109.4 \times 10^{-6}$$

$$C = 109.4 \mu F$$

\Rightarrow Soln,

Branch 1

Since the first branch take a leading current it's contains a capacitive reactance X_C .

Then

$$V = (100 + j200) V$$

$$= 223.6 \angle 63.43^\circ V$$

Now,

$$Z_1 = \frac{V}{I} = \frac{223.6}{16} = 13.975 \Omega$$

Then

$$Z_1^2 = R_1^2 + X_C^2$$

$$X_C = \sqrt{(13.975)^2 - 5^2}$$

$$= 13.04 \Omega$$

$$Z_C = R - jX_C = 5 - j13.04$$

$$= 13.975 \angle -69^\circ$$

Then,

$$\begin{aligned} I_1 &= \frac{V}{Z_1} = \frac{223 \angle 63.43^\circ}{13.975 \angle -69^\circ} \\ &= 16 \angle 132.43^\circ A \end{aligned}$$

$$I = 16 \angle 132.43^\circ A$$

Branch 2,

Total power consumed in both the branches

$$P = I_1^2 R_2 + R_2^2 P_2$$

$$500 \text{ W} = 16^2 \times 5 + I_1^2 P_2$$

$$I_1^2 P_2 = 3720 \text{ W} \quad (\text{iii})$$

Since the power factor is lagging for branch 2,
 X_2 is + inductive

$$\cos \phi_2 = \frac{R_2}{Z_2}, \quad Z_2 = \frac{R_2}{\cos \phi_2} = \frac{R_2}{0.8} = 1.25 R_2$$

$$I_1 = \frac{V}{Z_2} = \frac{223.6}{1.25 R_2}$$

$$= 178.8 \text{ A} \quad (\text{iv})$$

 Eq^n (ii) \rightarrow eq^n (iii)

$$\frac{I_1^2 R_2}{I_2 R_2} = \frac{3720}{178.88}$$

$$\text{Then } R_2 = \frac{I_2 R_2}{I_1} = \frac{178.88}{20.796}$$

$$I_2 = 20.796 \text{ A}$$

$$= 8.60 \Omega$$

$$Z_2 = 1.25 R_2 = 1.25 \times 8.60$$

$$= 10.75 \Omega$$

Argin.

$$Z_2^2 = R_2^2 + X_2^2$$

$$X_2 = \sqrt{Z_2^2 - R_2^2}$$

$$= \sqrt{(10.75)^2 - (8.6)^2}$$

$$= 6.45 \Omega$$

$$Z_2 = R + j X_2$$

$$= 8.6 + j 6.45$$

$$= 10.75 \angle 36.87^\circ \Omega$$

$$\frac{I_2}{Z_2} = \frac{V}{Z_2} = \frac{223.6 \angle 63.43^\circ}{50.75 \angle 31.87^\circ}$$

$$I_2 = 20.8 \angle 26.56^\circ A$$

Finally,

$$\text{Total current } (I) = I_1 + I_2$$

$$= 16 \angle 132.43^\circ + 20.8 \angle 26.56^\circ$$


$$= 7.81 + 21.1j$$

$$= 22.5 \angle 69.69^\circ A$$

$$I = 22.5 \angle 69.69^\circ A$$

Ques

\Rightarrow Soln.

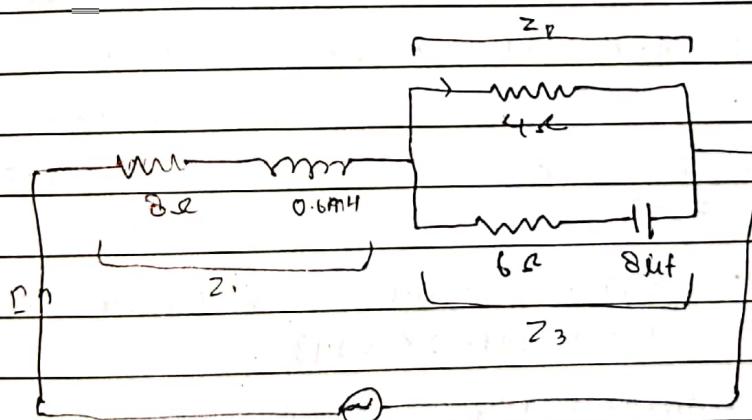

for Z_1

$$L = 0.6 \text{ mH.} = 0.6 \times 10^{-3} \text{ H}$$

$$X_L = 2\pi f L = 2\pi \times 50 \times 0.6 \times 10^{-3}$$

$$= 0.188$$

Then,

$$Z_1 = 8 + j0.188$$

$$= 8 \angle 1.34^\circ \Omega$$

$$Z_1 = 4 + j0$$

$$= 4 \angle 0^\circ$$

$$Z_2 = 6 - jX_1$$

$$= 6 - j1$$

$$2\pi 50 \times 10^{-3}$$

$$= 6 - j297.92$$

$$= 397.92 \angle -89.13^\circ \Omega$$

Then

$$Z_t = Z_1 + Z_2 \parallel Z_3$$

$$= Z_1 + Z_2 \times Z_3$$

$$Z_2 + Z_3$$

$$= 8 \angle 1.34^\circ + (4 \angle 0^\circ) \times (397.92 \angle -89.13^\circ)$$

$$(4 \angle 0^\circ) + (397.92 \angle -89.13^\circ)$$

$$= 18.34 \angle 0.70^\circ$$

Then,

$$I = \frac{V}{2\pi} = \frac{220 \angle 0^\circ}{18.34 \angle 0.70^\circ} = 18.34 \angle -0.70^\circ A$$

$$I = 18.34 \angle -0.70^\circ A$$

Again,

$$I_1 = \frac{Z_3}{Z_2 + Z_3} \cdot I$$

$$= \frac{397.92 \angle -89.13^\circ}{4 \angle 0^\circ + 397.92 \angle -89.13^\circ} \times 18.34 \angle -0.70^\circ$$

$$= 18.33 \angle -1.27^\circ$$

$$I_1 = 18.33 \angle -1.27^\circ$$

Finally,

$$\begin{aligned} I_2 &= I - I_1 = 18.34 \angle -0.70^\circ - 18.33 \angle -1.27^\circ \\ &= 0.18 \angle 85.87^\circ A \end{aligned}$$

$$I_2 = 0.18 \angle 85.87^\circ A$$

7.8.44

Soln:

$$Z_1 = 10 - j318 \cdot 31 = 320.81 \angle -82.83^\circ \Omega$$

$$Z_2 = 50 + j62.83 = 80.29 \angle 51.48^\circ$$

Then

$$\begin{aligned} Z_1 &= \frac{Z_1 \times Z_2}{Z_1 + Z_2} = \frac{(320.81 \angle -82.83^\circ) \times (80.29 \angle 51.48^\circ)}{(320.81 \angle -82.83^\circ) + (80.29 \angle 51.48^\circ)} \\ &= 70.65 + j0.14 \\ &= 70.65 \angle 0.14^\circ \end{aligned}$$

Then,

$$\text{ii) Current through } (I) = \frac{V}{Z_1} = \frac{100 \angle 0^\circ}{\cancel{95.08} \angle 39.23^\circ} = 1.05 \angle -39.23^\circ A$$

$$\begin{aligned} \text{iii) } S &= V \times I^* \\ &= 100 \angle 0^\circ \times (1.05 \angle -39.23^\circ)^* \\ &= 100 \angle 0^\circ \times (1.05 \angle 39.23^\circ) \\ &= 105 \angle 39.23^\circ \\ &= 81.33 + j66.40 \\ &= P + jQ \end{aligned}$$

$$\text{Active power } (P) = 81.33 \text{ W}$$

$$\text{Reactive power } (Q) = 66.40 \text{ VAk}$$

$$\text{Apparent power } (S) = 105 \text{ VA}$$

Q8.54 \Rightarrow Soln,

The effect of low power factor are as follows.

- i) Low power factor for given voltage & given active power requirement of load cause higher current to flow in the circuit requiring higher rating protective device such as fuse, relay etc.
- ii) Higher flow of current in the circuit leads to the higher heat loss internally of copper loss in the system thus reducing the overall transmission efficiency.
- iii) Due to high exchange of reactive power the system, larger voltage drop is observed which makes voltage quality poor.

 \Rightarrow Soln,

$$P_L = 7 \text{ kW}$$

$$P_f = 0.7$$

$$\cos \phi_1 = 0.7$$

$$\phi_1 = 45.57^\circ$$

$$P_f_2 = 0.9$$

$$\cos \phi_2 = 0.9$$

$$\phi_2 = 25.84^\circ$$


Then $\angle \theta_2 = \phi_1$

$$\begin{aligned} Q_2 &= P_1 (\tan \phi_1 - \tan \phi_2) \\ &= I (\tan 45.57^\circ - \tan 25.84^\circ) \\ &= I \times 0.535 \end{aligned}$$

$$Q_2 = 3.745 \text{ kVAR}$$

gbsq)

\Rightarrow Soln,

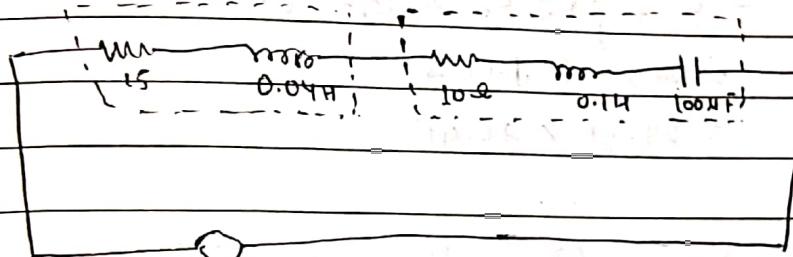

$$V = 230V$$

$$f = 50\text{Hz}$$

for Z_1 ,

$$R_1 = 15 \Omega$$

$$L_1 = 0.04H$$

$$X_L = 2\pi f X_L = 2\pi \times 50 \times 0.04 = 12.56 \Omega$$

$$Z_1 = R_1 + jX_L$$

$$= 15 + j12.56 \Omega = 19.56 \angle 39.94^\circ \Omega$$

for Z_2

$$R_2 = 10 \Omega$$

$$L_2 = 0.1H$$

$$\begin{aligned} X_L &= 2\pi f L_2 = 2\pi \times 50 \times 0.1 \\ &= 31.416 \Omega \end{aligned}$$

$$C = 100 \mu F = 100 \times 10^{-6} \text{ F}$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 160 \times 10^{-9}} \\ = 31.83 \Omega$$

Then

$$Z_2 = R_2 + jX_L - jX_C \\ = 10 + j31.416 - j31.83 \\ = 10 - j0.414 \\ = 10.00 \angle -2.37^\circ \Omega$$

Then

$$Z_T = Z_1 + Z_2 \\ = 15 + j12.56 + 10 - j0.414 \\ = 25 + j12.146 \angle \\ = 27.91 \angle 26.41^\circ$$

again.

$$\text{i) current drawn } (I) = \frac{V}{Z_T} = \frac{230 \angle 0}{27.91 \angle 26.41} \\ = 8.24 \angle -26.41$$

$$\text{ii) voltage across } Z_1 (V_1) = I \cdot Z_1 \\ = (8.24 \angle -26.41) \times (19.56 \angle 39.94) \\ = 163.627 \angle 13.53^\circ V.$$

$$\text{iii) voltage across } Z_2 (V_2) = I \cdot Z_2 \\ = (8.24 \angle -26.41) (10 \angle -2.37) \\ = 82.4 \angle -28.83 V.$$

(iv) Now

$$V = 230 \angle 0$$


$$I = 8.24 \angle -26.41$$

current lags voltage by 26.41°

phase angle (ϕ) = 26.41°

$$\begin{aligned}
 \text{Total power factor} &= \cos \phi \\
 &= \cos (26.41) \\
 &= 0.895 \text{ (1ugg)}
 \end{aligned}$$



v) Phasor diagram

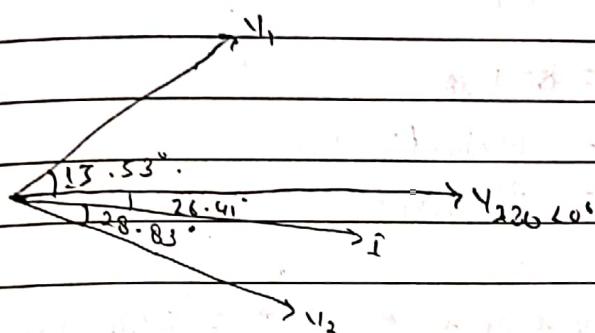

Ans Aashad

4.b

Q.

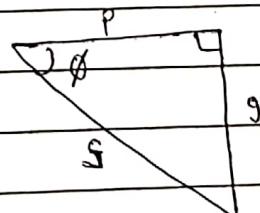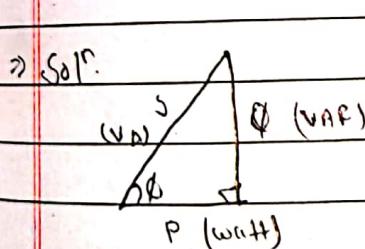

Load A

$$S_1 = 250 \text{ kVA}$$

$$\cos \phi = 0.8$$

$$\phi = 36.86^\circ$$

Load B

$$P_2 = 20 \text{ kW}$$

$$\cos \phi = 1$$

$$\phi = 0^\circ$$

$$S_2 = \frac{P}{\cos \phi} = 20 \text{ kVA}$$

$$P_1 = S \times \cos \phi$$

$$= 250 \times 0.8$$

$$= 200 \text{ kW}$$

$$Q_2 = P \tan \phi = 20 \times \tan(0)$$

$$= 0$$

Load c.

$$P_3 = 48 \text{ kW}$$

$$\cos \phi = 0.6$$

$$\phi = \cos^{-1}(0.6)$$

$$= 53.13^\circ$$

$$S_3 = \frac{P}{\cos \phi} = \frac{48}{0.6}$$

$$= 80 \text{ kVA}$$

$$Q_3 = P \cdot \tan \phi = 48 \times \tan(53.13^\circ) \\ = 84 \text{ kVAR}$$

$$\text{i) total kW} = 200 + 20 + 48 = 268 \text{ kW (P)}$$

$$\text{ii) total kVAR} = 150 + 0 + 84 = 234 \text{ kVAR (Q)}$$

$$\text{iii) total kVA.} = 250 + 20 + 80 = 350 \text{ kVA (S)}$$


$$\text{iv) Overall power factor} = \frac{P}{S} = \frac{268}{350} = 0.765$$

2070 AshadQ. 3.C

⇒ Soln.

$$Z_1 = 3 - 4j$$

$$Z_2 = 8 + 6j$$

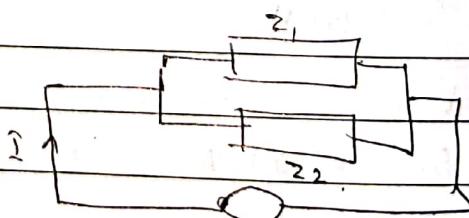

& Current $I = 25 \text{ A}$ with no phase diff.

$$\phi = 0^\circ$$

$$I = 25 < 0^\circ$$

Then

$$Z_T = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2}$$

$$= \frac{(3 - 4j) \times (8 + 6j)}{(3 - 4j) + (8 + 6j)}$$

$$= 4 - 2j$$

$$= 4.47 \angle -26.56^\circ$$

since they are parallel to each other.

$$\vec{V}_1 = \vec{V}_2 = \vec{i} \cdot \vec{z}$$

$$= (25 \angle 0^\circ) (4.47 \angle -26.56^\circ)$$

$$= 111.75 \angle -26.56^\circ$$

Then

$$\text{Active power } (P) = V_i i \cos \phi$$

$$= 111.75 \times 25 \times \cos(26.56^\circ)$$

$$= 2500 \text{ Watts}$$

2060 B.G.S.H.U.L

12 - 4.1 A

Q

Ans,

$$\vec{V} = 100 \angle 0^\circ \text{ V}$$

$$\vec{V}_{21} = 40 \angle -30^\circ \text{ V}$$

Simp they are in series

$$\vec{V}_{21} = \vec{V}_1 + \vec{V}_2$$

$$= 100 \angle 0^\circ + 40 \angle -30^\circ$$

$$= 68.35 \angle 17.01^\circ$$

$$\vec{V}_{21} = 68.35 \angle 17.01^\circ \text{ V}$$

Now

$$I = \frac{\vec{V}_{21}}{\vec{Z}_1} = \frac{68.35 \angle 17.01^\circ}{20 \angle 30^\circ}$$

$$= 3.458 \angle -12.93^\circ \text{ A}$$

Finally.

$$Z_1 = \frac{V_{21}}{I} = \frac{11.0 \angle -30^\circ}{3.910 \angle -12.93^\circ}$$


$$= 11.187 \angle -3.43^\circ$$

$$\underline{Z}_1 = 11.76 \angle -17.045^\circ$$

2072 Mugh
Q 4.

Q 1. \Rightarrow Sol'n.

$$Z_1 = 10 + j15$$

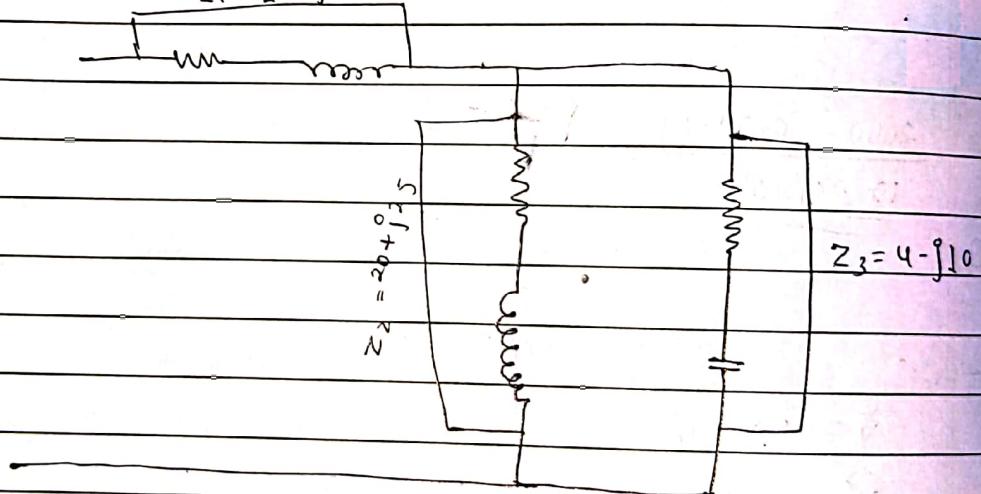

Here,

let Z_T be the equivalent impedance

$$Z_1 = 10 + j15$$

$$Z_2 = 20 + j12.5$$

$$Z_3 = 4 - j10$$

then,

$$Z_T = Z_1 + Z_2 // Z_3$$

$$= (10 + j15) + \frac{(20 + j12.5) \times (4 - j10)}{(20 + j12.5) + (4 - j10)}$$

$$= 10 + j15 + \frac{330 - 100j}{24 + j5j}$$

$$= 18.014 + j5.823$$


$$Z_T = 18.014 + j5.823 \Omega$$

206g chaitra

54

8

3 soln,

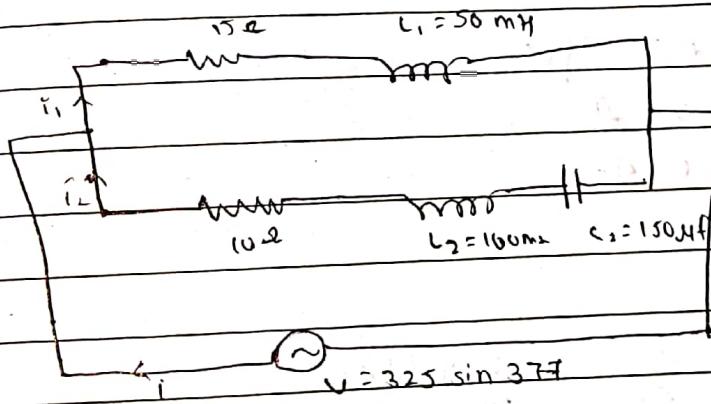

$$\text{voltage } (v) = 325 \sin 377t$$

comparing with $v = V_m \sin(\omega t + \phi)$

$$V_m = 325$$

$$\omega = 377$$

$$\phi = 0^\circ$$

$$R_{rms} \text{ voltage } (V_{rms}) = \frac{V_m}{\sqrt{2}} = \frac{325}{\sqrt{2}} = 229.01 \text{ V}$$

$$Z_1 = R_1 + jX_L$$

$$= 10 + j377$$

$$w_L = 377 \times 50 \times 10^{-3}$$

$$= 1.885 \Omega$$

$$Z_1 = 15 + j18.85 \Omega$$

$$Z_1 = 24.089 \angle 51.48^\circ$$

Then,

$$Z_2 = R_2 + jX_L - jX_C$$

$$R_2 = 10 \Omega$$

$$L = 150 \text{ mH}$$

$$= 150 \times 10^{-3}$$

$$L = 100 \text{ mH}$$

$$= 100 \times 10^{-3}$$

$$= 1.5 \times 10^{-4} \text{ F}$$

$$V_L = 2\pi f L$$

$$= \omega L$$

$$= 3.14 \times 100 \times 10^{-3}$$

$$= 37.7 \Omega$$

Then,

$$X_C = \frac{1}{\omega C}$$

$$= \frac{1}{377 \times 1.5 \times 10^{-4}}$$

Then

$$Z_2 = 10 + j37.7 - j17.68$$

$$= 10 + 20.02 j \Omega$$

$$= 22.37 \angle 63.45^\circ$$

i) For path 1

$$\text{current } (i) = \frac{V}{Z_1} = \frac{229.81 \angle 0^\circ}{24.089 \angle 51.48^\circ}$$

$$= 9.54 \angle -51.48^\circ$$

$$\text{power factor} = \cos \phi = \cos (51.48^\circ)$$

$$= 0.622 (\text{lagging})$$

$$\text{Active power } (P) = VI \cos \phi$$

$$= 229.81 \times 9.54 \times 0.622$$

$$= 1363.66 \text{ WATT}$$

(ii) For path 2

current through path 2

$$i_2 = \frac{V}{Z_2} = \frac{229.81}{22.37 + j63.45}$$

$$= 10.27 \angle -63.45^\circ$$

$$\text{Power factor} = \cos \phi_2$$

$$= \cos(63.45)$$

$$= 0.44 \text{ (lagging)}$$

$$\text{Reactive power (Q)} = V i_2 \sin \phi$$

$$= 229.81 \times 10.27 \times \sin(63.45)$$

$$= 1038.46 \text{ VAR}$$

(iii) For whole circuit.

$$I = i_1 - i_2$$

$$= 9.54 \angle -51.18^\circ + 10.27 \angle -63.45^\circ$$

$$I = 19.70 \angle -57.68^\circ$$

power factor of whole circuit

$$= \cos \phi$$

$$= \cos(57.68)$$

$$= 0.534 \text{ (lag)}$$