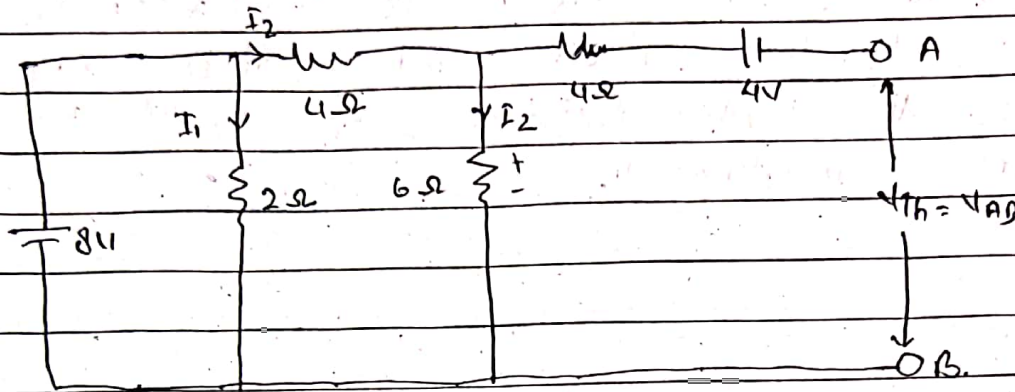


DC Portion

Q.N.2) Soln, In order to determine power transfer, to find V_{th} ;



$$V_{th} = V_{AB} = V_A - V_B$$


$$= 6I_2 - 4 \times 0 - 4$$

$$= 6 \times \frac{8}{4+6} - 4$$

$$= 0.8V$$

$$[\therefore I_2 = \frac{8}{4+6} = \frac{8}{10} A]$$

To find R_{th} :

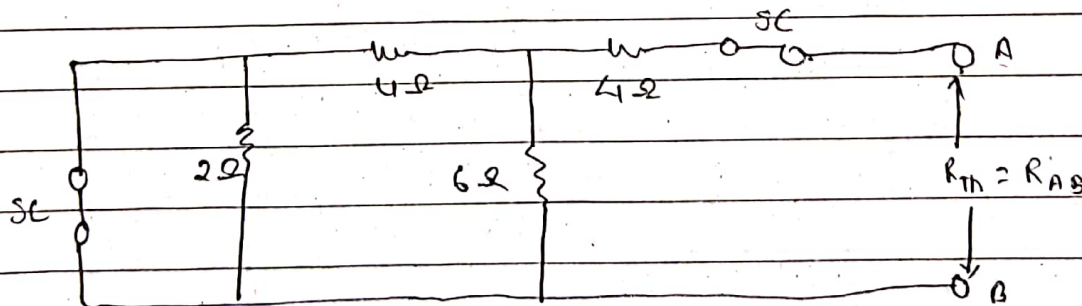

$$R_{th} = R_{AB}$$

$$= (4 \parallel 6) + 4$$

$$= \frac{4 \times 6}{4+6} + 4$$

$$= 6.4 \Omega$$


\therefore A) per the maximum power transfer theorem

$$R_{th} = R_L = 6.4 \Omega$$

⇒

Maximum power transfer theorem states that "the DC voltage source will deliver maximum power to the variable load resistor only when the load resistance is equal to the source resistance".

Q.3

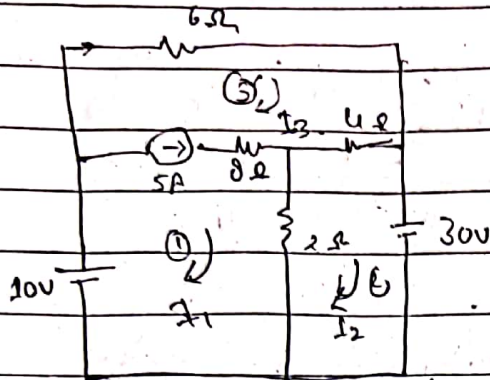Solⁿ,Mesh I & mesh III we get, $I_1 - I_3 = 5A$ (i)

Applying KVL on super mesh I & III, we get

$$10 - 6I_3 - 4(I_3 - I_2) - 2(I_1 - I_2) = 0$$

$$10 - 6I_3 - 4I_3 + 4I_2 - 2I_1 + 2I_2 = 0$$

$$-2I_1 + 6I_2 - 10I_3 = -10 \quad \text{(ii)}$$

Applying KVL on mesh II we get.

$$-30 - 2(I_2 - I_1) - 4(I_2 - I_3) = 0$$

$$-30 - 2I_2 + 2I_1 - 4I_2 + 4I_3 = 0$$

$$2I_1 - 6I_2 + 4I_3 = 30 \quad \text{(iii)}$$

Solve eqⁿ (i), (ii) & (iii) we get

$$I_1 = \frac{5}{3} A = 1.667 A$$

$$I_2 = -\frac{20}{3} A = -6.667 A$$

$$I_3 = -\frac{10}{3} A = -3.33 A$$

Now,


~~current in~~

$$\begin{aligned} \text{current in branch containing } 4 \Omega \text{ resistor} \\ &= 6.667 - 3.33 \\ &= 3.334 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{current in branch containing } 2 \Omega \text{ resistor} \\ &= 1.667 + 6.667 \\ &= 8.334 \text{ A} \end{aligned}$$

Q.N.4)

Here w^l 1st when connected to series

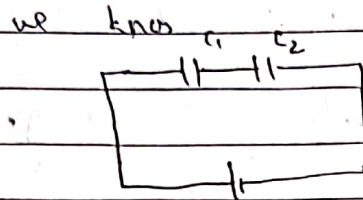


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{0.025} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$40 = \frac{C_1 + C_2}{C_1 C_2} \quad \text{--- (i)}$$

Again In case of parallel

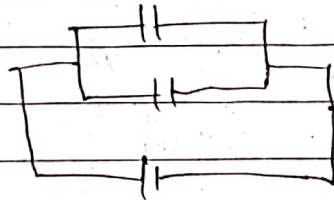

$$0.15 = C_1 + C_2$$

$$C_1 = (0.15 - C_2) \quad \text{--- (ii)}$$

putting the value of C_1 in eq (i) we get

$$40 = \frac{(0.15 - C_2) + C_2}{(0.15 - C_2) C_2}$$

$$9 \quad 40 = \frac{0.15 - C_2 + C_2^2}{0.15 C_2 - C_2^2}$$

$$6C_2 - 40C_2^2 = 0.15$$

$$40C_2^2 - 6C_2 + 0.15 = 0$$

Solving above quadratic eqⁿ we get

$$C_2 = 0.031 \mu\text{f} \quad \text{or, } 0.1183 \mu\text{f}$$

when,

$$C_2 = 0.031 \mu\text{f}$$

$$C_1 = 0.15 - C_2 \\ = 0.118 \mu\text{f}$$

when

$$C_2 = 0.118 \mu\text{f}$$

$$C_1 = 0.031 \mu\text{f} \quad \#$$

\therefore The capacitance of each capacitor is $0.118 \mu\text{f}$ & $0.031 \mu\text{f}$