

Chapter 2.2 Intel 8255A (Contd...)

Example 3

Figure (on the right) shows an interfacing circuit using the 8255A in Mode 1. Port A is designated as the input port for a keyboard with interrupt I/O and port B is designated as the output port for a printer with status check I/O.

- Find port addresses by analyzing the decode logic.
- Determine the control word to set up port A as input and port B as output in Mode 1.
- Determine the BSR word to enable $INTE_A$.
- Determine the masking byte to verify the OBF_B line in status check I/O.
- Write subroutine to accept character from keyboard and send character to printer.

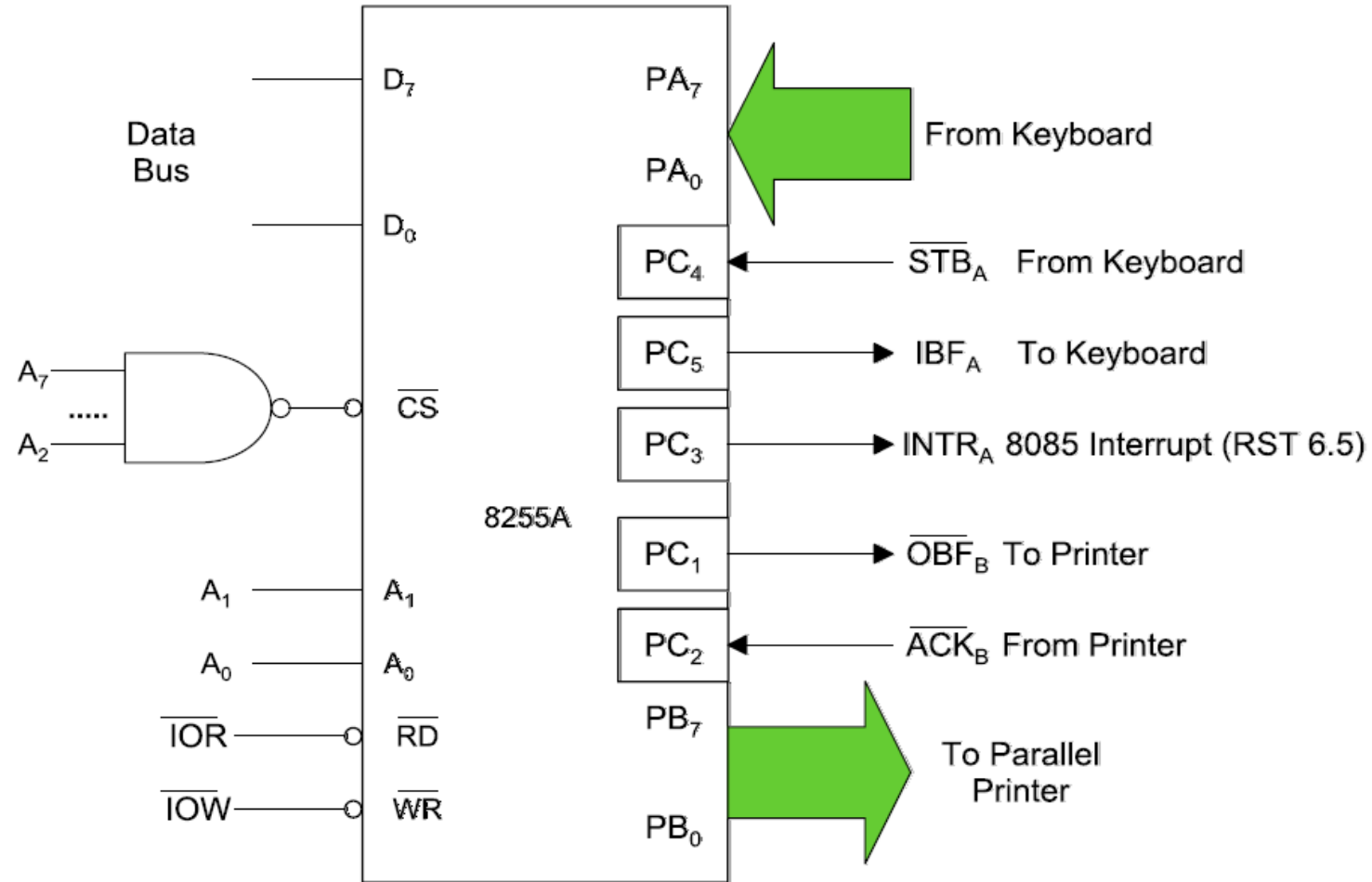


Fig: 8255A Mode 1 Example

Chapter 2.2 Intel 8255A (Contd...)

Solution

- a) The 8255A is connected as I/O mapped I/O. When the address lines A7-A2 are all 1, the output of NAND gate goes low and selects 8255A. The port addresses are calculated as 1111 11XX:

Port A = 1111 1100 (FCH)

Port B = 1111 1101 (FDH)

Port C = 1111 1110 (FEH)

Control Register = 1111 1111 (FFH)

- b) Control word to set up port A as input and port B as output Mode 1 is:

D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	
1	0	1	1	X	1	0	X	= B4H

- c) BSR word to set INTE_A

D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	
0	0	0	0	1	0	0	1	= 09H

- d) Status word to check OBF_B'

D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	
X	X	X	X	X	X	OBF _B '	X	Masking Byte = 02H

Chapter 2.2 Intel 8255A (Contd...)

e) Subroutines to accept character from keyboard and send to printer:

MVI A, B4H ; Initialize control word	PRINT:	
OUT FFH ; Using I/O Mode	IN FEH ; Read port C	
MVI A, 09H ; Set INTE _A (PC ₄)	ANI 02H ; Check OBF _B ' (D ₁)	
OUT FFH ; Using BSR Mode	JZ PRINT	
EI ; Enable Interrupt	MOV A, C ; Get Character	
CALL READ ; Read Character	OUT FDH ; Send Character to port B	
CALL PRINT ; Display Character	RET	
HLT ; Terminate Program		

READ: ; Keyboard Read Subroutine

IN FEH ; Read Port C	
ANI 20H ; Check IBF _A (PC ₅)	
JZ READ	
IN FCH ; Read ASCII code of character	
MOV C, A ; Save Character	
RET	

Chapter 2.2 Intel 8255A (Contd...)

Programming in Mode 2 (Strobe Bidirectional Bus I/O)

- When the 8255 is operated in Mode 2
 - Port A can be used as a bidirectional 8-bit I/O bus using PC₃–PC₇ for handshaking
 - Port B can be programmed only in Mode 0 (PC₀–PC₂ as Input or Output), or in Mode 1 (with PC₀–PC₂ for handshaking).
- Interrupts are generated for both output and input operations on the same INTR_A(PC₃) line.
- The control signal definitions for Mode 2 are:
- **Output Control Signals**
 - **OB_F (Output Buffer Full)** : This is an active low output which indicates that the CPU has written data into Port A.
 - **ACK (Acknowledge)** : This is an active low input signal (generated by the peripheral) which enables the tri-state output buffer or Port A and makes Port A data available to the peripheral. In Mode 2, Port A outputs are in tri-state until enabled.
 - **INTE 1** : This is the flip-flop associated with Output Buffer Full. INTE 1 can be used to enable to disable the interrupt by setting or resetting PC₆ in the BSR Mode.
- **Input Control Signals**
 - **STB(Strobe Input)** : This is an active low input signal which enables Port A to latch the data available as its input.
 - **IBF (Input Buffer Full Flip-Flop)** : This is an active high output which indicates that data has been loaded into the input latch of Port A.
 - **INTE 2** : This is an Interrupt enable flip-flop associated with Input Buffer Full. It can be controlled by setting or resetting PC₄ in the BSR Mode.

Chapter 2.2 Intel 8255A (Contd...)

Programming in Mode 2 (Strobe Bidirectional Bus I/O) (Contd...)

- **Status Word in Mode 2**
- The status word for Mode 2 (accessed by reading Port C) is shown in above figure. D_7 – D_3 of the status word carry information about \overline{OBF} , $INTE_1$, IBF_A , $INTE_2$, and $INTR_A$. The status of the bits D_2 – D_0 depend on the mode setting of Group B. If B is programmed in Mode 0, D_2 – D_0 carry information about the control signals for B, depending upon whether B is an Input port or Output port respectively.

Chapter 2.2 Intel 8255A (Contd...)

Programming in Mode 2 (Strobe Bidirectional Bus I/O) (Contd...)

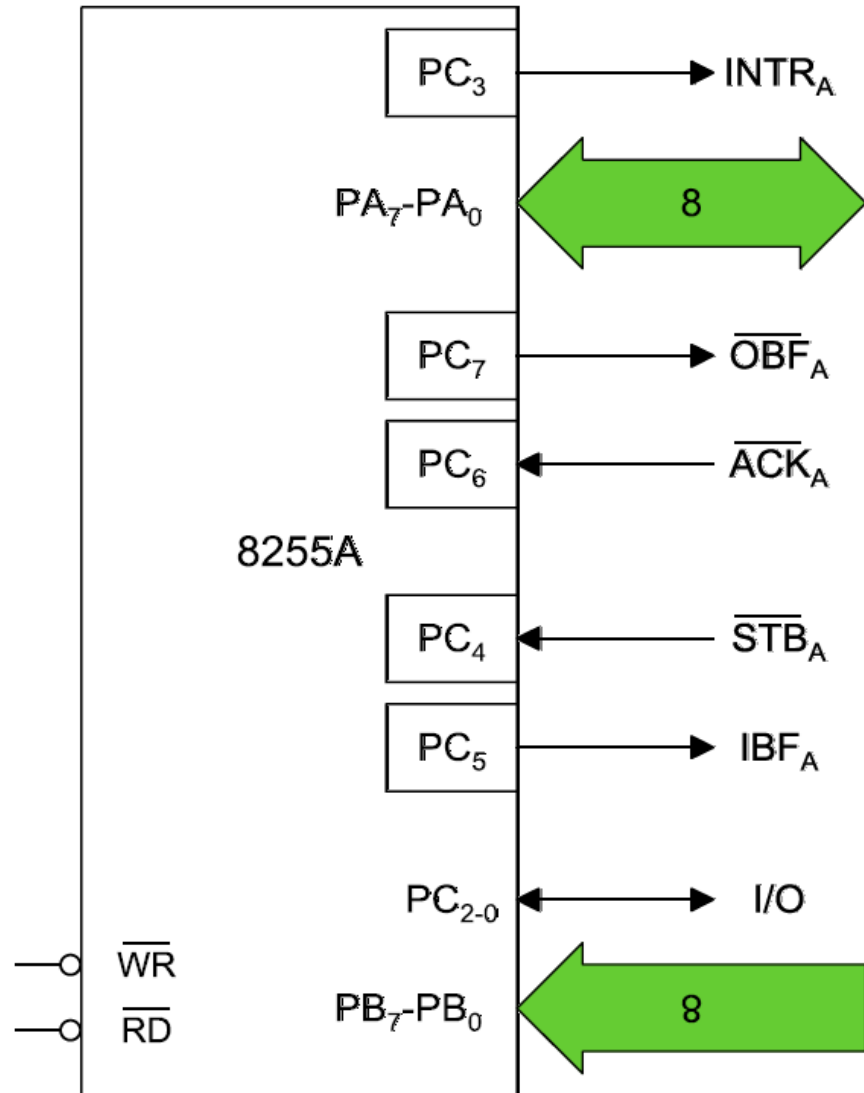


Fig: 8255A Mode 2 and Mode 0 Input Configuration

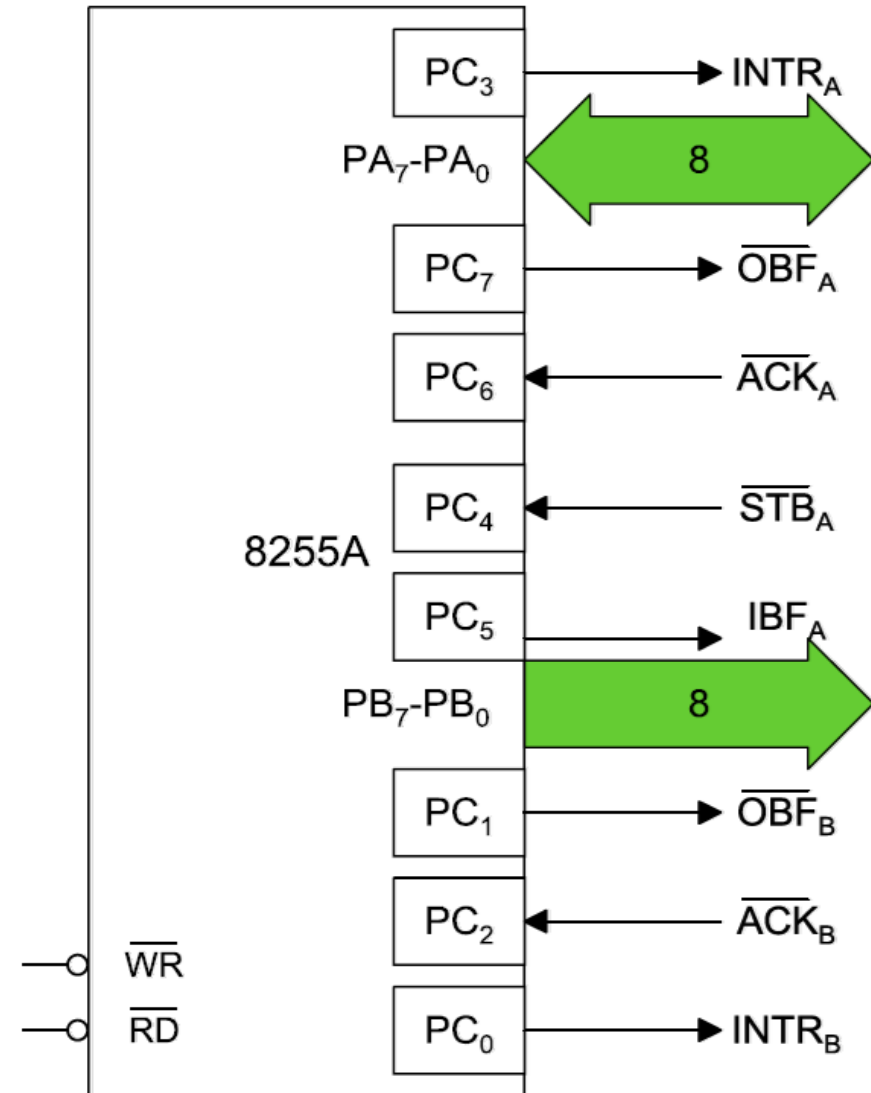


Fig: 8255A Mode 2 and Mode 1 Output Configuration

Chapter 2.2 Intel 8255A (Contd...)

Programming in Mode 2 (Strobe Bidirectional Bus I/O) (Contd...)

 


Fig: Control Word - Mode 2 and Mode 1 Output Configuration

Fig: Control Word - Mode 2 and Mode 0 Input Configuration

 


Fig: Status Word - Mode 2 Configuration

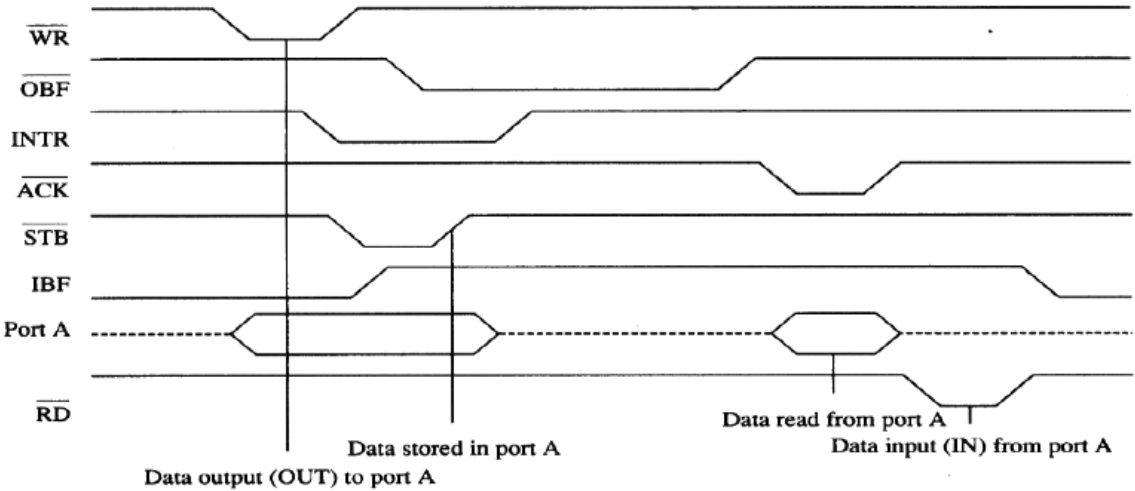


Fig: Timing Waveform for Mode 2 Configuration

EXAMPLE:

2. Design an interfacing circuit to set-up bidirectional data communication in the master-slave format between two 8085A microcomputers. Use the 8255A as the interfacing device between the master and the slave microcomputers. Write necessary program to transfer a block of data from the master to the slave.

Solution:

The block diagram shows two bidirectional data buses interconnected through the 8255A, which serves as a peripheral device of the master MPU. Port A of 8255A is used for bidirectional data transfer and five signals from Port C are used for handshaking. When the master MPU writes a data byte in the 8255A, the OBF' signal goes low to inform the slave that a byte of data is available, and the slave acknowledges when it reads the byte.


Similarly, two other handshake signals are used when the slave transfers a data byte to the master. The master requires I/O ports to read and write data and check the status of the handshake signals. Similarly, the slave MPU required I/O ports to perform read and write operations. For this example, let's suppose that both MPUs are set up under the status check mode.

According to assumed decode logic, the addresses of individual ports are selected as:

1. Port A = FCH ($A_1 = 0, A_0 = 0$)
2. Port B = FDH ($A_1 = 0, A_0 = 1$)
3. Port C = FEH ($A_1 = 1, A_0 = 0$)
4. Control Register = FFH ($A_1 = 1, A_0 = 1$)

Control word can be expressed as:

D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
1	1	X	X	X	1/0	1/0	1/0

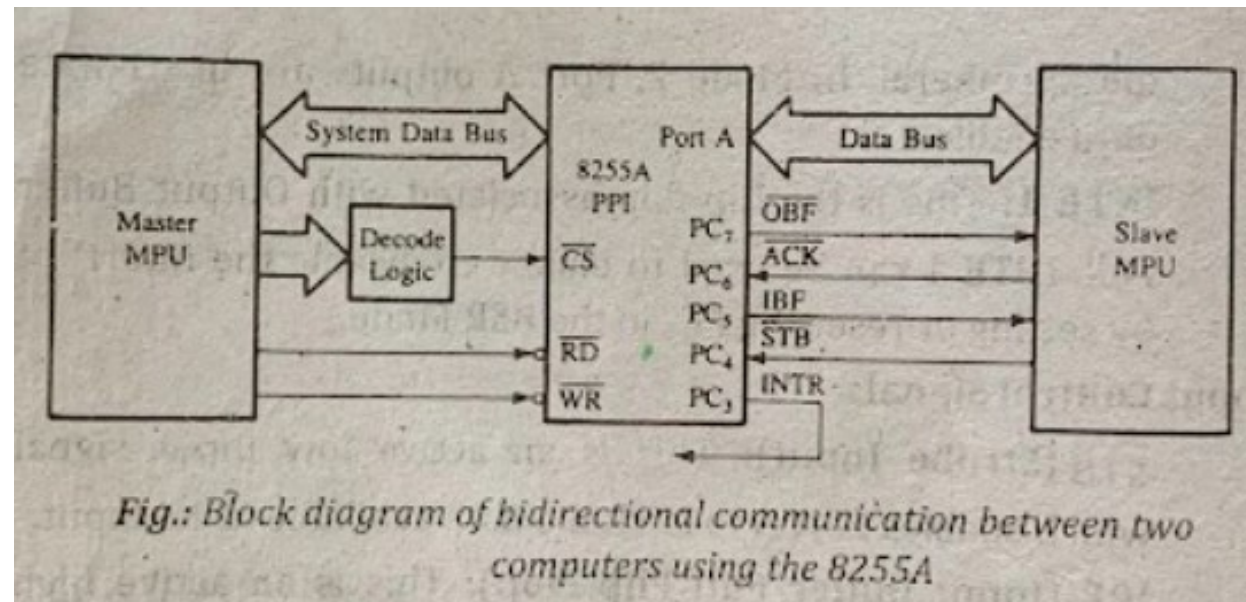

Data transfer from master MPU to slave MPU:

1. The master MPU reads the status of OBF' to verify whether the previous byte has been read by the slave MPU.
2. The master writes data into Port A and the 8255A informs the slave by causing the signal OBF' to go low.
3. The slave checks OBF' signal from the master for data availability.
4. The slave MPU reads data from Port A and acknowledges the reading at the same time by making the signal ACK' low.

Data transfer from slave MPU to master MPU:

1. The slave MPU checks the handshake signal IBF to find out whether Port A is available (i.e. empty) to transfer a data byte.
2. The slave MPU place a data byte on the data bus and informs 8255A by enabling the STB' signal.
3. The 8255A causes the IBF to go high, and the master MPU reads the signal to find out whether a data byte is available.
4. Master MPU reads the data byte.

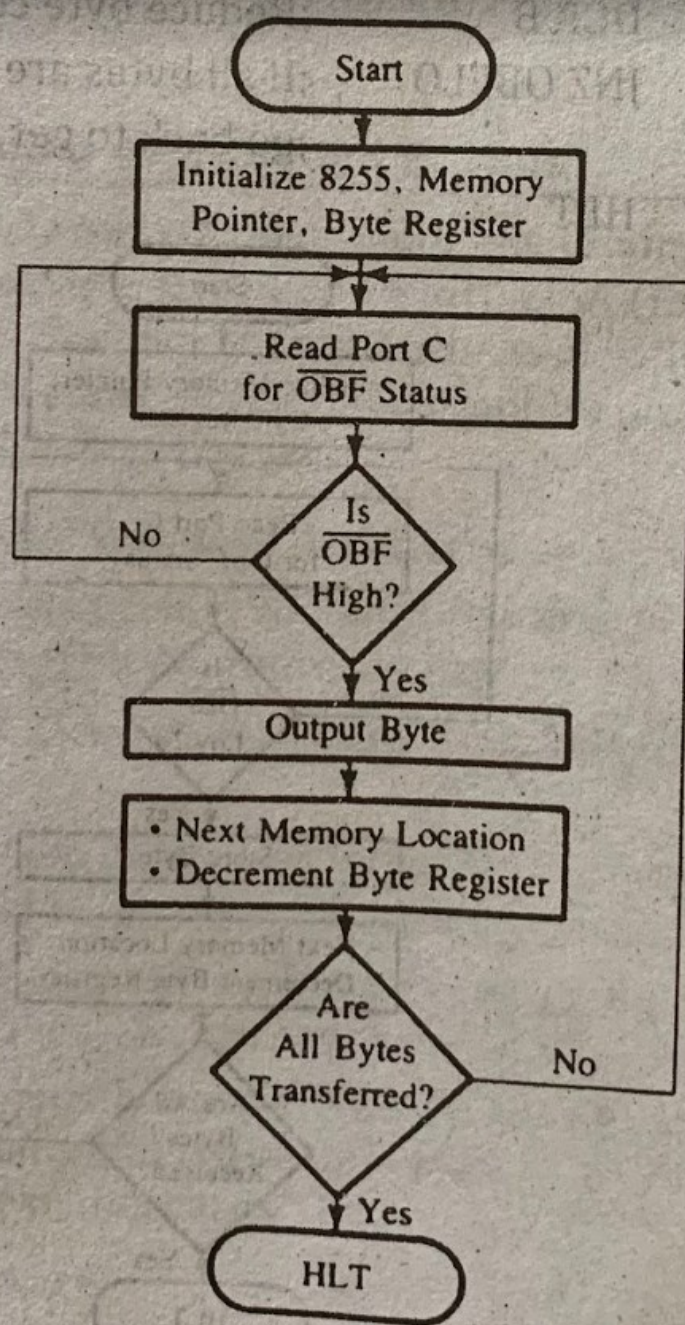


Fig.: Flowchart of Master program

Master Program

LXI SP, STACK1

LXI H, MASTER ; Memory pointer for data

MVI B, BYTES ; No. of bytes to be sent

MVI A, CTRL ; Control word

OUT FFH ; Initialize 8255A

OBFLO:IN FEH; Read Port C for status

RAL ;Place OBF' status in CY

JNC OBFLO ;If OBF' is low, wait

MOV A, M ;Get byte

OUT FCH ;Sent byte to Port A

INX H ;Next memory location

DCR B ;Reduce byte count by 1

JNZ OBFLO ; If all bytes are not
;transferred, to back to get next byte

HLT

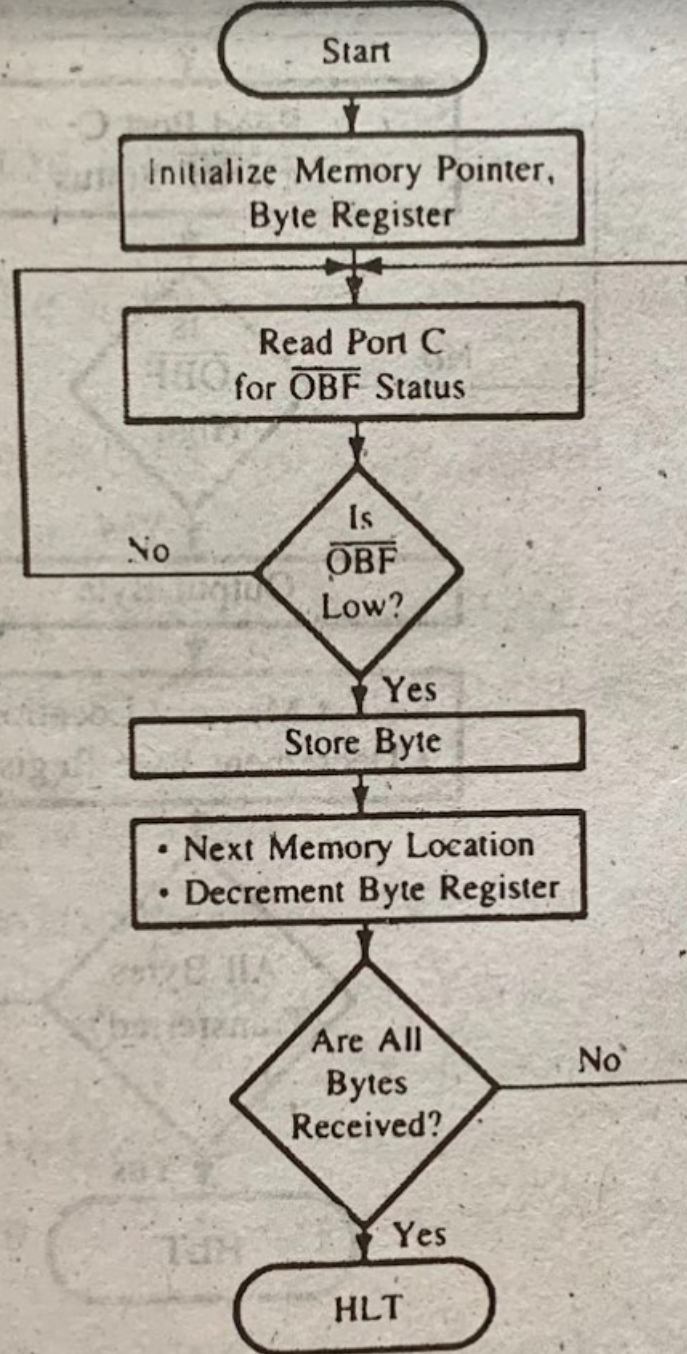


Fig.: Flowchart of Slave program

Slave Program

LXI SP, STACK1

LXI H, SLAVE ; Memory pointer for destination data

MVI B, BYTES ; No. of bytes to be received

OBFHI: IN FEH; Read Port C for OBF'

RAL ;Place OBF' (in D₇) status in CY

JC OBFHI ;If OBF' is high, wait

IN FCH ;Read byte

MOV M, A ;Store data

INX H ;Next memory location

DCR B ;Reduce byte count by 1

JNZ OBFHI ; If all bytes are not received, to back to ;get next byte

HLT

Chapter 2.3 Parallel Interfacing with ISA and PCI bus


I/O buses are used to connect the system bus (address, data, and control buses) for example ISA (8 or 16 bit), EISA (Extended ISA - 32 bit), VESA (Video Electronics Standards Association) local bus (VL Bus), PCI (32 or 64 bit), Accelerated graphics port (AGP), PCI-X (64 bit, 133MHZ), PCI-Express etc.

- **ISA Bus (Industry Standard Architecture)**
- First introduced in 1982 with the first PC (IBM/PC) – [Intel 8088 8 bit microprocessor].
- Originally ISA bus was with 8-bit bus which runs at 4.77 MHz.
- 16 bit version of ISA was introduced in 1984 used with Intl 80286 (16-bit microprocessor).
- Peripheral devices such as sound cards, disk drives, network cards etc. are connected via ISA slots.
- ISA bus is mostly obsolete for PC nowadays, but is still used in many industrial applications due to their low costs and existing cards.

Chapter 2.3 Parallel Interfacing with ISA and PCI bus

• 8-bit ISA bus Architecture

- Has data bus width of 8 bits and address bus width of 20 bits.
- Number of pins in ISA slots/cards are 62.
- Clock frequency of 4.77 MHz.
- ISA bus connector contains:
 - 20 bit address bus ($A_{19}-A_0$)
 - 8 bit data bus
 - MEMR', MEMW', IOR', IOW' control signal for controlling I/O or memory on the ISA card.
 - Interrupt request lines IRQ_2-IRQ_7
 - DMA request inputs DRQ_1-DRQ_3
 - DMA acknowledgement O/Ps $DACK_0'-DACK_3'$
 - Clock signals
 - Power lines and Reset

 

Chapter 2.3 Parallel Interfacing with ISA and PCI bus

- **16-bit ISA bus Architecture**

- Data bus width of 16 bit and address bus width of 24 bits.
- Number of pins in ISA card/slot are 98
- Clock frequency of 8.33 MHz
- Consists of an extra connector with 36 pins behind the 8-bit connector.
- Compatible with both 8-bit and 16-bit ISA cards.
- 16-bit card consists of two edge connectors
 - One plugs into the original 8-bit connector
 - Other plugs into the new 16-bit connector
- Extra connector consists of
 - 4 additional address lines – 24 lines in total
 - 8 additional data lines – 16 lines in total
 - 4-bit DMA channel request and acknowledgement lines
 - Additional Interrupt lines
 - Control lines to select 8 or 16 bit transfer

Chapter 2.3 Parallel Interfacing with ISA and PCI bus

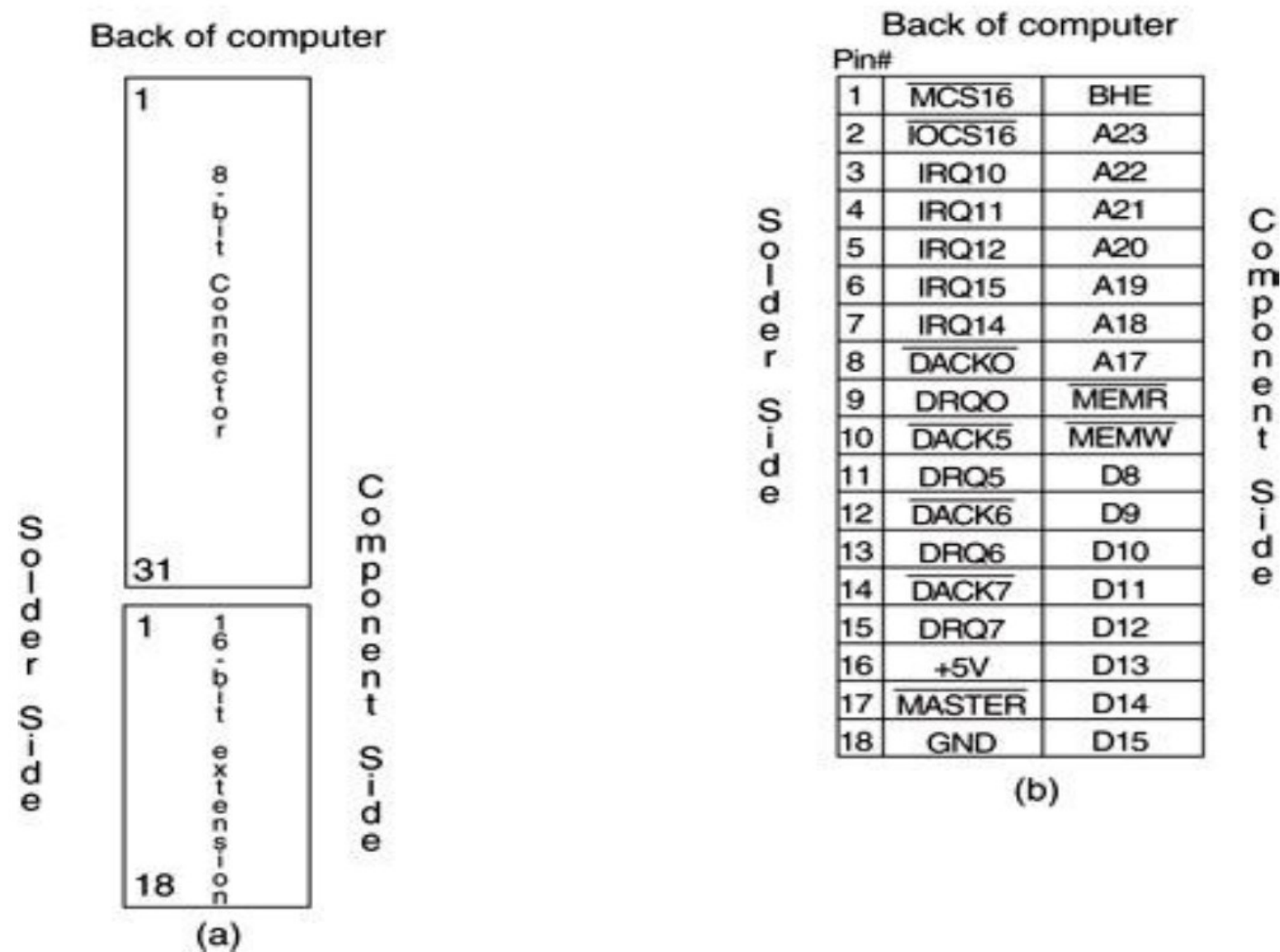


Fig: The 16-bit ISA bus. (a) Both 8- and 16-bit connectors and (b) the pinout of the 16-bit connector.

Chapter 2.3 Parallel Interfacing with ISA and PCI bus

- **Reasons for elimination of ISA Bus**

- ISA bus is slow, hard to use and bulky.
- Once each ISA slot/card uses dedicated interrupt lines, only limited number of cards can be used.
- Since address lines of 24 bits, a maximum of $2^{24}=16$ MB of RAM can only be accessed for DMA.
- Since data bus size is 16 bits only, higher bits data (32-bits) communication would reduce system performance.
- ISA cards do not have plug and play (PnP) technology i.e. they can't be configured automatically by BIOS or operating system.
- ISA cards must be controlled manually by setting the I/O addresses, interrupts and clock speed using jumpers and switches on the card itself.


- **Improvements in ISA bus**

- EISA (Extended ISA) of 32-bits, 8 MHz; now obsolete
- ISA PnP for plug and play; now obsolete
- VL-Bus of 32-bits operated at the speed of local bus (CPU)
- Used only for graphics cards
- Possibility of interference with the performance of the CPU

Chapter 2.3 Parallel Interfacing with ISA and PCI bus

- **PCI Bus (Peripheral Component Interconnect)**
 - Introduced in 1990 by Intel
 - Provides direct access to the CPU and system memory but uses a bridge to connect to the system bus to eliminate the potential for interference with CPU.
 - PCI bus is independent of processor type or speed
 - Originally operated at 33 MHz using 32-bit data lines
 - Revised standard at 66 MHz using 64-bit data lines
 - The 32-bit PCI connector has 124 pins and 64-bit PCI connector has 188 pins
 - The PCI bus is able to work with so few pins because of hardware multiplexing i.e. the device sends more than one signal over a single pin
 - Also, PCI supports devices that use 5v signalling voltage levels
 - PCI card support plug and play (PnP) feature i.e. PCI devices are automatically recognized and configured to work in system.
- **Advancement in PCI bus**
 - PCI-X (PCI extended): runs at 133 MHz, 32-bit and 1.06 GBps data rate
 - PCI-E (PCI express): replaced PCI, PCI-X & AGP standards
 - The microprocessor connects to the PCI bus through an IC called a PCI bridge
 - Virtually any processor can interface to PCI with a bridge
 - The resident local bus is often called front side bus

 Chapter 2.3 Parallel Interfacing with ISA and PCI bus



Back of computer

Pin #		
1	-12V	TRST
2	TCK	+12V
3	GND	TMS
4	TD0	TD1
5	+5V	+5V
6	+5V	INTA
7	INTB	INTC
8	INTD	+5V
9	PRSENT 1	
10		+VIO
11	PRSENT 2	
12	KEY	KEY
13	KEY	KEY
14		
15	GND	RST
16	CLK	VIO
17	GND	VNT
18	REQ	GND
19	+V IO	
20	AD31	AD30
21	AD29	+3.3V
22	GND	AD28
23	AD27	AD26
24	AD25	GND
25	+3.3V	AD24
26	C/BE3	IDSEL
27	AD23	+3.3V
28	GND	AD22
29	AD21	AD20
30	AD19	GND
31	+3.3V	AD18
32	AD17	AD16
33	C/BE2	+3.3V
34	GND	FRAME
35	TRDY	GND
36	+3.3V	TRDY
37	DEVSEL	GND
38	GND	STOP
39	LOCK	+3.3V
40	PERR	SOONE

Solder Side

Component Side

Pin #		
41	+3.3V	SB0
42	SERR	GND
43	+3.3V	PAR
44	C/BE1	AD15
45	AD14	+3.3V
46	GND	AD13
47	AD12	AD11
48	AD10	GND
49	GND	AD9
50	KEY	KEY
51	KEY	KEY
52	AD8	C/BE0
53	AD7	+3.3V
54	+3.3V	AD6
55	AD5	AD4
56	AD3	GND
57	GND	AD2
58	AD1	AD0
59	+V IO	+V IO
60	ACK64F	REQ64
61	+5V	+5V
62	+5V	+5V
63		GND
64	GND	C/BE7
65	C/BE6	C/BE5
66	C/BE4	+V IO
67	GND	PAR64
68	AD63	AD62
69	AD61	GND
70	+V IO	AD60
71	AD59	AD58
72	AD57	GND
73	GND	AD56
74	AD55	AD54
75	AD53	+V IO
76	GND	AD52
77	AD51	AD50
78	AD49	GND
79	+V IO	AD48
80	AD47	AD46
81	AD45	GND
82	GND	AD44
83	AD43	AD42
84	AD41	+VIO
85	GND	AD40
86	AD39	AD38
87	AD37	GND
88	+VIO	AD36
89	AD35	AD34
90	AD33	GND
91	GND	AD32
92		
93		GND
94	GND	

Solder Side

Component Side

- Notes: (1) pins 63–84 exist only on the 64-bit PCI card
 (2) + VIO is 3.3V on a 3.3V board and +5V on a 5V board
 (3) blank pins are reserved

PA3	1	40	PA4
PA2	2	39	PA5
PA1	3	38	PA6
PA0	4	37	PA7
$\overline{\text{RD}}$	5	36	$\overline{\text{WR}}$
$\overline{\text{CS}}$	6	35	RESET
GND	7	34	D0
A1	8	33	D1
A0	9	32	D2
PC7	10	31	D3
PC6	11	30	D4
PC5	12	29	D5
PC4	13	28	D6
PC0	14	27	D7
PC1	15	26	V _{cc}
PC2	16	25	PB7
PC3	17	24	PB6
PB0	18	23	PB5
PB1	19	22	PB4
PB2	20	21	PB3


Pins and their usage in Intel 8255

TUTORIAL EXAMPLES:

- **Tutorials:**
- 1. Assume that your group has decided to make a PC based control system for a wine company. After studying the system, your group found out that the following to be implemented for controlling purpose:
 - Pressure measurement (6 points)
 - Temperature measurement (5 points)
 - Weight measurement (1 point)
 - Volume measurement for filling (5 points)
- Your group also decided to use 8255A PPI card at base address 0550H.
 - a) List out collected documents and components
 - b) List out different signals you need to derive and/or can be directly connected to your interfacing circuit.
 - c) Draw minimum mapping circuit for above system
 - d) What are the address captured by card
 - e) Generate necessary control word
 - f) Write a program module for measuring the pressure of all the points and control if the pressure is not in a range, Assume suitable data if necessary.

Solution:

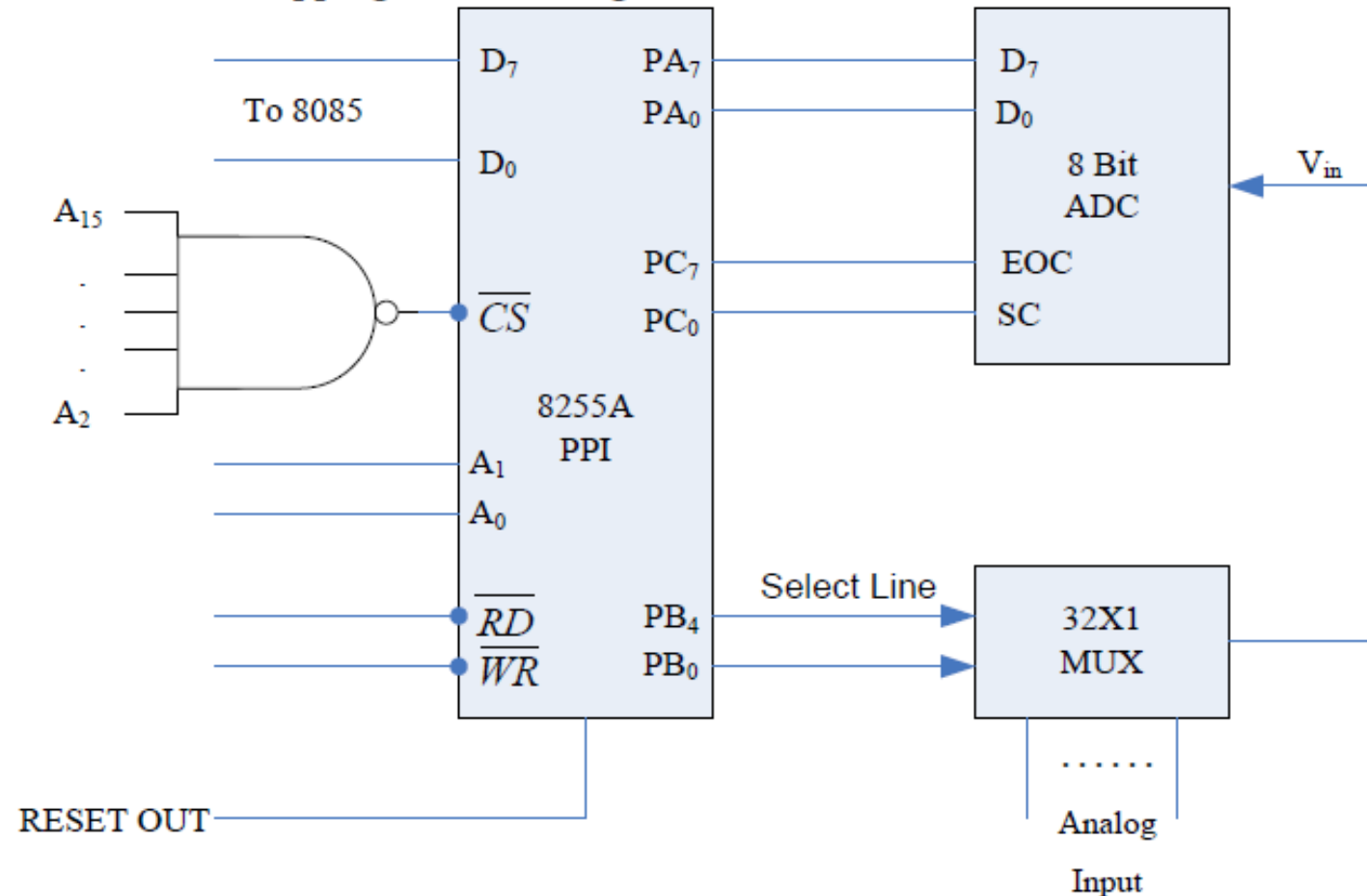- a) Components: 8255A card, ADC, MUX, Memory, Processor, connecting wires, power supplies (+5V, GND), gates etc.
Documents: Data sheets and technical documentation of above components
- b) Signals needed to be derived on directly connected to circuit
- A1, A2, Chip Select (\overline{CS}) for Port selection of 8255A, RESET signal
 - Read (\overline{RD}) and Write (\overline{WR}) signals
 - Start Conversion (SC) and End of Conversion (EOC)
- c) The minimum mapping circuit is as given below:



d) The base address of card is 0550H, following are address captured by card.

Port	Address	A 1 5	A 1 4	A 1 3	A 1 2	A 1 1	A 1 0	A 9	A 8	A 7	A 6	A 5	A 4	A 3	A 2	A 1	A 0
A	0550H	0	0	0	0	0	1	0	1	0	1	0	1	0	0	0	0
B	0551H	0	0	0	0	0	1	0	1	0	1	0	1	0	0	0	1
C	0552H	0	0	0	0	0	1	0	1	0	1	0	1	0	0	1	0
CR	0553H	0	0	0	0	0	1	0	1	0	1	0	1	0	0	1	1

The total numbers of monitoring points are 17. If we use 1 ADC for all of them, we need to select any one at given time. So, we can use 32X1 MUX which would then have $2^5=32$ i.e. 5 selection lines (B_0 to B_4). These lines can have defined for any of the 17 lines.

In the above circuit,

Port A → Input port to read data from ADC in mode 0

Port B → Output port to select any one of 17 lines from MUX in mode 0

Port C → Output port (PC_0 as SC) and Input port (PC_7 as EOC)

e) Control word and BSR words:

Control word to set up port ports in above configuration:

D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	= 98H
1	0	0	1	1	0	0	0	

BSR word to set PC_0

D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	= 01H
0	0	0	0	0	0	0	1	


```

f) Program Module:
    LXI H, MEMORY
    MVI A, 98H
    STA 0553H; write control word in CR
    MVI C, 06H; set counter to read 6 pressure points
    MVI B, 00H; selection of points for MUX
NEXT: MOV A, B
    STA 0551H; select first pressure point
    MVI A, 01H; load A with BSR word to set PC0
    STA 0553H; set SC line
    CALL DELAY
    MVI A, 00H; load A with BSR word to reset PC0
    STA 0553H; reset SC line
READ: LDA 0552H; read port C
    RAL
    JNC READ; check for PC7
    LDA 0550H; read data from port A
    MOV M, A; store value in memory
    CPI MAX_VALUE; compare with maximum value
    JNC CONTROL; control value
    CPI MIN_VALUE; compare with minimum value
    JC CONTROL; control value
    INR B
    INX H
    DCR C
    JNZ NEXT

```