

- Design an address decoding circuit of an input and output ports where output interface port is B0H and input interface port is B5H.


#### Step 1: Memory Mapping

Device Address	A <sub>7</sub>	A <sub>6</sub>	A <sub>5</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
Output: B0H	1	0	1	1	0	0	0	0
Input: B5H	1	0	1	1	0	1	0	1

#### Step 2: Decide decoder pins

Here, bit A<sub>2</sub> and A<sub>0</sub> in address lines for input and output are different, so we require a 2X4 decoder. Rest of the address lines will be decoded to generate chip enable signals for 2X4 decoder.

#### Step 3: Draw a decoding circuit

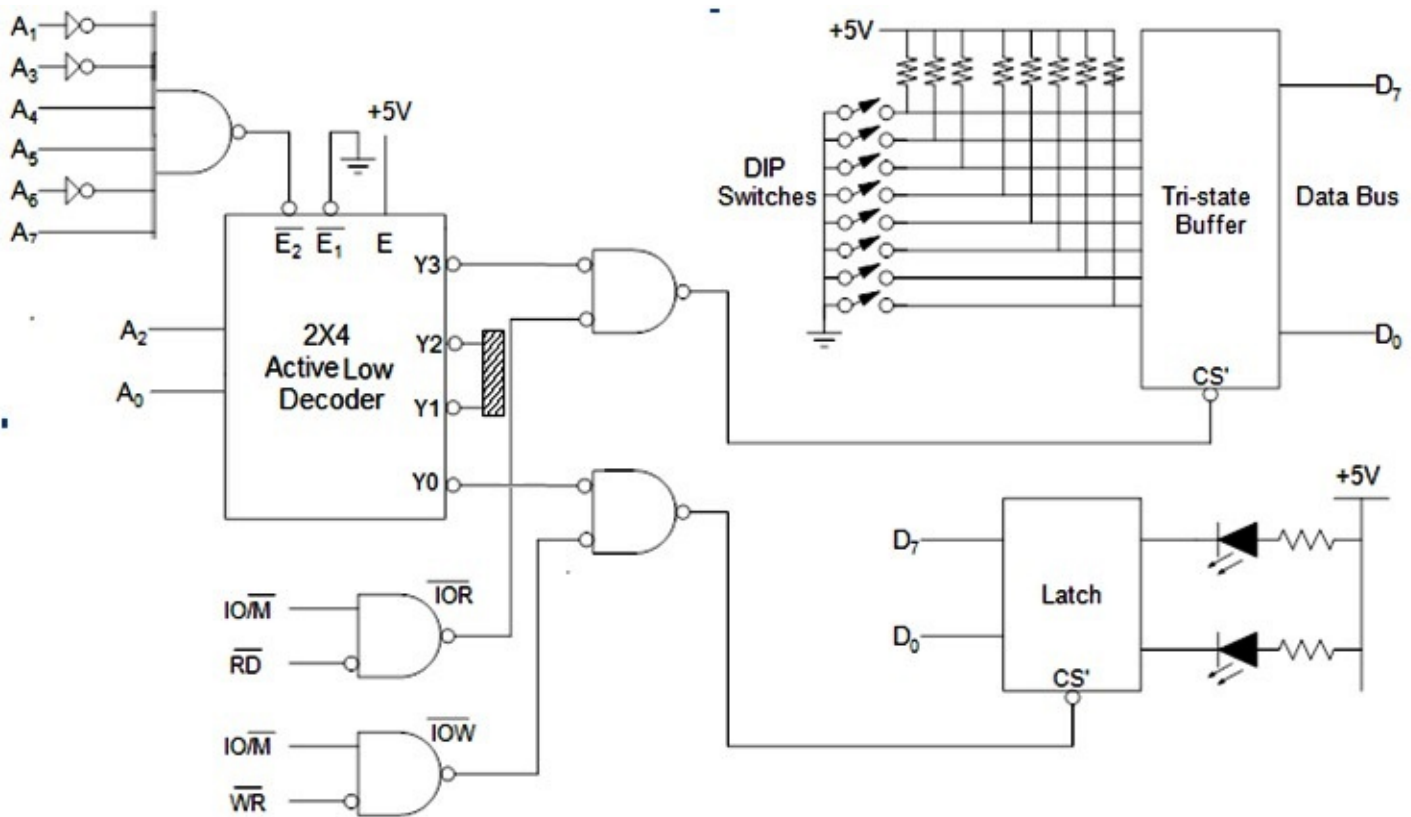

#### Step 4: Explanation

Here A<sub>0</sub> and A<sub>2</sub> are used as inputs of decoder. Output port (latch) is connected at output Y0 and will be selected when A<sub>2</sub>A<sub>0</sub>=00. Input port (tri-state buffer) is connected at input Y3 and will be selected when A<sub>2</sub>A<sub>0</sub>=11. Rest of the address bits are used to enable decoder and it will be enabled when A<sub>7</sub>A<sub>6</sub>A<sub>5</sub>A<sub>4</sub>A<sub>3</sub>A<sub>1</sub>=101100.




### Step 3: Decide address bits for RAM and ROM

We check start and end bits one by one of RAM starting from MSB until we get different bits. After getting different bits, we can say the address bits required for RAM is from different bit to  $A_0$ . We repeat same process for ROM.

Memory Block	Address	$A_{15}$	$A_{14}$	$A_{13}$	$A_{12}$	$A_{11}$	$A_{10}$	$A_9$	$A_8$	$A_7$	$A_6$	$A_5$	$A_4$	$A_3$	$A_2$	$A_1$	$A_0$
RAM	Start:5000H	0	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0
	End:57FFH	0	1	0	1	0	1	1	1	1	1	1	1	1	1	1	1
ROM	Start:5800H	0	1	0	1	1	0	0	0	0	0	0	0	0	0	0	0
	End:67FFH	0	1	1	0	0	1	1	1	1	1	1	1	1	1	1	1

### Step 4: Draw decoding circuit

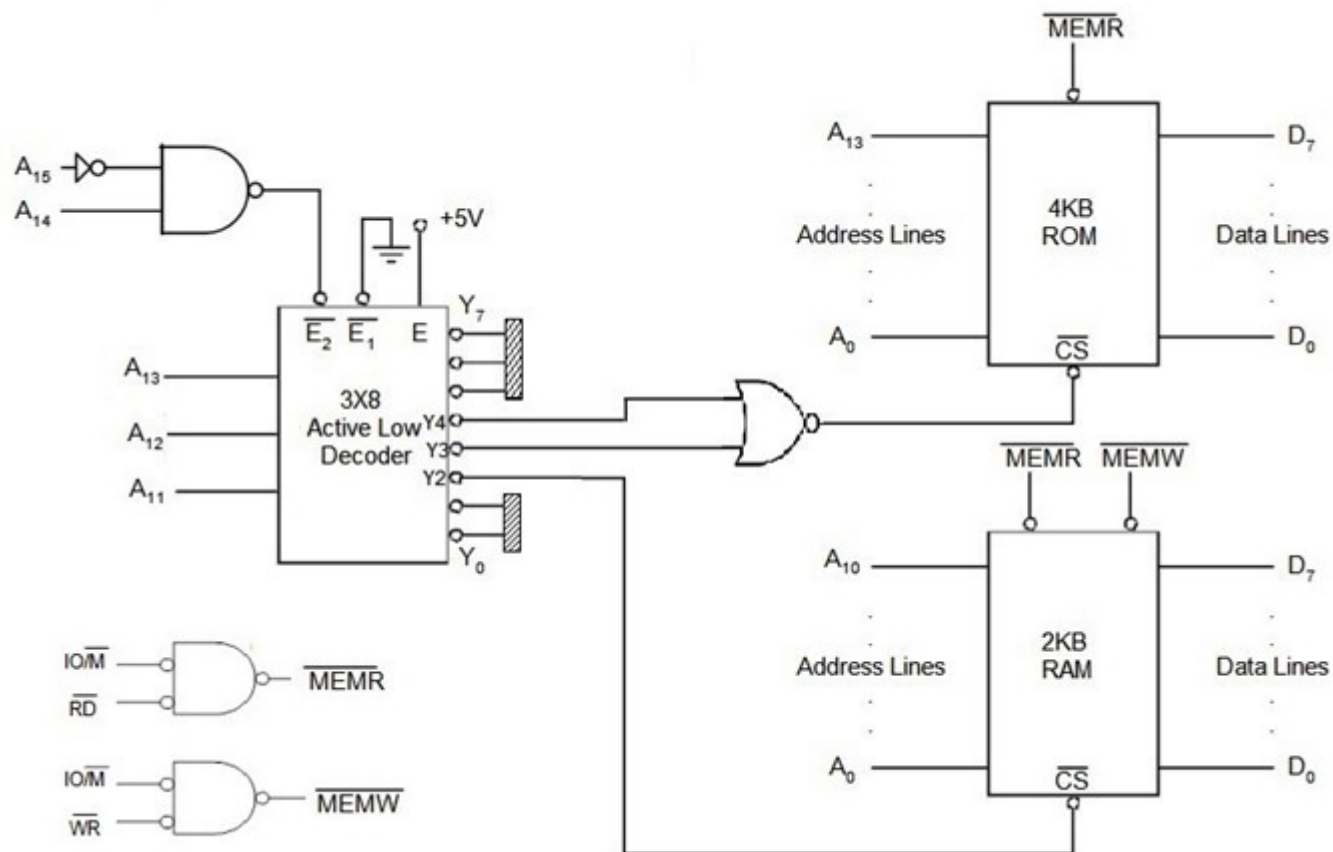

### Step 5: Explanation

Here  $A_{15}A_{14}$  bits are used to enable 3x8 decoder and will be enabled when  $A_{15}A_{14}=01$ .  $A_{13}A_{12}A_{11}$  are used as input of 3x8 decoder. When  $A_{13}A_{12}A_{11}=010$ , RAM will be selected and when  $A_{13}A_{12}A_{11}=011$  or  $100$ , ROM will be selected.

