

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity logic_gates is
    Port ( a : in  STD_LOGIC;
          b : in  STD_LOGIC;
          and_out, or_out, not_out, nand_out, nor_out, xor_out, xnor_out : out  STD_LOGIC);
end logic_gates;


architecture Behavioral of logic_gates is

begin

    and_out <= a and b;
    or_out <= a or b;
    not_out <= not a;
    nand_out <= a nand b;
    nor_out <= a nor b;
    xor_out <= a xor b;
    xnor_out <= a xnor b;

end Behavioral;

```

 

Full Adder


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity fulladder is
    port (      a,b,cin: in std_logic;
            sum, cout: out std_logic);
end fulladder;

architecture Behavioral of fulladder is

begin
    sum <= (a xor b) xor cin;
    cout <= (a and b) or (b and cin) or (a and cin);

end Behavioral;
```

 

Multiplexer

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;


entity mux is
    Port (
        sel : in STD_LOGIC_VECTOR ( 1 downto 0 );
        input : in STD_LOGIC_VECTOR ( 3 downto 0 );
        output : out STD_LOGIC);
end mux;

architecture Behavioral of mux is

begin
    with sel select
        output <=  input(0) when "00",
                    input(1) when "01",
                    input(2) when "10",
                    input(3) when "11",
                    '0' when others;

end Behavioral;

```

 


Decoder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity decoder is
    port (
        input: in std_logic_vector (2 downto 0);
        output: out std_logic_vector (7 downto 0));
end decoder;

architecture Behavioral of decoder is

begin
    output(0) <= '1' when input = "000" else '0';
    output(1) <= '1' when input = "001" else '0';
    output(2) <= '1' when input = "010" else '0';
    output(3) <= '1' when input = "011" else '0';
    output(4) <= '1' when input = "100" else '0';
    output(5) <= '1' when input = "101" else '0';
    output(6) <= '1' when input = "110" else '0';
    output(7) <= '1' when input = "111" else '0';
end Behavioral;
```

 

Seven Segment Display

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity sevensegment is
    port (
        a: in std_logic_vector (1 downto 0);
        b: in std_logic_vector (3 downto 0);
        an: out std_logic_vector (3 downto 0);
        seg: out std_logic_vector (6 downto 0));
end sevensegment;

architecture Behavioral of sevensegment is

begin
    seg<= "0000001" when b = "0000" else
        "1001111" when b = "0001" else
        "0010010" when b = "0010" else
        "0000110" when b = "0011" else
        "1001100" when b = "0100" else
        "0100100" when b = "0101" else
        "0100000" when b = "0110" else
        "0001111" when b = "0111" else
        "0000000" when b = "1000" else
        "0000100" when b = "1001" else
        "0001000" when b = "1010" else
        "0000000" when b = "1011" else
        "0110001" when b = "1100" else
        "0000001" when b = "1101" else
        "0110000" when b = "1110" else
        "0111000" when b = "1111" else
        "1111111";

    an <= "1110" when a = "00" else
        "1101" when a = "01" else
        "1011" when a = "10" else
        "0111" when a = "11" else
        "1111";

end Behavioral;
```

Note: This program doesn't contain any diagrams, the program was directly implemented in hardware

D-FlipFlop

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity dflipflop is
    Port( clr,clk,d: in std_logic;
          q: out std_logic );
end dflipflop;

architecture Behavioral of dflipflop is

begin
    process(clk,clr)
    begin
        if (clr='0') then q<='0';
        elsif rising_edge(clk) then q<=d;
        end if;
    end process;

end Behavioral;
```

JK-FlipFlop

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity jkflipflop is
    Port ( j,k,clr,clk: in STD_LOGIC;
          q,q0: out STD_LOGIC);
end jkflipflop;

architecture Behavioral of jkflipflop is
    signal qtemp: std_logic;
begin

    process (clr,clk)
    begin
        if (clr='0') then qtemp<='0';
        elsif rising_edge(clk) then
            if (j='0' and k='0') then NULL;
            elsif (j='0' and k='1') then qtemp<='1';
            elsif (j='1' and k='0') then qtemp<='0';
            elsif (j='1' and k='1') then qtemp<= not qtemp;
            end if;
        end if;
    end process;
    q<=qtemp;
    q0<=not qtemp;

end Behavioral;
```

Hex-Counter

counter.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity counter is
    Port (
        clk: in STD_LOGIC;
        count: out STD_LOGIC_VECTOR (3 downto 0)
    );
end counter;

architecture Behavioral of counter is
    signal c: STD_LOGIC_VECTOR (29 downto 0);
begin
    process(clk)
    begin
        if(rising_edge(clk)) then
            c <= c + 1;
        end if;
    end process;
    count <= c(28 downto 25);
end Behavioral;
```

sevensegment.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity sevensegment is
    port (
        a: in std_logic_vector (1 downto 0);
        b: in std_logic_vector (3 downto 0);
        an: out std_logic_vector (3 downto 0);
        seg: out std_logic_vector (6 downto 0));
end sevensegment;

architecture Behavioral of sevensegment is
```



```

begin
    seg <="00000001" when b = "0000" else
        "10011111" when b = "0001" else
        "0010010" when b = "0010" else
        "0000110" when b = "0011" else
        "1001100" when b = "0100" else
        "0100100" when b = "0101" else
        "0100000" when b = "0110" else
        "0001111" when b = "0111" else
        "0000000" when b = "1000" else
        "0000100" when b = "1001" else
        "0001000" when b = "1010" else
        "0000000" when b = "1011" else
        "0110001" when b = "1100" else
        "0000001" when b = "1101" else
        "0110000" when b = "1110" else
        "0111000" when b = "1111" else
        "1111111";

    an <= "1110" when a = "00" else
        "1101" when a = "01" else
        "1011" when a = "10" else
        "0111" when a = "11" else
        "1111";

end Behavioral;

```

hexcounter.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity hexcounter is
    Port (
        clk_50MHz: in STD_LOGIC;
        an: out STD_LOGIC_VECTOR(3 downto 0);
        seg: out STD_LOGIC_VECTOR(6 downto 0)
    );
end hexcounter;

architecture Behavioral of hexcounter is
    component counter is

```

```

    Port (
        clk: in STD_LOGIC;
        count: out STD_LOGIC_VECTOR (3 downto 0)
    );
end component;
component sevensegment is
    port (
        a: in std_logic_vector (1 downto 0);
        b: in std_logic_vector (3 downto 0);
        an: out std_logic_vector (3 downto 0);
        seg: out std_logic_vector (6 downto 0)
    );
end component;
signal s: STD_LOGIC_VECTOR(3 downto 0);
begin
    c1: counter port map (clk=>clk_50MHz, count=>s);
    l1: sevensegment port map (a=>"00", b=>s, seg=>seg, an=>an);

end Behavioral;

```

STATE MACHINE

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

---- Uncomment the following library declaration if instantiating
---- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity FSM is
port(F : out STD_LOGIC_VECTOR (2 downto 0);
      clk, clr: in STD_LOGIC;
      k      : out STD_LOGIC ;
      ip      : in STD_LOGIC);
end FSM;

architecture Behavioral of FSM is

    signal count: integer;
    type state_type is (idle, s1,s2,s4,s5,s7);
    signal state:state_type;
    begin
    process(clk,clr)

    begin

    if (clr = '0') then state <= idle;

    elsif rising_edge(clk) then
    count <= count +1;
    if(count = 50) then
    count <= 0;
    if(state = idle and ip = '1') then
        state <= s1;
        k <= '1';

    elsif(state = idle and ip = '0') then
        NULL;

    elsif(state = s1 and ip = '1') then
        state <= s2;
        k <= '0';

    elsif(state = s1 and ip = '0') then
        NULL;

    elsif(state = s2 and ip = '1') then
```

```

        state <= s4;
        k <= '0';

elseif(state = s2 and ip = '0') then
    NULL;

elseif(state = s4 and ip = '1') then
    state <= s5;
    k <= '1';

elseif(state = s4 and ip = '0') then
    NULL;

elseif(state = s5 and ip = '1') then
    state <= s7;
    k <= '1';

elseif(state = s5 and ip = '0') then
    NULL;

elseif(state = s7 and ip = '1') then
    state <= s1;
    k <= '1';

elseif(state = s7 and ip = '0') then
    NULL;

else
    NULL;

end if;
end if;
end if;

end process;
F <= "000" WHEN state = idle else
    "001" when state = s1 else
    "010" when state = s2 else
    "100" when state = s4 else
    "101" when state = s5 else
    "111" when state = s7 else
    "000";

end Behavioral;

```

