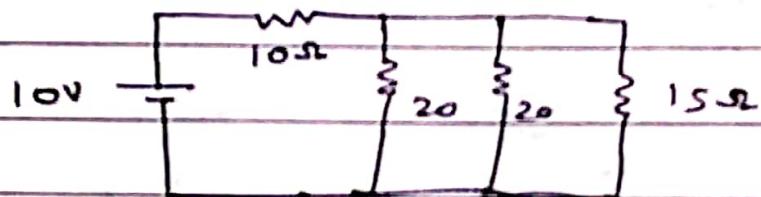



Thevenin's & Norton cont

2. Determine the current I_L through the $15\ \Omega$ resistor in the network given in fig 1 by a) Thevenin's theorem
b) Norton's theorem

Q





for R_{TH} or R_N

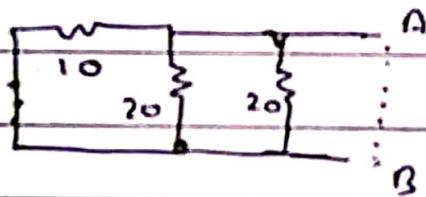

$$R_{TH} = R_N = (10 // 20) // 20 \\ = 5\ \Omega$$

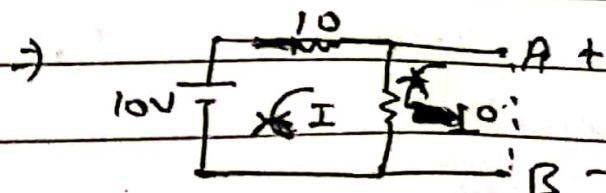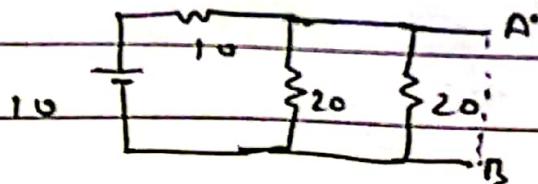- a) By Thevenin's theorem
Calculation of V_{TH}



Using KVL

$$10V = 10I + 10I$$


$$\therefore I = 0.5$$

$$- V_{Th} = 10(0.5)$$

$$V_{Th} = 10I = 10 \times 0.5 = 5V$$

Then eq. of thevenin circuit is

$$R_{Th} = 5\Omega$$

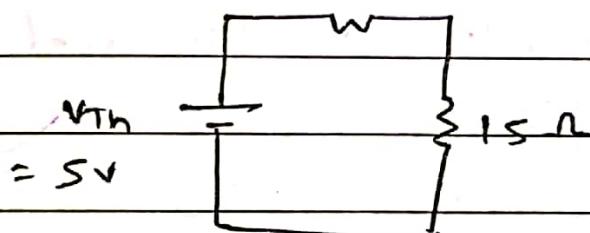


$$\text{Then } I_L = \frac{V_{Th}}{5+15} = \frac{5}{20}$$

$$= 0.25A$$

$$= 0.25A$$


b) By norton's theorem

calculation of I_N

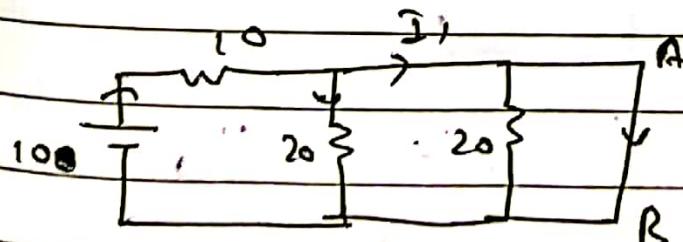

$$I = \frac{100}{5} = 20A$$


$$I_N = \frac{20}{20+20} = 10A$$

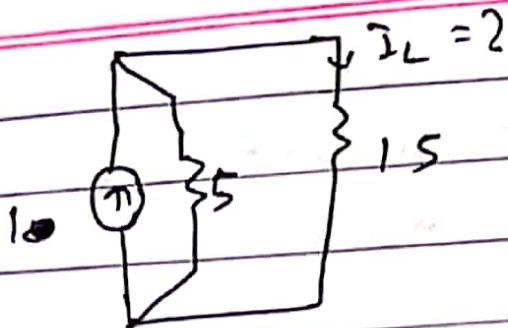


$$I_L = \frac{10 \times 5}{15 + 5} \times 10$$

$$= -0.5\text{A} \quad 0.25\text{A}$$

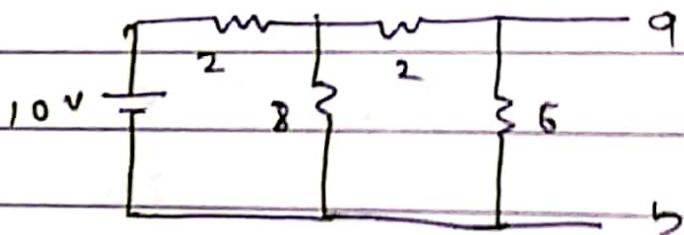2. Obtain the Thevenin and Norton equivalent circuit at terminal ab for networks of fig 2.




$$R_{Th} = R_N =$$

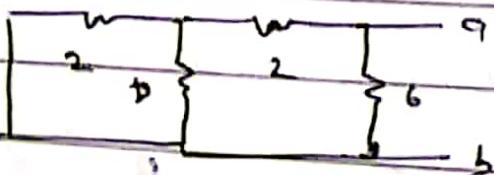

$$\begin{aligned} R_{Th} &= R_N = ((2/12) + 2) // 6 \\ &= 3.6 // 1.6 \\ &= 2.25 \Omega \end{aligned}$$

By thevenin's theorem

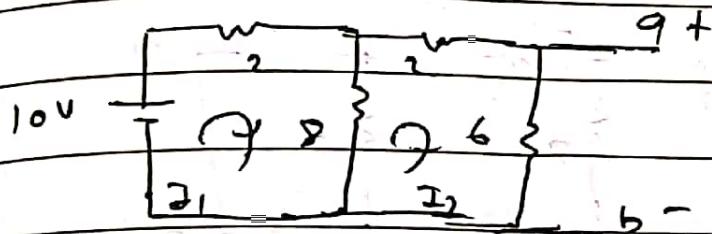

~~Mesh I~~ Mesh I

$$2I_1 + 8(I_1 - I_2) = 10$$

$$10I_1 - 8I_2 = 10 \quad \text{--- (1)}$$

Mesh II

$$2I_2 + 6I_2 + 8(I_2 - I_1) = 0$$

$$16I_2 - 8I_1 = 0$$

$$-8I_1 + 16I_2 = 0 \quad \text{--- (2)}$$


$$I_1 = 1.667 = \frac{5}{3}, \quad I_2 = 0.8333 = \frac{5}{6}$$

Then

$$V_{TH} = I_2 \times 6 = \frac{5}{6} \times 6 = 5 \text{ V}$$

$$\therefore V_{TH} = 5 \text{ V}$$

By norton equivalent.

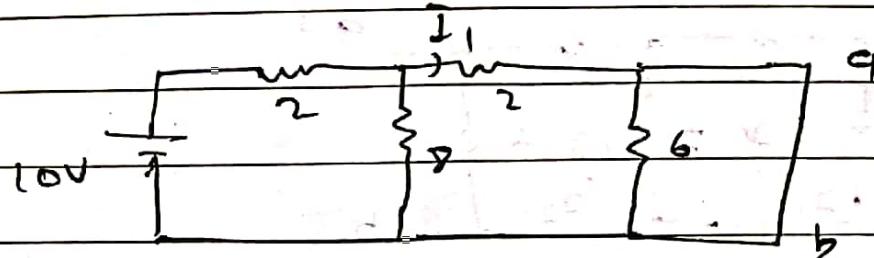


$$\cancel{I_1} = \frac{10}{2+8} = 1 \text{ A}$$

$$\cancel{I_2} = \frac{8}{2+8} \times 1 = 0.8 \text{ A}$$

$$= \frac{32}{9} = 3.556 \text{ A}$$

$$= 3.556 \text{ A}$$

then

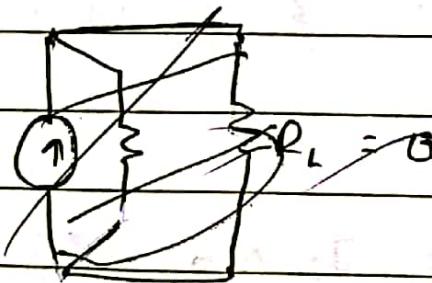

IN 2




$$R_{eq} = (8/12) + 2 = 3.66 \Omega$$

$$I = \frac{10}{3.6} = 2.778 A = 2.5 A$$


Then

$$\bar{I}_N = \frac{8}{2+8} \times 25 = 2.22 A$$

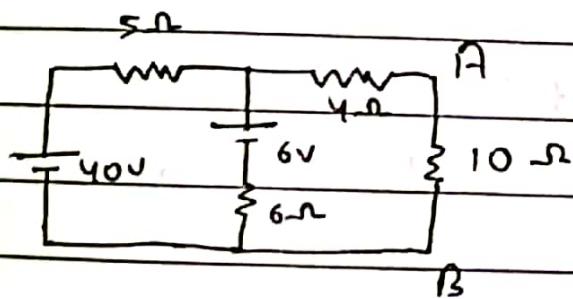3. Find pd across AB in the circuit shown in fig 3
- Using Thevenin's theorem
 - using Norton's Theorem




for, R_{Th} or R_N

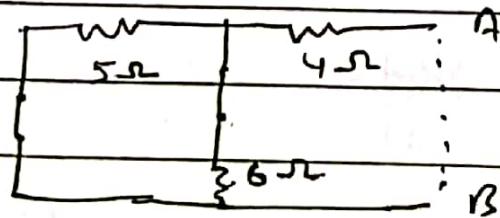

$$R_{Th} / R_N = (6/11) + 4$$

$$= 74 = 6.727 \Omega$$

By thevenin's theorem

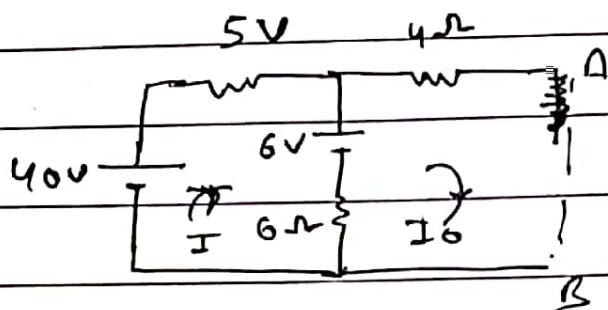

Calculation of V_{Th}

Apply KVL

$$40 - 6 = 5I + 6I$$

$$34 = 11I$$

$$I = \frac{34}{11} = 3.09$$

~~$$V_{BA} + 6 = 6I$$

$$= \frac{6 \times 34}{11} + \frac{4 \times 34}{11} - 6$$~~

$$V_{BA} + 6 = 6(0.34)$$

$$V_{BA} = -\frac{6 \times 34}{11} - 6$$


$$V_{BA} = -\frac{270}{11}$$

$$V_{AB} = \frac{270}{11} = 24.545 \text{ V} = V_{Th}$$

The thevenin's circuit is

~~24.545~~

24.545

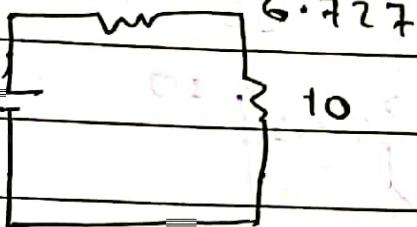


then

$$\text{Reqd } I_L = \frac{24.545}{6.727 + 10}$$

$$= 1.46 A$$

By Norton's theorem

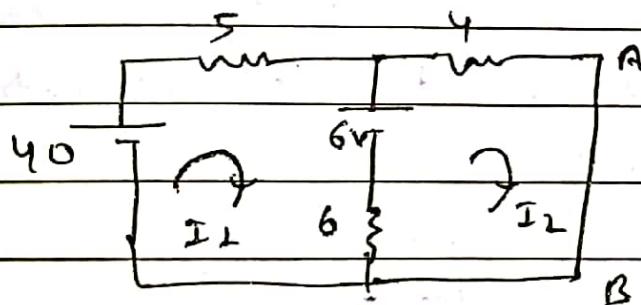

$$\text{Mesh I} \quad 40 - 6 = 5I_1 + 6I_1 - 6I_2$$

$$34 = 11I_1 - 6I_2 \quad -(1)$$


$$6 = 4I_2 + 6I_2 - 6I_1$$

$$6 = -6I_1 + 10I_2 \quad -(2)$$

Solving (1) & (2)


$$I_1 = 5.08 A \quad I_2 = 3.64 A$$

$$\text{So, } I_N = 3.64 A$$

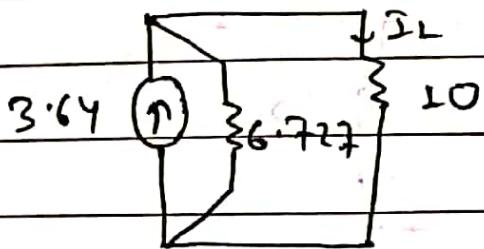


$$\text{Then } I_L = \frac{6.727 \times 3.64}{10 + 6.727} = 1.46 \text{ A}$$

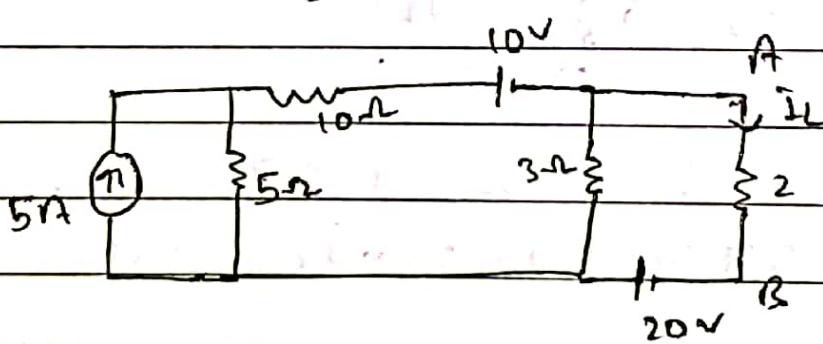
- (4) Use Thevenin's and Norton equivalent theorem to determine the current I_L , through the 2 ohm resistor of the network shown in fig 4



for R_{Th} or R_N

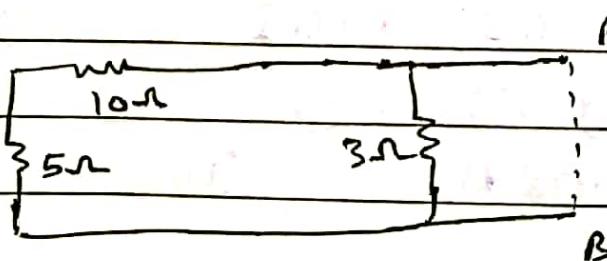

$$\therefore R_{Th} / R_N = (10+5)/3 = 2.5 \Omega$$

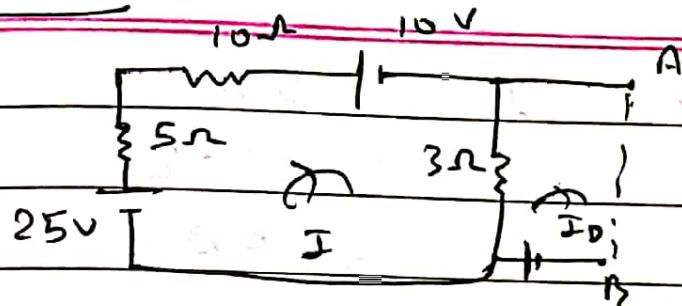Thevenin's

$$\text{Mesh I} \quad 25 - 10 = 5I + 10I + 3I$$

$$15 = 18I$$

$$I = \frac{5}{18} = 0.833$$


Mesh II

~~$$V_{BA} = -3I = -3 \times 0.833$$~~

~~$$V_{BA} = -2.5$$~~

~~$$V_{AB} = 2.5 = V_{Th}$$~~

Then

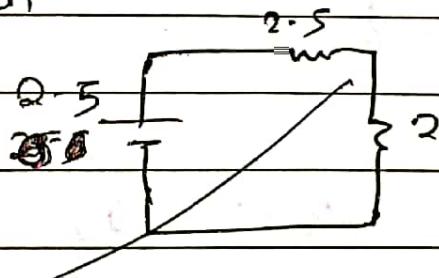


~~$$I_{Th} = \frac{2.5}{2.5+2} = 0.5556$$~~

$$V_{BA} + 20 = -3I$$

$$-V_{Th} = -3 \times \frac{5}{6} + -20$$


$$V_{Th} = 22.5$$

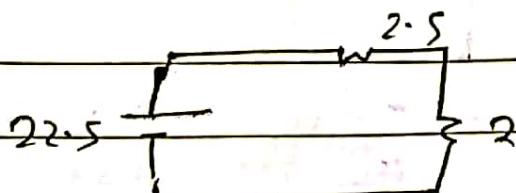

$$\text{Then } I_1 = \frac{22.5}{2.5 + 2}$$

$$= 5A$$

By Norton's

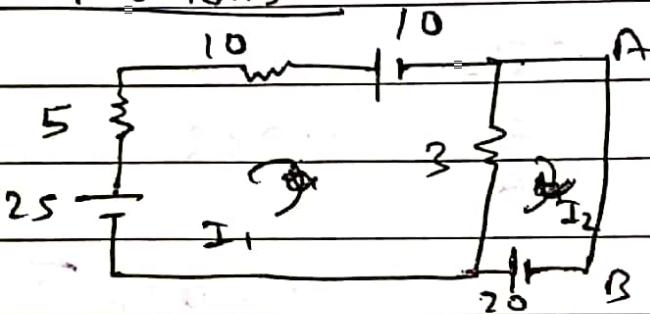

$$\text{Mesh I} - 10I_1 + 25 = 5I_1 + 10I_2 + 3I_1 - 3I_2$$

$$+15 = 18I_1 - 3I_2 \quad \text{--- (i)}$$

$$\cancel{I_1 = +\frac{15}{18}}$$

Mesh II

$$+20 = 3(I_2 - I_1)$$


$$+20 = 3I_2 \cancel{- 3I_1} = 3I_2 \quad \text{--- (ii)}$$

Solving (i) and (ii)

$$I_1 = 2.33A$$

$$I_2 = \cancel{+5.83} \cancel{- 9} A$$


Then

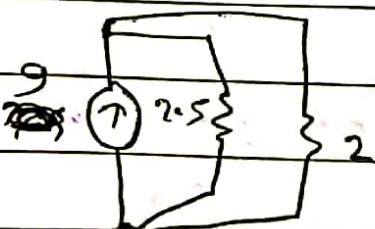



$$\text{Then } I_L = \frac{22.5}{2.5 + 2} = 5A$$

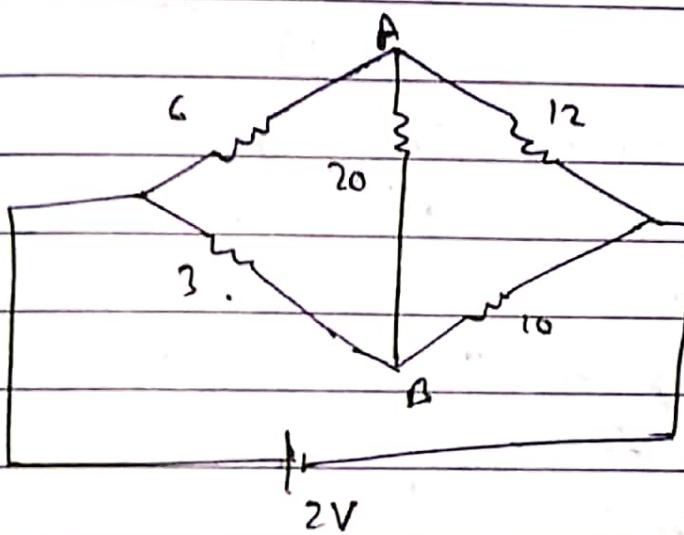5. Determine the current in 20Ω resistor of the network shown in Fig 5 a)

Using Thévenin's theorem b) Using Norton's theorem




Calculating R_{Th} or R_N

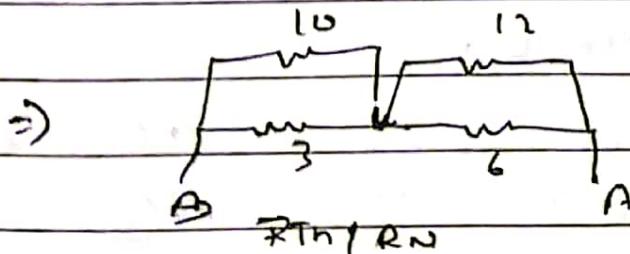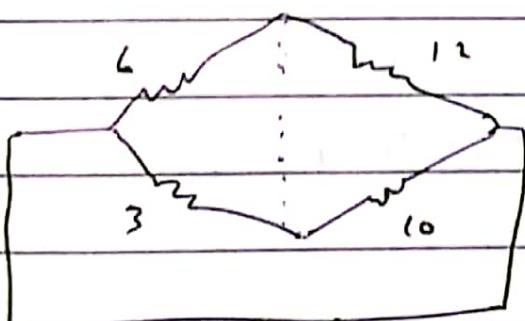

$$\begin{aligned}
 R_{Th} = R_N &= (3 \parallel 10) + (2 \parallel 6) \\
 &= 3 \times 10 + 12 \times 6 \\
 &\quad 3+10 \quad 12+6 \\
 &= 82 \\
 &\quad 13
 \end{aligned}$$

By Thevenin's theorem

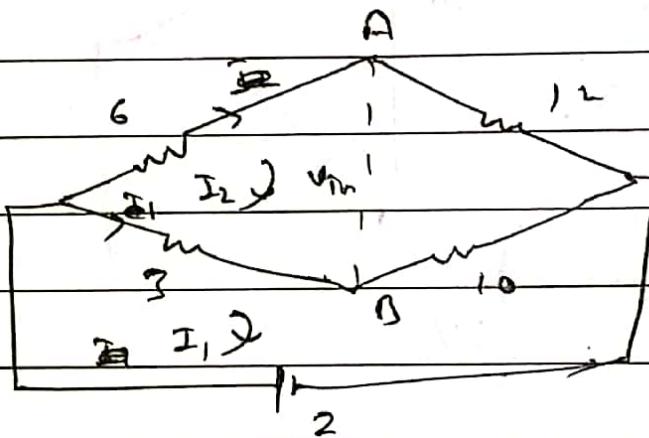

Applying KVL

$$2 = 3I_2 + 10I_1$$

$$I_1 = \frac{2}{13} A$$

Applying KCL,

Mesh I1,

$$2 = 3(2 - I_2) + 10(2 - I_1)$$

$$2 = 13I_1 - 13I_2 \quad \text{---(1)}$$

Mesh II

$$0 = 6(\bar{I}_2) \cancel{-} + 12\bar{I}_2 + 10(\bar{I}_2 - \bar{I}_1) + 3(\bar{I}_2 - \bar{I}_1)$$

$$0 = -13\bar{I}_1 + 31\bar{I}_2$$

$$\therefore \bar{I}_1 = \frac{3}{117}$$

$$\therefore \bar{I}_2 = \frac{1}{9}$$

Then

$$V_{Tn} = 3(\bar{I}_2 - \bar{I}_1) + 6\bar{I}_2$$


$$= 9\bar{I}_2 - 3\bar{I}_1$$

$$= 9 \times \frac{1}{9} - 3 \times \frac{3}{117}$$

$$V_{Th} = \frac{8}{39} = V_{AB}$$


$$\therefore V_{AB} = -\frac{8}{39}$$

Then

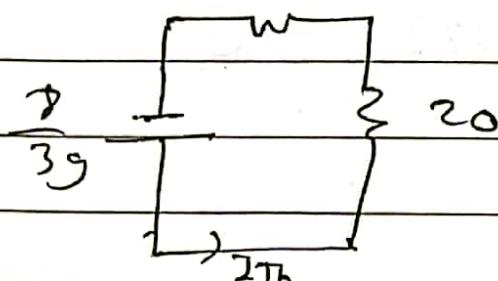

$$I_{Th} = \frac{82/13}{82/13 + 20} = 7.79 \times 10^{-3} = 7.79mA$$

b) Norton's Theorem

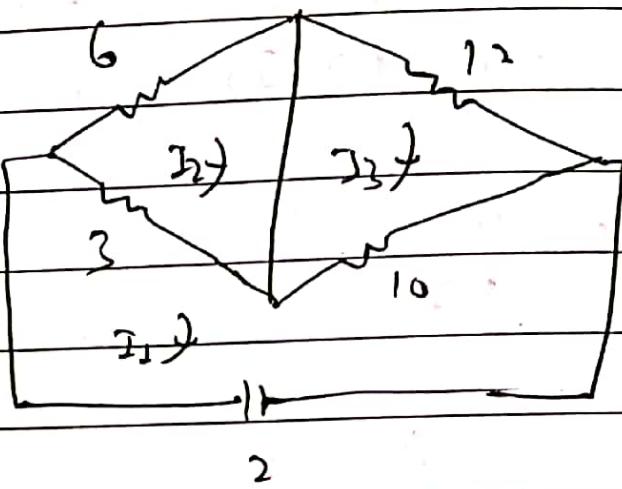

Mesh I

$$2 = 3(I_1 - I_2) + 10(I_1 - I_3)$$

$$2 = 3I_1 - 3I_2 + 10I_1 - 10I_3$$

$$2 = 13I_1 - 3I_2 - 10I_3 \quad (1)$$

Mesh II

$$3(I_2 - I_1) + 6I_2 = 0$$

$$-3I_1 + 9I_2 = 0 \quad (2)$$

Mesh III

$$12I_3 + 10(I_3 - I_1) = 0$$

$$-10I_1 + 22I_3 = 0 \quad (3)$$

Solving,


$$I_1 = \frac{11}{41}$$

$$I_2 = \frac{11}{123}$$

$$I_3 = \frac{5}{41}$$

$$I_n = I_3 - I_2 \\ = \frac{5}{41} - \frac{11}{123}$$
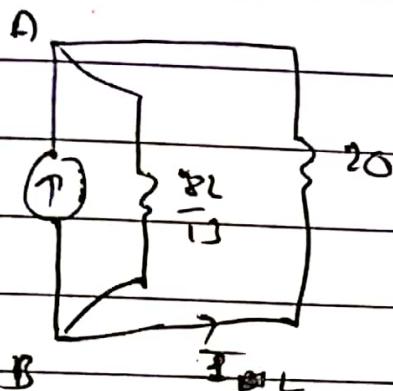
$$= \frac{4}{123} \quad (\cancel{B+A}) \quad (B \rightarrow A)$$



$$I_L = \frac{82/13}{20 + 82/13} \times \frac{4}{123}$$

$$= \frac{82}{13} \times \frac{13}{342} \times \frac{4}{123}$$

$$= \underline{8}$$

39

$$= 7.8 \text{ mA} \quad \text{Ans}$$

Name: Bhaskar Subedi
Class: BCTA 22

classmate


Date _____

Page _____

Tutorial No: 3


Q. Determine the current in 10Ω by

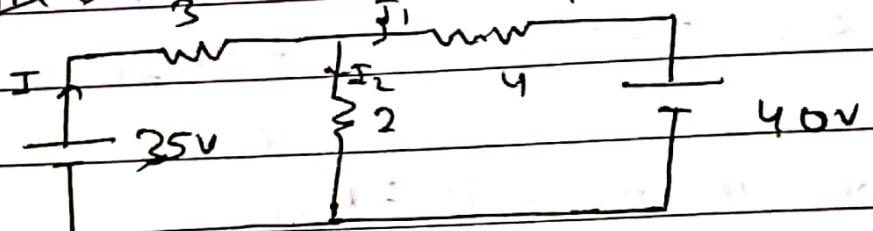10. By using superposition theorem. find the current in 10Ω and current from diff. branch



Soln

considering ~~10V~~ 35V only

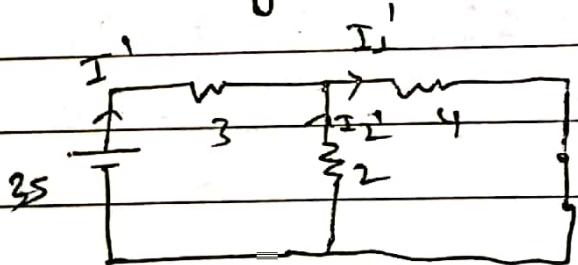


$$R_{eq} = 3 + (4 \parallel 2) \\ = 4.33 \Omega$$

$$I' = \frac{35}{4.33} = \frac{v}{R_{eq}} = 8.07 A$$

$$I_1 = \frac{2}{4+2} \times I' = \frac{2}{6} \times 8.07 = \boxed{2.69 A}$$

$$I_2 = \frac{4}{4+2} \times I' = \frac{4}{6} \times 8.07 = \boxed{5.38 A}$$

Again consider 40 V

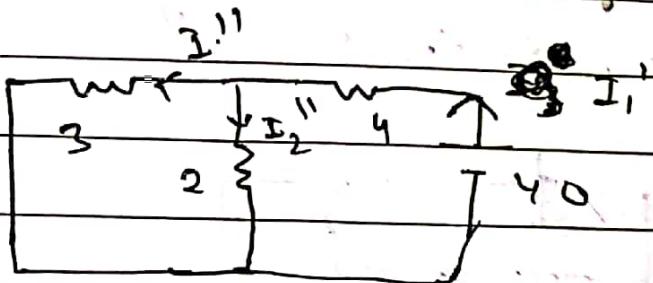

$$\text{Req} = 4 + (3 \parallel 2)$$

$$= 5.2 \Omega$$

$$I_1'' = \frac{V}{\text{Req}} = \frac{40}{5.2} = 7.69 \text{ A}$$

$$I_1' = \frac{2}{3+2} \times 7.69 = 3.076$$

$$I_2' = \frac{3}{3+2} \times 7.69 = 4.614$$

According to superposition

$$I_0 = I_1' - I_1''$$

$$= 8.07 - 3.07 = +5.2 \cancel{= 5.5}$$


$$I_1 = I_1' - I_1'' = \cancel{1.92} - 7.69 = \cancel{-5} - 2.69$$

$$= \cancel{-5.77} \cancel{= 5 \text{ A}}$$


$$I_2 = I_2' + I_2'' = \cancel{4.614} + \cancel{3.84} 5.38 + 4.614$$

$$= \cancel{8.154} \cancel{= 10 \text{ A}}$$

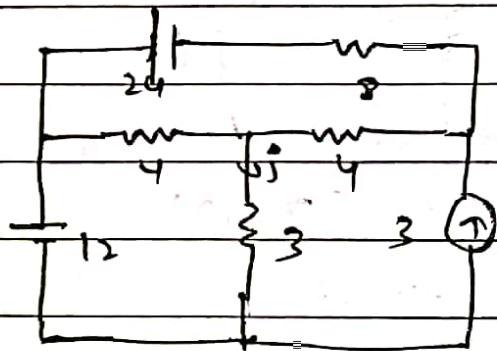(11) For the circuit in fig 11. Use superposition theorem to find it.



Consider 12V only

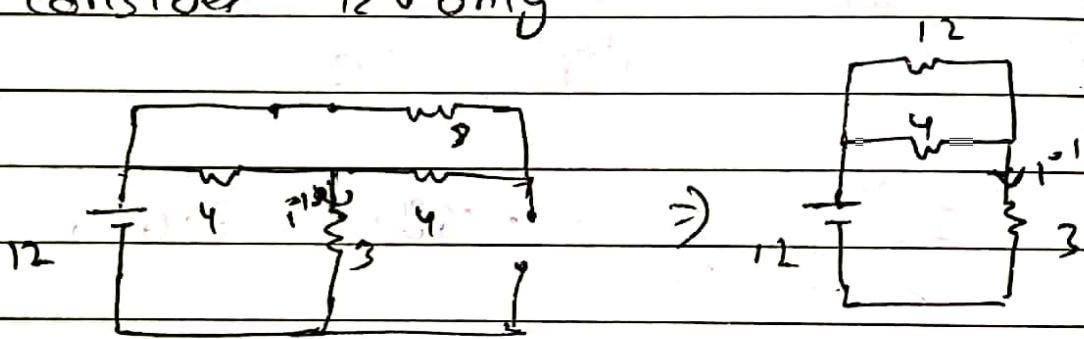

$$R_{eq} = \left(\frac{1}{4} \parallel \left(\frac{1}{8} + \frac{1}{4} \right) \right) + 3$$


$$= 6 \Omega$$

$$i' = \frac{12V}{6\Omega} = 2A$$

$$R = \frac{12V}{2A} = 6\Omega$$

$$= 2A$$

Consider 24V only

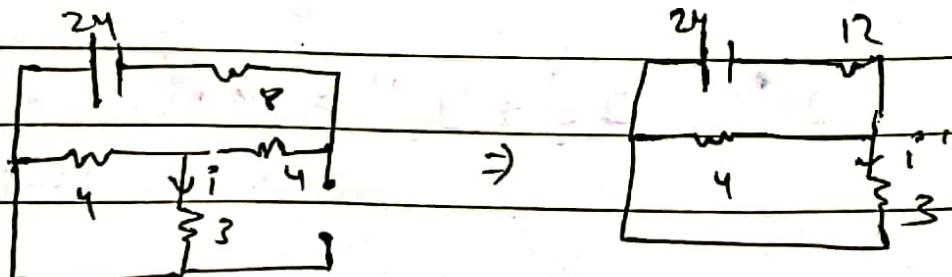

$$\text{Req} = 12 + (4 \parallel 13)$$

$$= 13.71\Omega$$

Then,


$$I = \frac{24}{13.71} = 1.75A$$

Then,



$$i'' = 4 \times 1.75 = 2A$$



$i_1 + i_2$

Consider 3A current source only

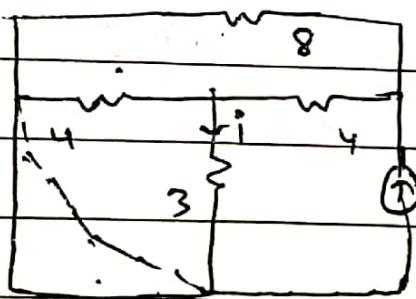

$$8 \parallel 4 = 1.2$$

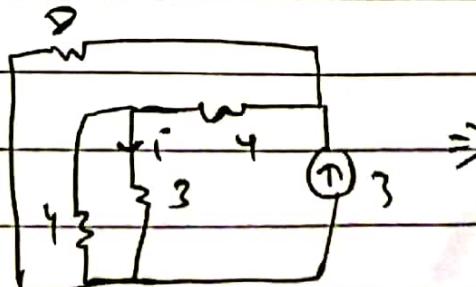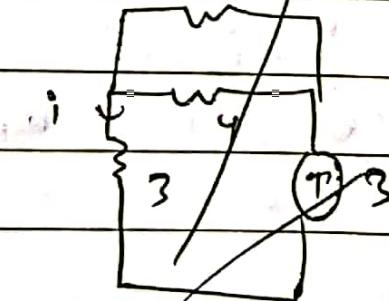

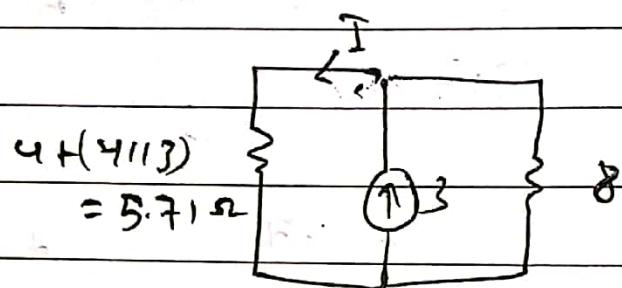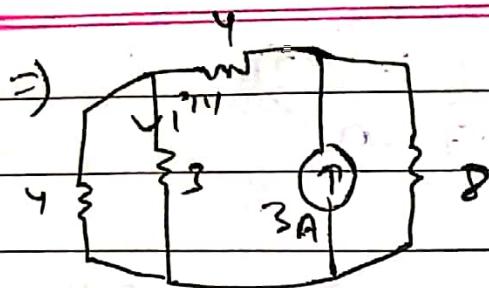

$$I = \frac{12}{5.75} = 2.09 \text{ A}$$

$$= 2.09 - 3 = -0.91 \text{ A}$$

Then

$$i'' = \frac{4}{4+3} \times 2.09 = 1.39 \text{ A}$$

Then


finally,

$$i = i' - i'' + i'''$$



$$= 2.09 - 1.39 + 1 = 1.7 \text{ A}$$

$$= 2 \text{ A}$$

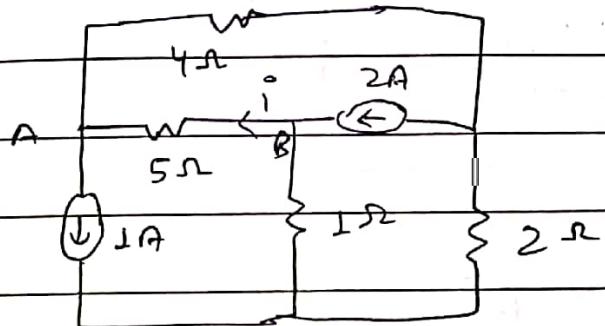(12) Using superposition theorem, find current through 5Ω .




Consider $2A$ only

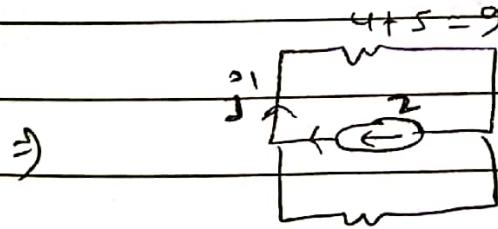
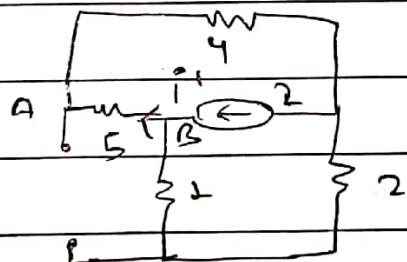


$$1+2 = 3$$

$$i_1 = \frac{3}{3+9} \times 2 = 0.5 \text{ A}$$

Consider $1A$ only

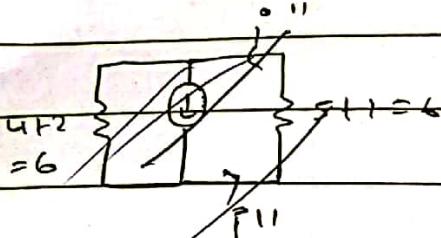

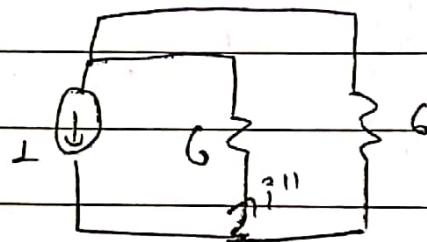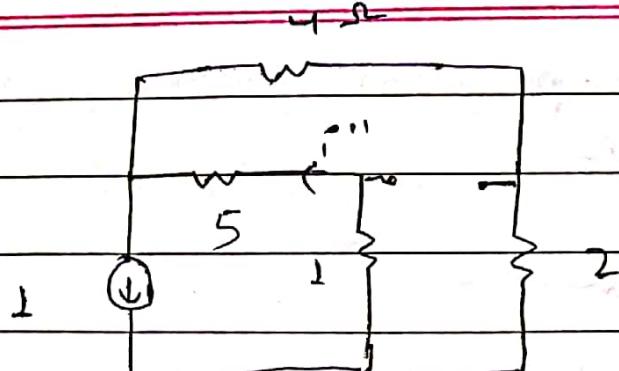


$$\cancel{0} = i'' = \frac{6 \cancel{0} \times 1}{6+6} = 0.5$$

$$i = i' + i''$$


$$\cancel{= 0.5 + 3 = 3.5A}$$

$$= 0.5 + 0.5 = 1A$$


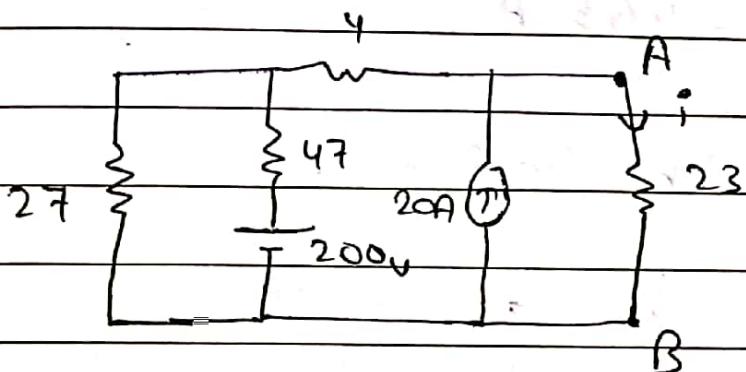
7. Compute the current through 23Ω resistor of the fig 7 using superposition theorem



Taking 200V only

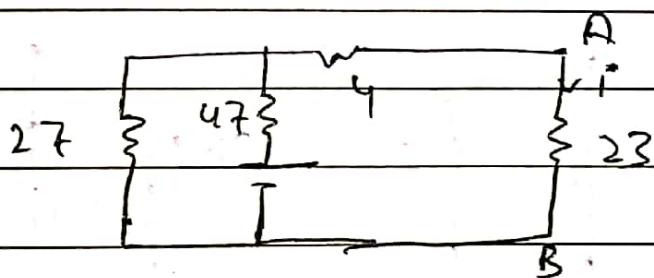

$$\therefore R_{eq} = (4 + 23)$$

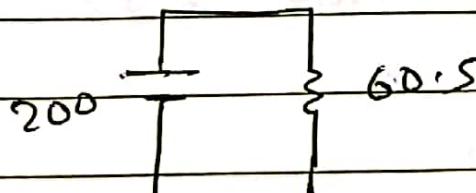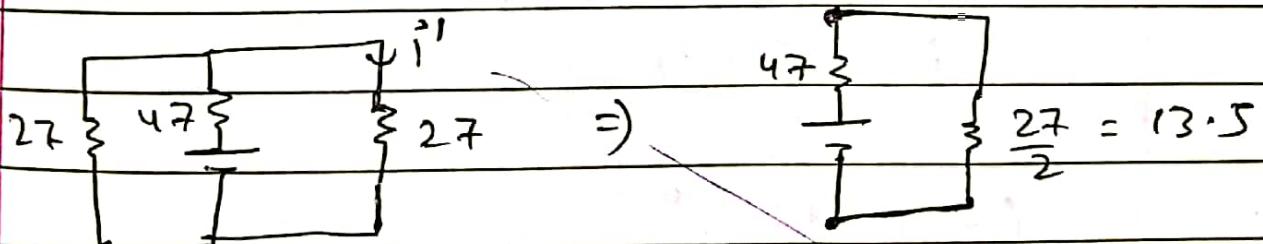



$$I = \frac{200}{60.5} = 3.305$$

$$i' = 27 \times 3.205$$

$$27 + 27$$

$$= 1.65 A$$

Consider 20A only

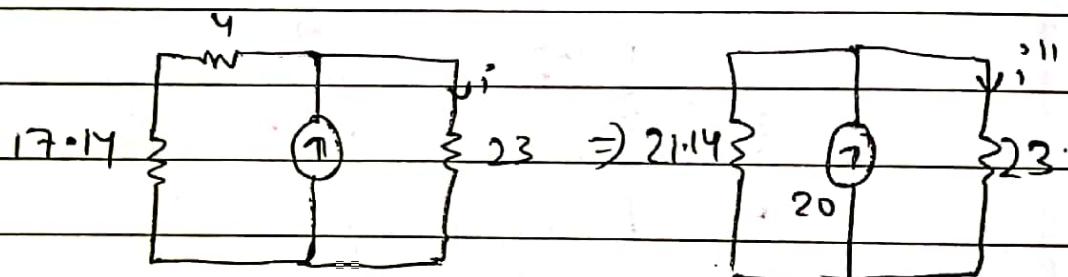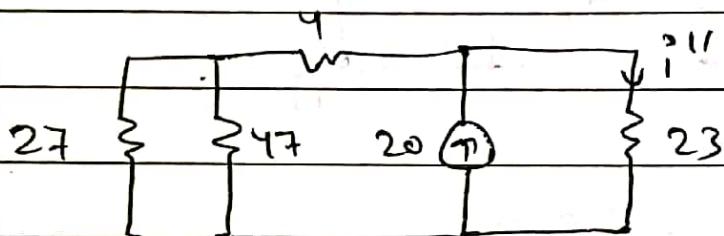

$$i'' = 21.14 \times 20$$

$$21.14 + 23$$


$$i'' = 9.58$$

$$i = i' + i''$$





$$= 9.58 + 1.65 + 9.58$$



$$= 11.23 A$$

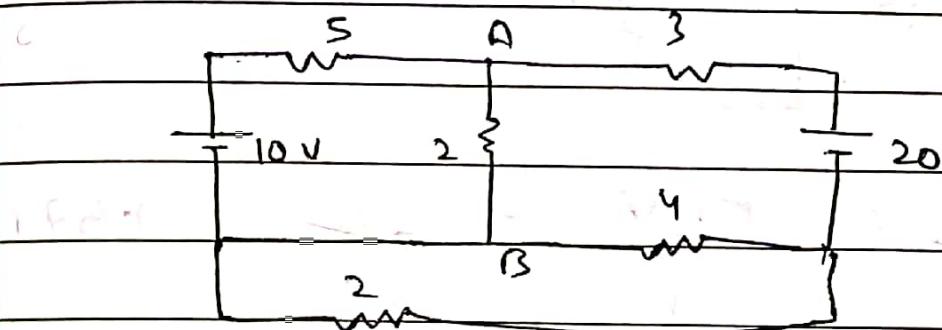(8) Find the current in 2Ω resistor between A and B for network shown in fig 8. using superposition theorem



Taking 10V only

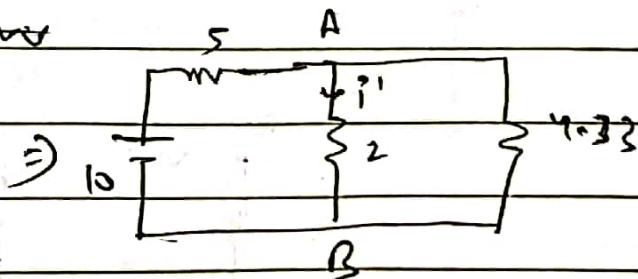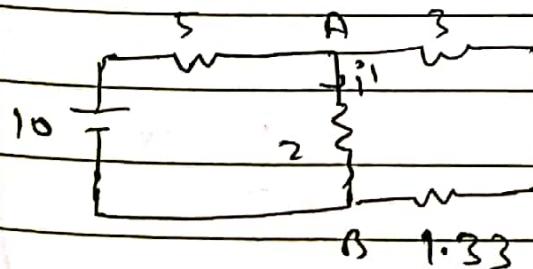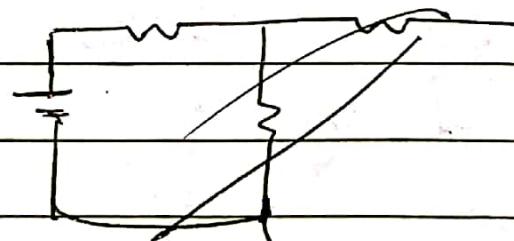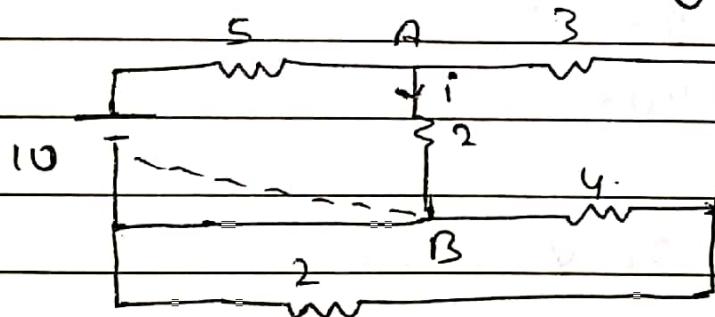

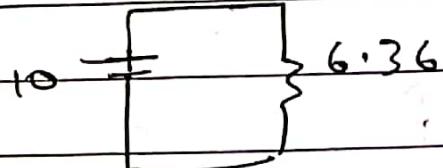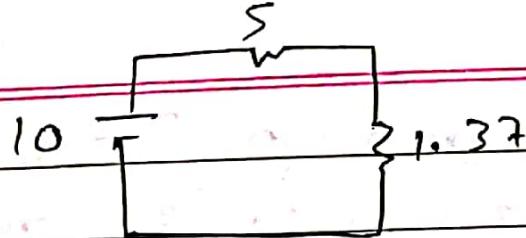



$$I = \frac{10}{5} = \frac{2}{6.36} = 1.57 \text{ A}$$

Req

$$i' = \frac{4.33}{2 + 4.33} \times 1.57$$

$$i' = 1.07$$

Taking 20V only

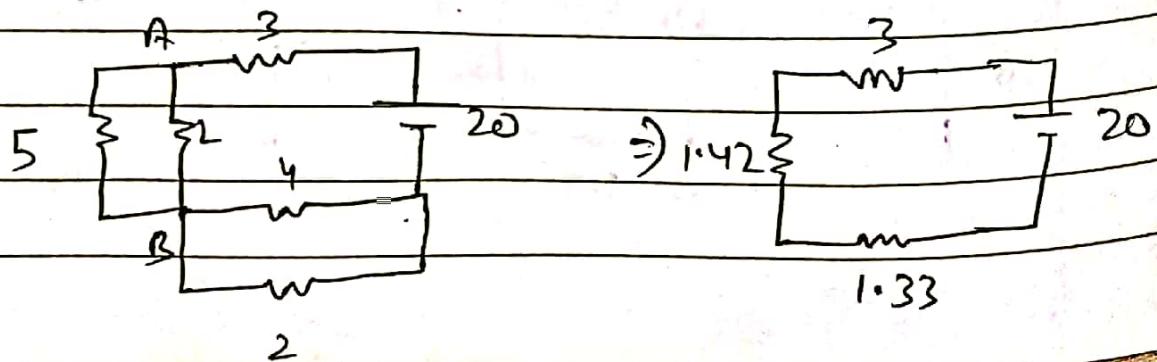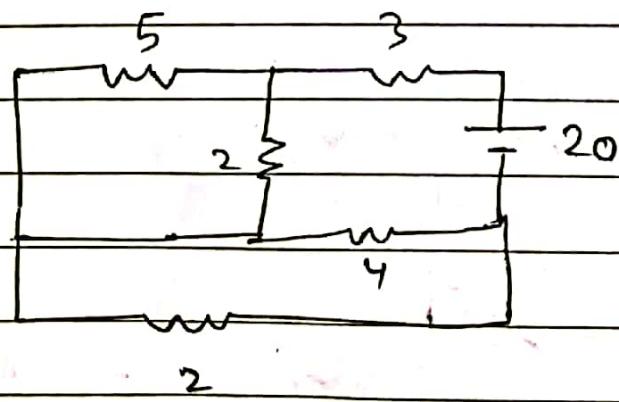

$$R_{eq} = 5.75$$

$$I = \frac{20}{5.75} = 3.47 A$$


Then

$$\begin{aligned} i'' &= 5 \times 3.47 \\ &= 5+2 \\ &= 2.48 \end{aligned}$$



Then


$$\begin{aligned} i &= i' + i'' \\ &= 1.07 + 2.48 \\ &= 3.55 A \end{aligned}$$

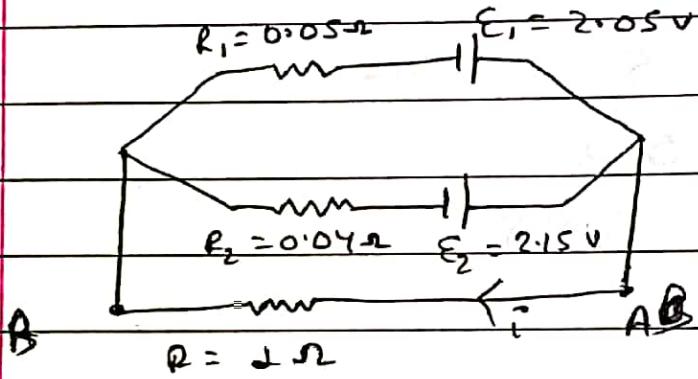(g) By using superposition theorem, find the current in resistance R shown in fig 9. Internal resistance of cells are negligible.



Taking $E_1 = 2.05$ only

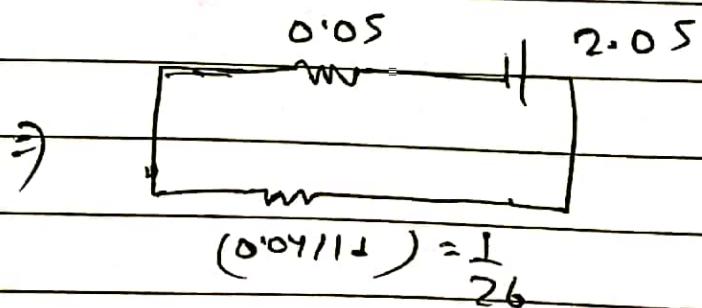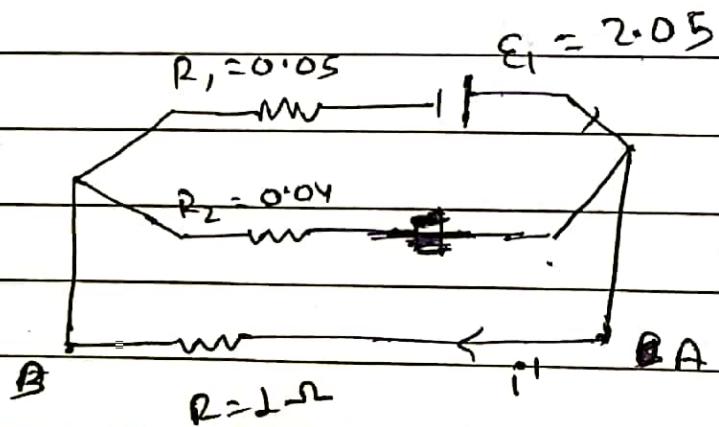



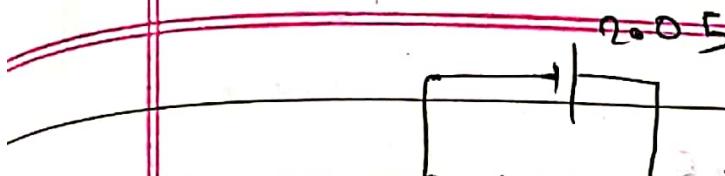


$$R_{eq} = 23/260$$

$$I = \frac{22.05}{0.088} = \frac{V}{R_{eq}} = 23.17 A$$

$$i' = \frac{0.04}{1+0.04} \times 23.17 = 0.89 A$$

Taking $\epsilon_2 = 2.15$ only

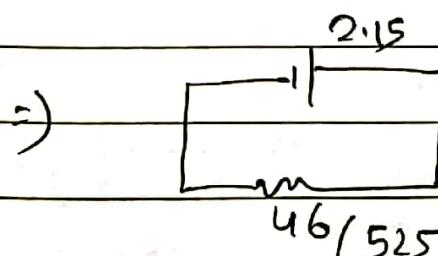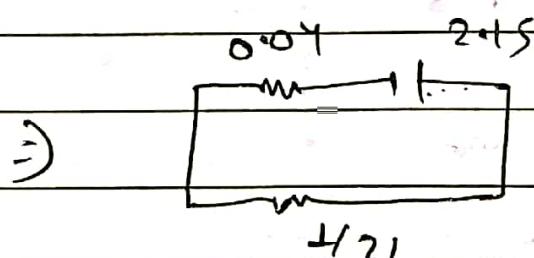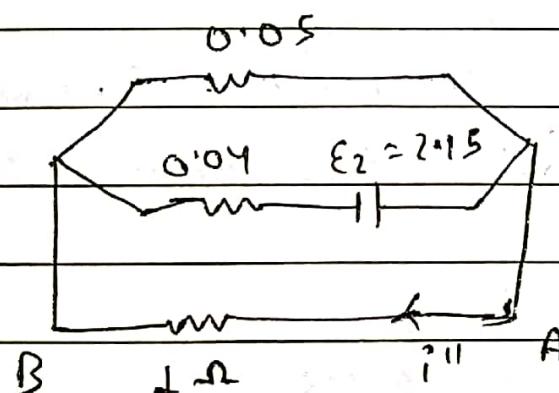

$$46/525$$

$$I = 2.15$$

$$46/525$$

$$= 24.53 \text{ A}$$

$$i' = 0.05 \times 24.53$$

$$1 + 0.05$$

$$= 1.168 \text{ A}$$



Now


$$\text{Total current } i = i' + i''$$

$$= 0.89 + 1.168$$

$$= 2.06 \text{ A}$$

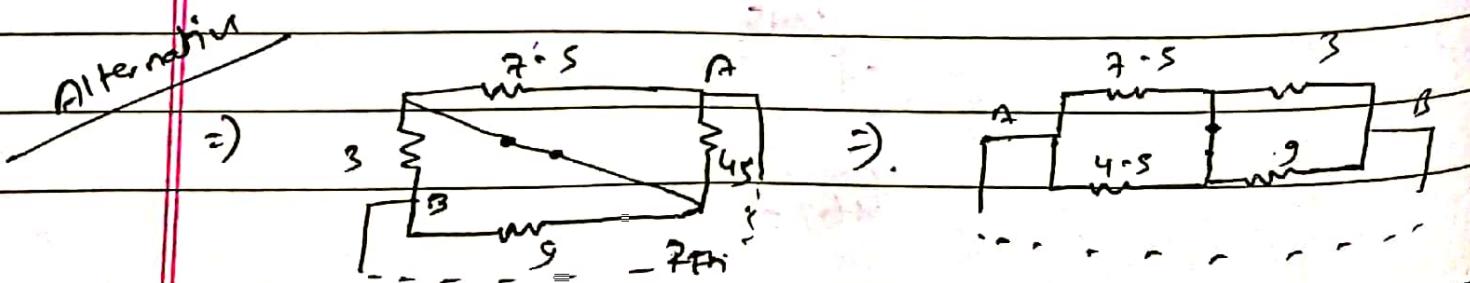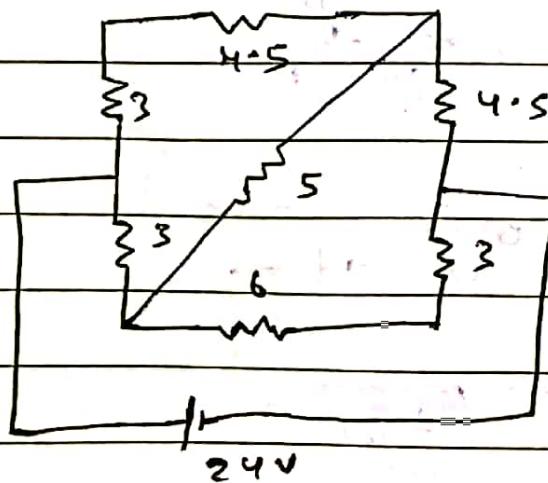
6. Calculate using Thevenin's Theorem the current through the branch 5Ω of fig 6



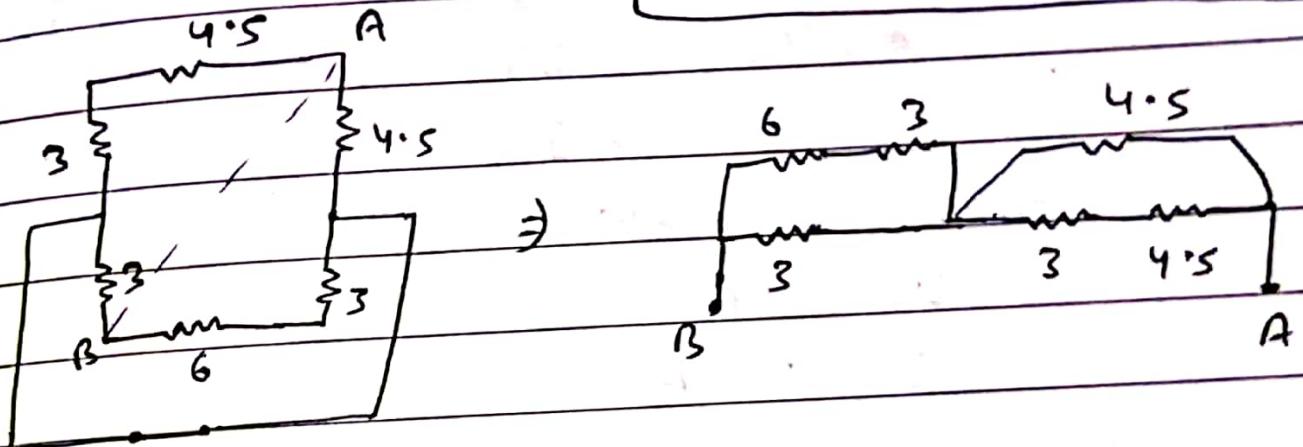

$$\begin{aligned}
 P_{TH} &= [(6+3)/13] + [4.5/1(3+4.5)] \\
 &= [9/13] + [4.5/17.5] \\
 &= 2.25 + 2.8125 \\
 &= 5.0625
 \end{aligned}$$

calculate of V_{TH}

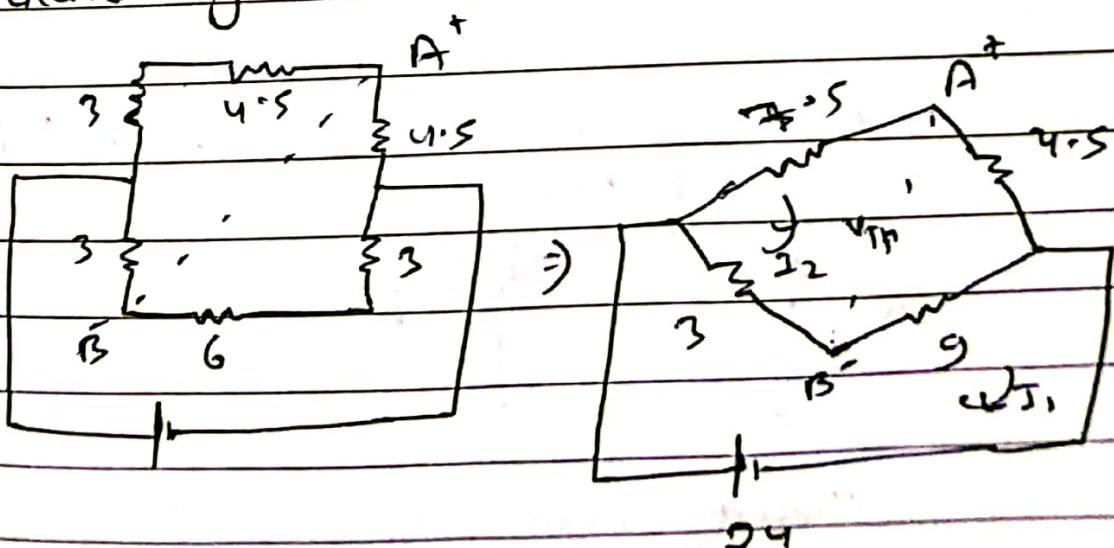

In Mesh 3

$$24 = 3(I_1 - I_2) - 5(I_1 - I_2)$$

$$+I_1 - I_2 = +2 \quad \textcircled{1}$$

In Mesh II

$$3(I_2 - I_1) + 7 \cdot 5I_2 + 4 \cdot 5I_2 + 9(I_2 - I_1) = 0$$

$$\Rightarrow 24I_2 - 12I_1 = 0$$

$$I_1 - 2I_2 = 0$$

on calculating,

$$I_1 = 4A$$

$$I_2 = 2A$$

from fig,

current going from B to BA


$$-V_{Th} = 3(I_2 - I_1) + 7 \cdot 5I_2$$

$$V_{Th} = 3(2 - 4) + 7 \cdot 5(2)$$

$$V_{Th} = -6 + 15$$

$$V_{Th} = 9V \quad (\text{B to A})$$

Now Thevenin eq. ckt is

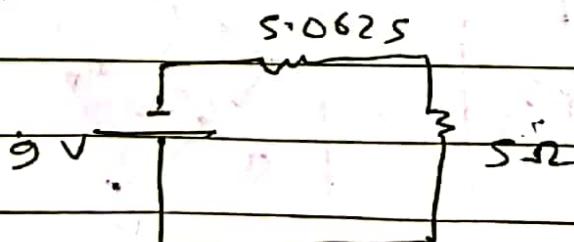

Current through 5Ω = 9

$$5.0625 \times 5 = 0.894A \cdot A_m$$